 


UNIT 4. CMOS


1.4. Design a XOR function with complementary CMOS logic. Estimate the number of transistors and compare with a traditional design based on logic gates.

Note: $F = A \oplus B = \overline{A}B + A\overline{B}$


$$F = \overline{\overline{A}B + A\overline{B}} = \overline{(A+B) \cdot (\overline{A}+\overline{B})}$$



12 transistors

 

Traditional:

 


22 transistors

We save 10 designing directly using transistors!

UNIT 4. CMOS

2.1. Given a NMOS transmission gate with a transistor of $|V_T| = 1.5V$. A voltage of 0V is applied to the input and 5V to gate terminal G. What voltage is obtained at its output?:

- A) 5V
- B) 0V
- C) 3.5V
- D) 1.5V

 

$$V_{GS} > V_T \Rightarrow V_G - V_S > V_T \Rightarrow \\ V_S < V_G - V_T; \quad V_o < V_G - V_T = 3.5V$$