



# UNIT 1: THE PROCESSOR

---

Estructura de Computadores (Computer Organization)

Course 2018/2019

ETS Ingeniería Informática

Universitat Politècnica de València

# Unit goals

- To understand the resources needed for the execution of a simple, yet sufficient instruction subset of MIPS
- To understand the phases involved in the execution of instructions
- To design a simple datapath and hardwired control unit for a limited subset of MIPS
- To evaluate the design and to explore further alternatives
- Context: MIPS 32 architecture, using a reduced version of the MIPS R2000 processor

# Unit contents


- 1 An overview of the MIPS32 architecture
- 2 Datapath design
  - Introduction
  - Instruction subset
  - Components
  - Execution phases
  - Complete datapath
    - R-type instructions
    - Memory access instructions
    - Conditional branch instruction (beq)
      - Unconditional branch instructions (j, jr) in lab session 10
- 3 Control unit design
  - Hardwired CU
  - Evaluation
  - Other alternatives

# Bibliography

- D. Patterson, J. Hennessy. *Computer organization and design. The hardware/software interface*. 4<sup>th</sup> edition. 2009. Elsevier
  - Chapter 2 and chapter 4, sections 4.1 to 4.4
  - Annex D for further reading on microprogrammed control unit

# 1. MIPS32 architecture: an overview

## Components of a computer system

 

# Architecture vs. implementation

- Architecture
  - Denotes the instruction set, registers, memory management (including virtual memory), memory map, exception system, etc.
    - In summary, anything the *system programmer* needs to know about the underlying machinery
- Implementation
  - The realization of the features specified by the architecture – or how the processor applies the architecture specification

Instruction set version (*)	Registers width	Processors
MIPS I	32	R2000, R3000
MIPS II	32	R6000
MIPS III	64	R4000
MIPS IV	64	R5000, R10000,...
MIPS V	64	-


(\*) Note: MIPS32 is a superset of MIPS I and MIPS II

*Further info:*  
[https://en.wikipedia.org/wiki/List\\_of\\_MIPS\\_microarchitectures](https://en.wikipedia.org/wiki/List_of_MIPS_microarchitectures)  
<https://imgtec.com/mips/architectures>

# Main features of MIPS32 architecture

- RISC architecture (*Reduced Instruction Set Computer*)
  - A processor design especially amenable to *pipelining* (Unit 2)
  - MIPS = **M**icroprocessor with **I**nterlocked **P**ipeline **S**tages)
- 32-bit word size (largest data handled by single instruction)
- Main data sizes
  - byte (8-bit, *B*), half word (16-bit, *H*), word (32-bit, *W*)
- Load/store architecture
  - Only *load* and *store* instructions do access data in memory
  - All operands for arithmetic/logic instructions reside in registers
  - 3-operand A/L instructions (32-bit registers)
- Main operating modes
  - User – restricted, for regular user programs
  - Kernel – unrestricted, for the OS

# Hardware model

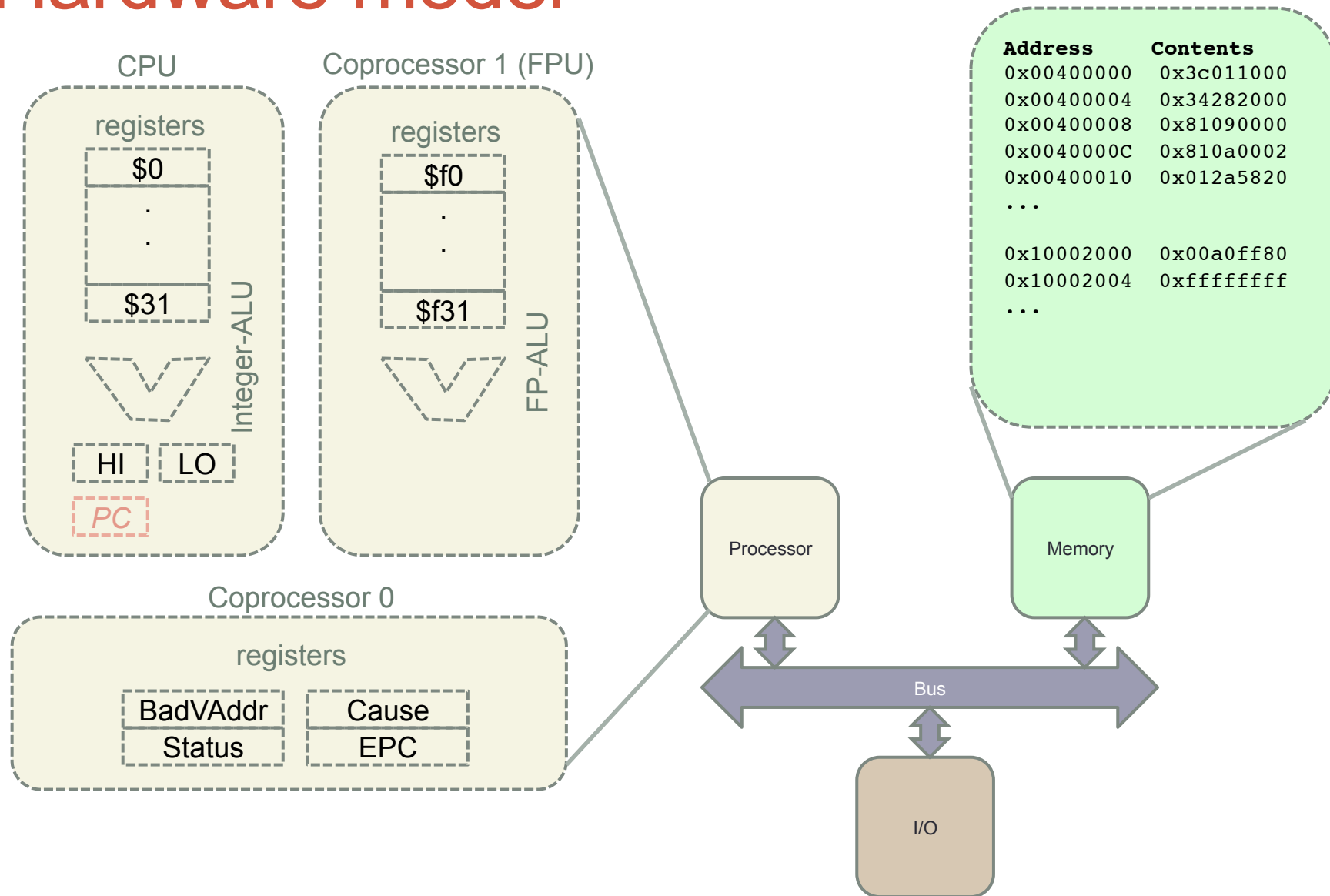




# Programming model – resources

- CPU
  - Thirty two 32-bit registers (\$0..\$31)
  - Integer Arithmetic-Logic Unit
  - HI and LO registers used for integer multiplication and division
  - Program counter (PC) points to next instruction to execute. The PC is not architecturally-visible, but is indirectly modified by certain instructions
- Coprocessor 0
  - Control resources (OS calls, operating modes, interrupts...)
    - 4 registers shown in previous slide, but there are more
- Coprocessor 1 (floating-point unit, optional)
  - Thirty two 32-bit floating-point registers (\$f0..\$f31)
  - Floating-Point Unit
    - Single-precision arithmetic (32 registers)
    - Double-precision arithmetic (16 pairs of 32-bit registers)


# Programming model – registers

Name	Reg Nr.	Conventional use – not enforced by the hardware, except (*)
\$zero	\$0	Hardwired, constant 0 (*)
\$at	\$1	Assembler temporary
\$v0-\$v1	\$2-\$3	Return of function results
\$a0-\$a3	\$4-\$7	Function arguments (parameters)
\$t0-\$t7	\$8-\$15	Temporary registers
\$s0-\$s7	\$16-\$23	Callee-saved temporary registers
\$t8-\$t9	\$24-\$25	Temporary registers
\$k0-\$k1	\$26-\$27	Used by the OS
\$gp	\$28	Global pointer (static global vars.)
\$sp	\$29	Stack pointer (local vars.)
\$fp	\$30	Frame pointer
\$ra	\$31	Return address (*)
\$f0-\$f31	\$f0..\$f31	Floating-point registers

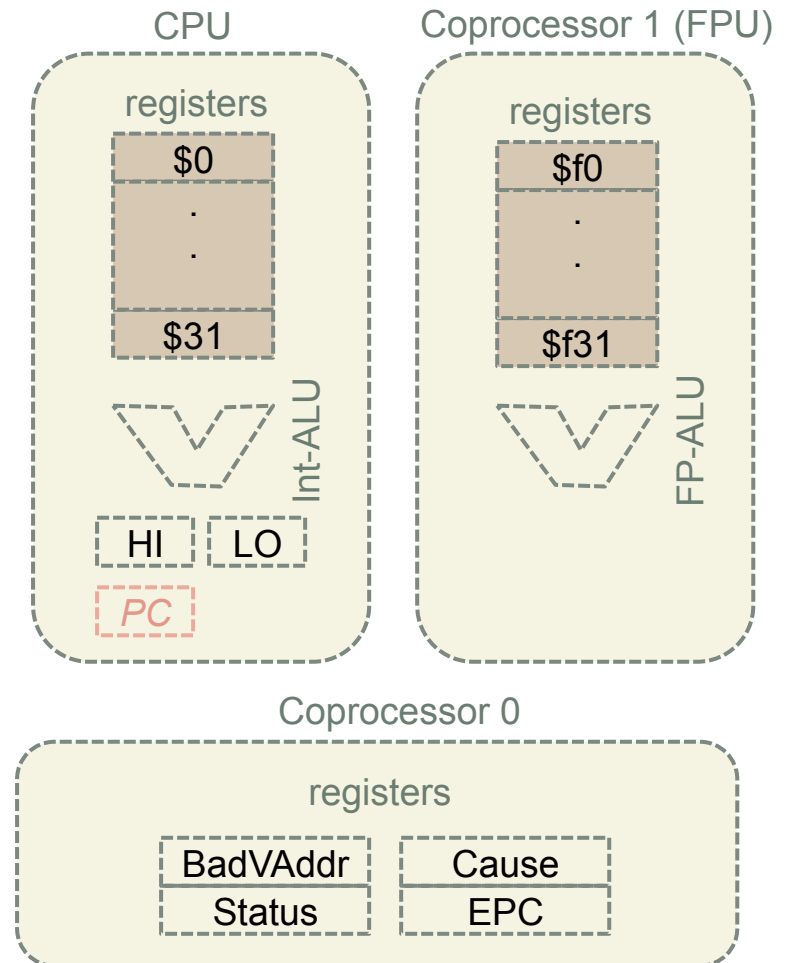

# Programming model – the memory

- Addressing space

 

# Programming model – the memory

- The memory layout of a program can be determined with assembly directives
  - Memory segment directives
    - `.data [address]` – start of a data segment
    - `.text [address]` – start of a code segment
    - `.end` – end of program code
  - Data allocation directives
    - `.byte b1 [,b2] ...` – bytes with initial values
    - `.half h1 [,h2] ...` – half words (16-bit)
    - `.word w1 [,w2] ...` – words (32-bit)
    - `.space n` – reserves  $n$  bytes
    - `.ascii string1 [,string2] ...` – char strings
    - `.asciiz string1 [,string2] ...` – null-ended char strings
  - *Labels ( $A$ ,  $W$ ,  $V$ ,  $C1$ ,  $C2$ ) improve readability – and make life easier!*

```
                .data 0x10000000
A:              .byte 2, 3, 4
W:              .word 33
V:              .space 100

                .data 0x10004000
C1:             .ascii "hello"
C2:             .asciiz "goodbye"

                .text 0x00400000
                lb $t0,A
                lw $t1,W
                ...
                .end
```

# Programming model – the memory

- Addressing
  - Byte-level addressing – every byte in memory has its own address
    - A byte is the smallest amount of accessible data in memory
  - MIPS32 supports both big-endian and little-endian modes
- Data alignment
  - A byte may reside in any address
  - A half word must start in an even address (multiple of 2)
  - A word must start in an address multiple of 4
    - (In MIPS64, *double words* correspondingly start in multiples of 8)
  - The assembler directive
    - `.align N`  
overrides automatic alignment of `.half`, `.word`, etc. and enforces alignment to next address multiple of  $2^N$ , creating a “gap” in the data segment, if needed
    - `.align 0` switches auto-alignment off – packed data

# Programming model – instructions

- Instruction groups

  - Arithmetic

  - Shift and rotate

  - Register transfer

  - Load and store

  - Others

  - Logical (bitwise)

  - Condition test (comparison)

  - Floating-point

  - Branch

- Syntax and encoding

  - <http://www.mrc.uidaho.edu/mrc/people/jff/digital/MIPSir.html>

  - [http://en.wikipedia.org/wiki/MIPS\\_architecture](http://en.wikipedia.org/wiki/MIPS_architecture)

- Instructions vs. pseudo-instructions

  - Instructions are directly supported by the hardware

  - Pseudo-instructions require the assembler to generate proper instructions

# Code in action: example

Data segment starts at address 0x10002000

Labels for easier data reference:  
a = 0x10002000  
c = 0x10002004

```
.data 0x10002000
a: .byte 0x80, 0xFF, 0xA0, 0x00
c: .word -1
```

Data segment layout  
(0x10002000 – 0x10002007)

0x10002000: 0x80  
0x10002001: 0xFF  
0x10002002: 0xA0  
0x10002003: 0x00  
0x10002004: 0xFFFFFFFF

Code segment starts at address 0x00400000

```
.text 0x00400000
la $t0, a
lb $t1, 0($t0)
lb $t2, 2($t0)
add $t3, $t1, $t2
sb $t3, 3($t0)
add $t1, $0, $0
.end
```


Add contents of \$t1 and \$t2 and leave result in \$t3

Store LSB of \$t3 in memory, at the address of a+3

Assembler directive for end of code


Assign register \$t0 the value of label a (0x10002000)

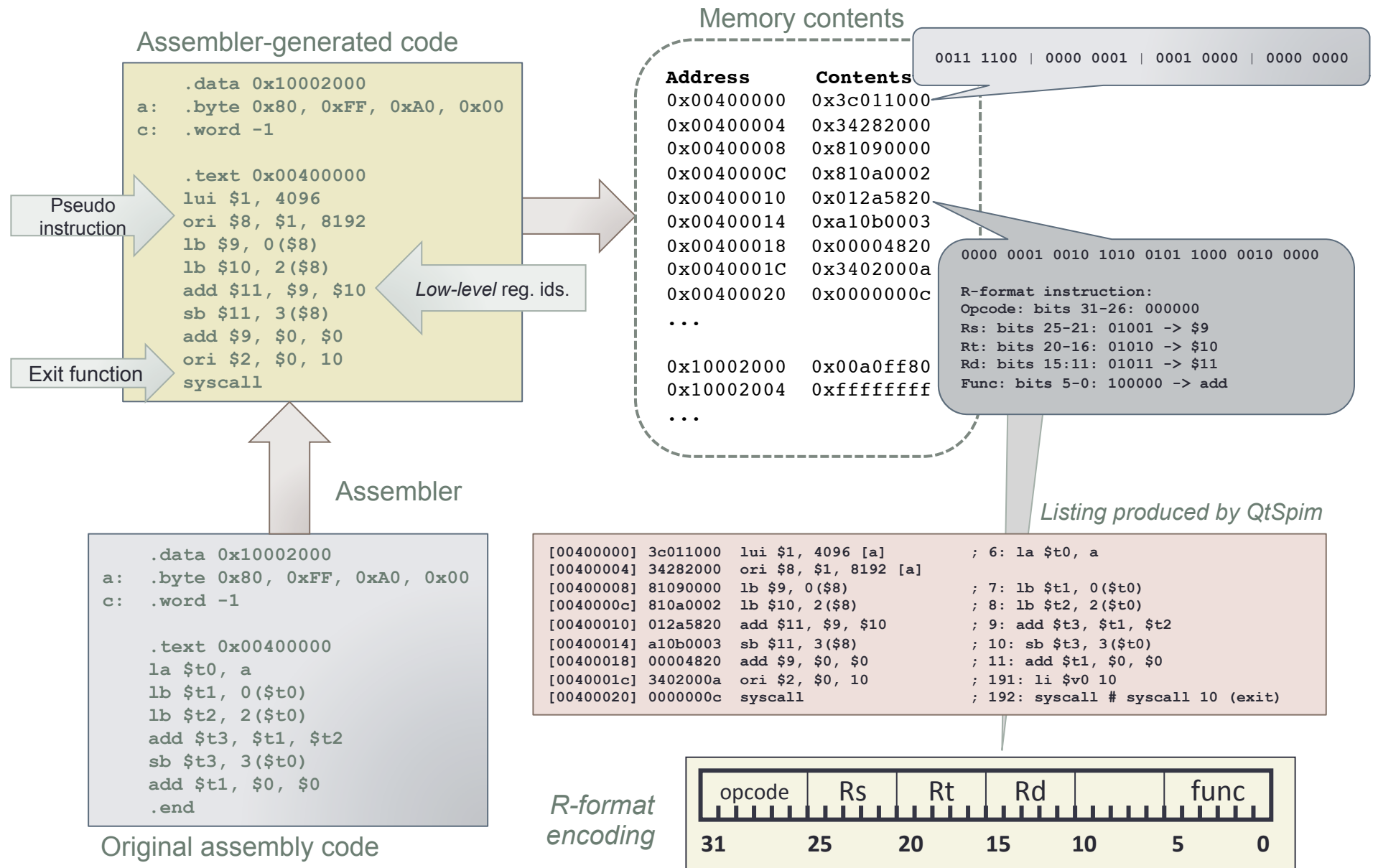Read two bytes from memory at addresses a and a+2, using registers \$t1 and \$t2







# Instruction 1

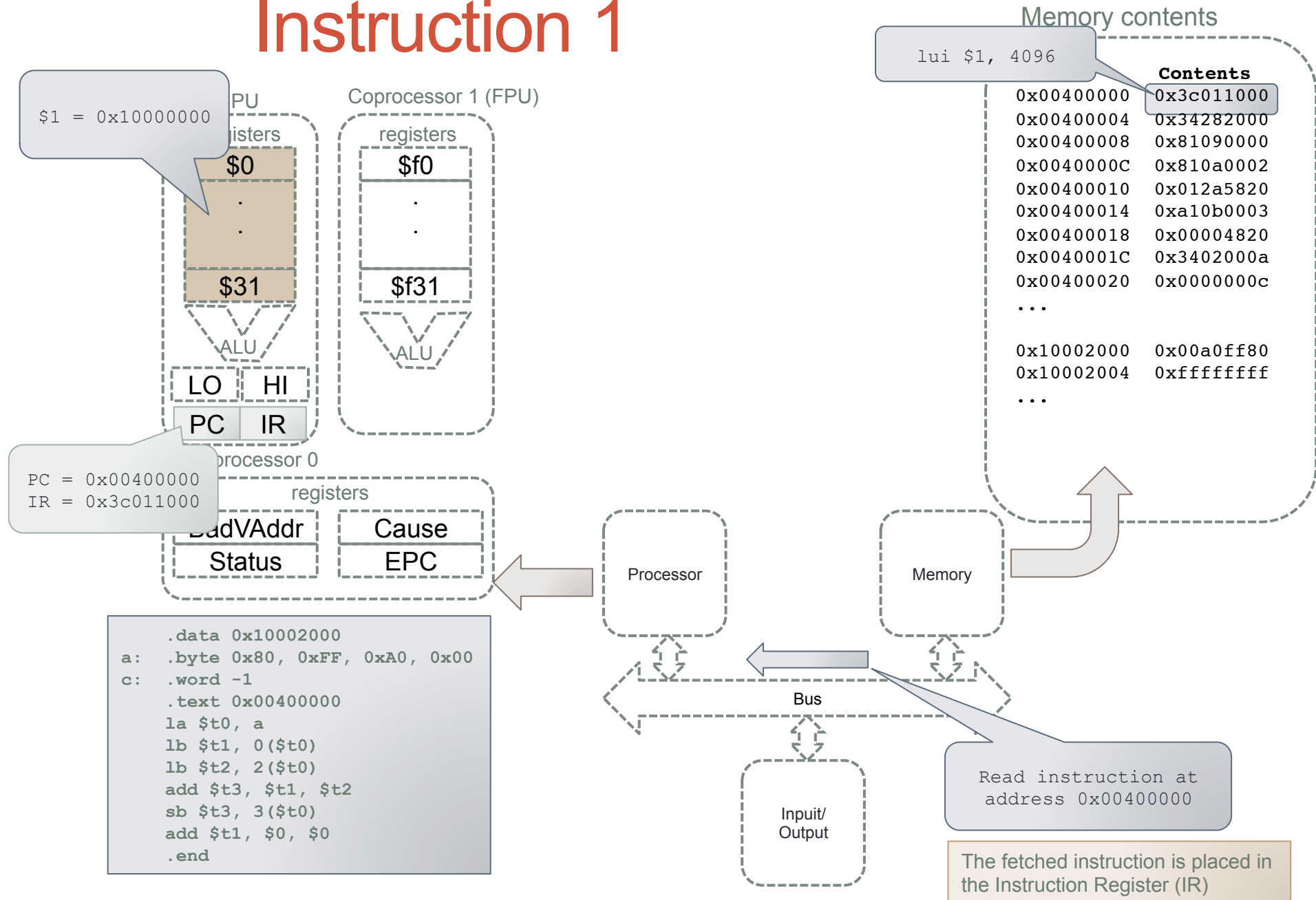


# Instruction 2

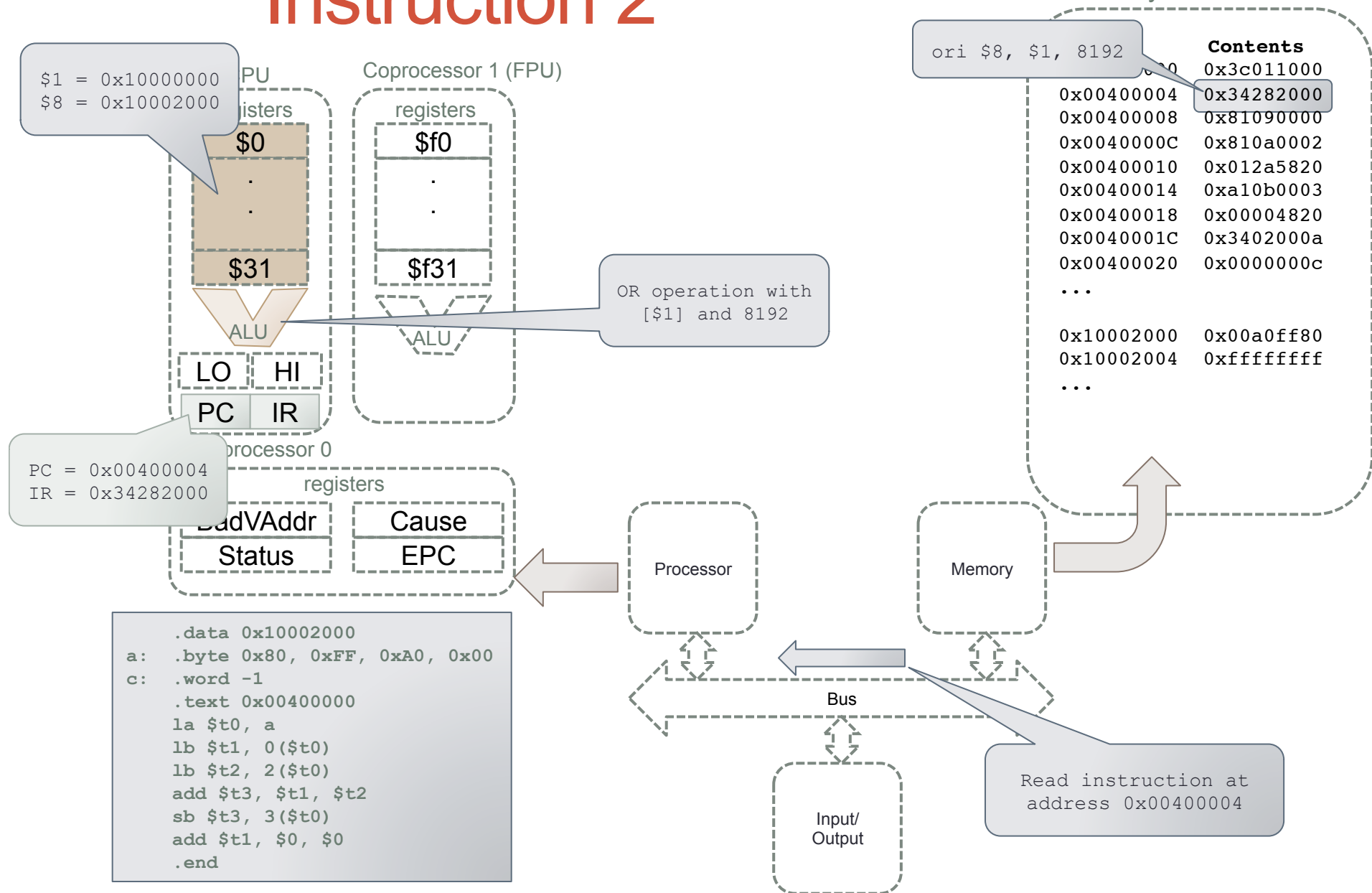


# Instruction 3

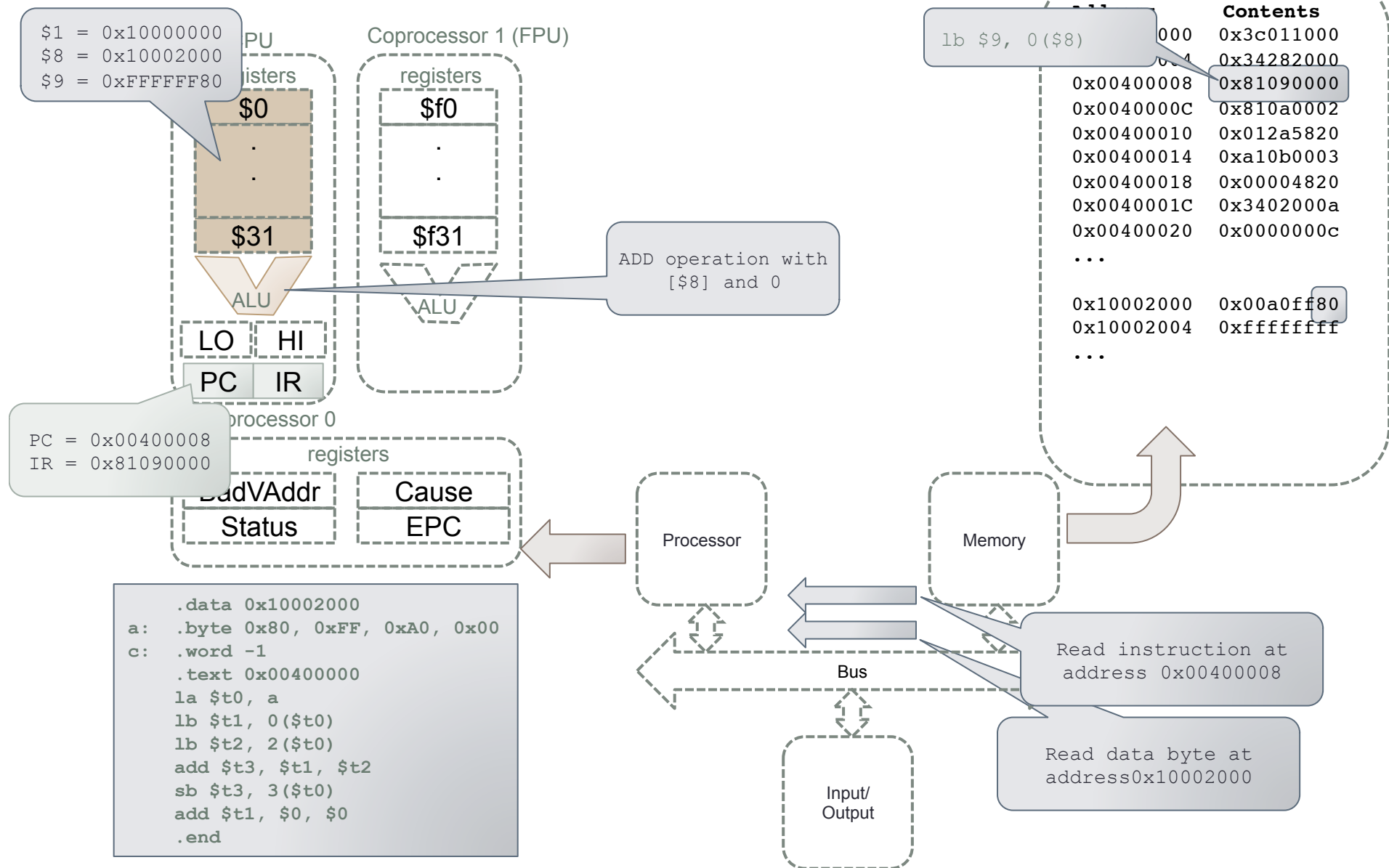


# Instruction 4

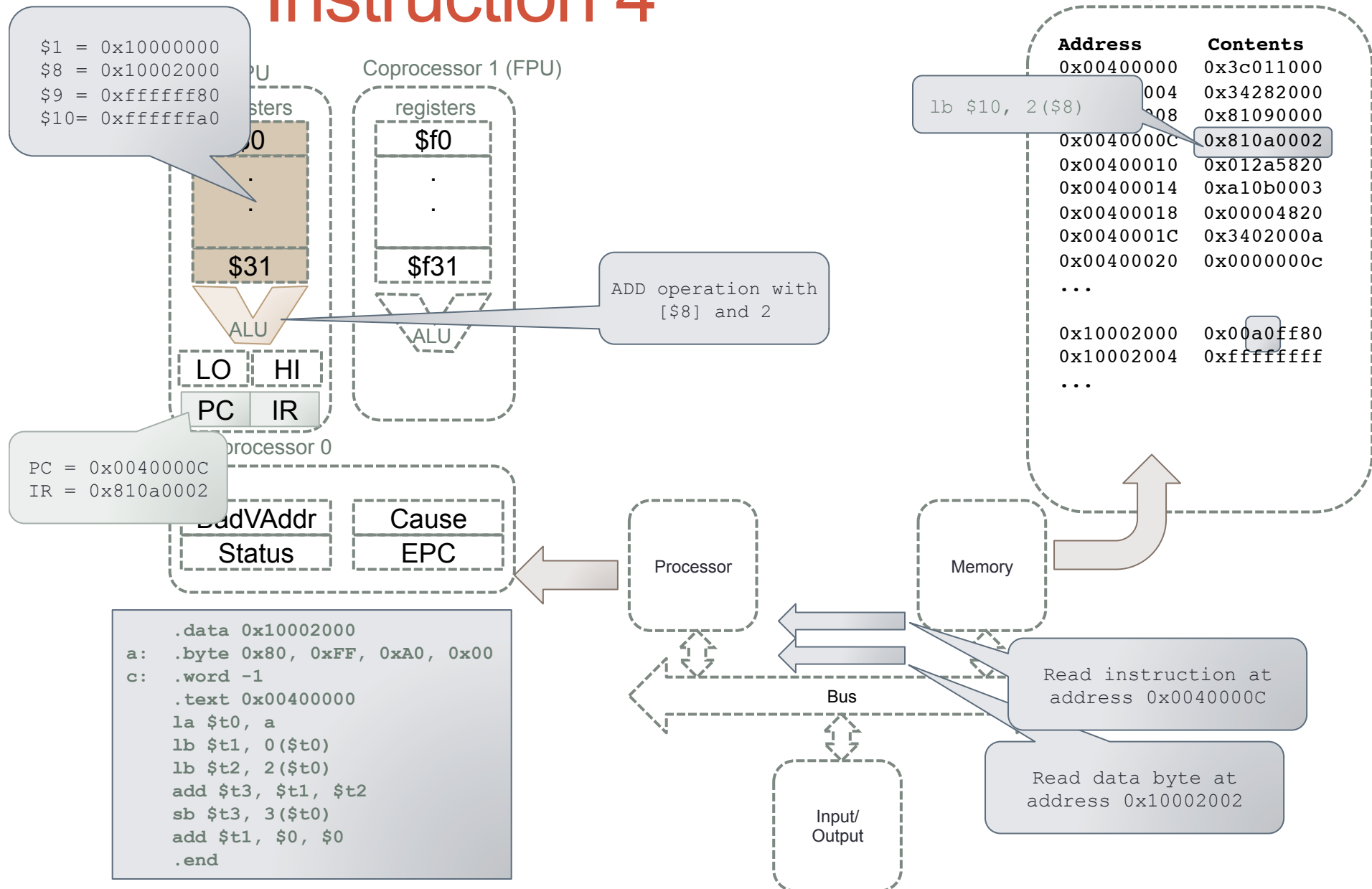


# Instruction 5

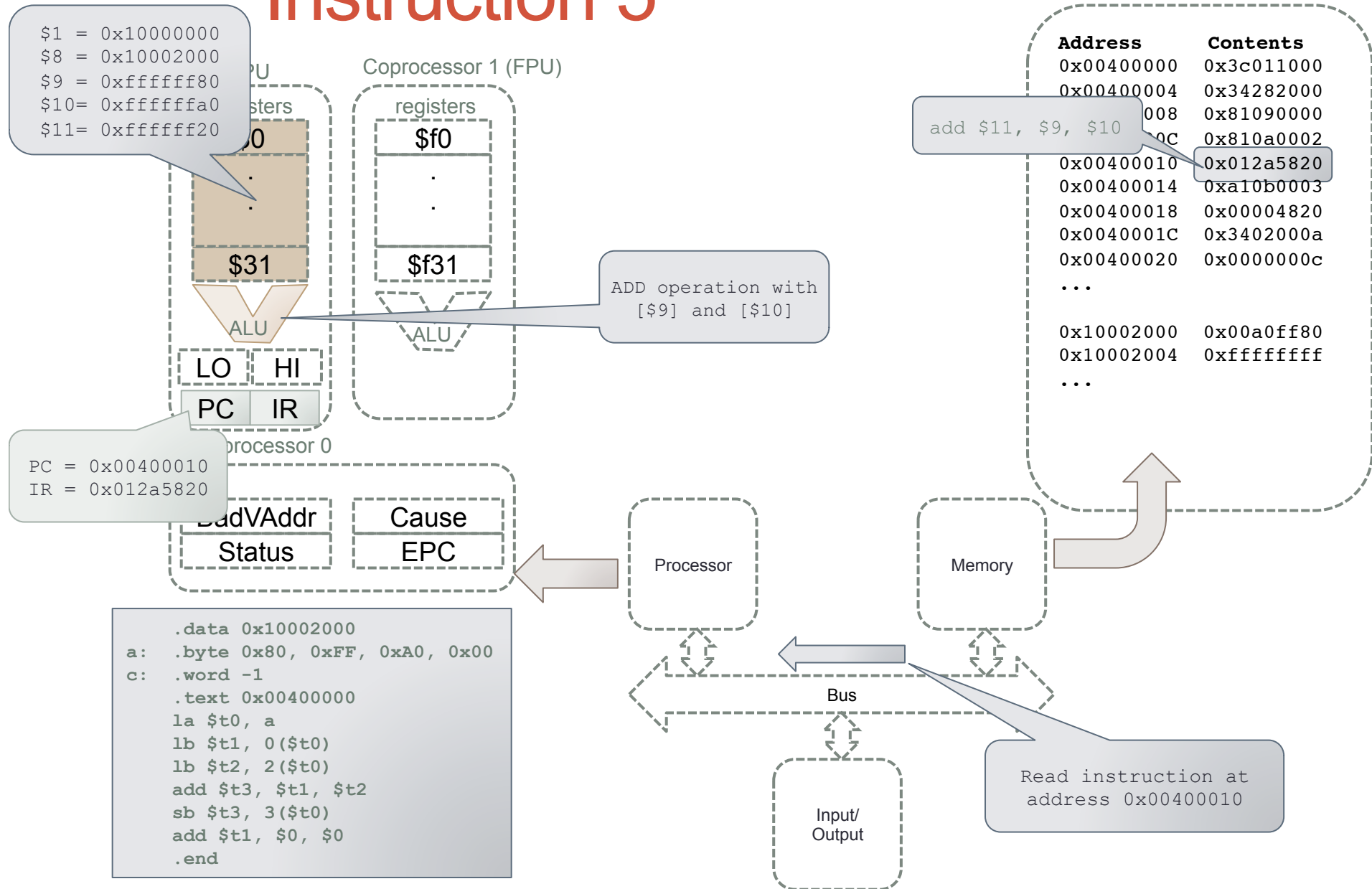


# Instruction 6

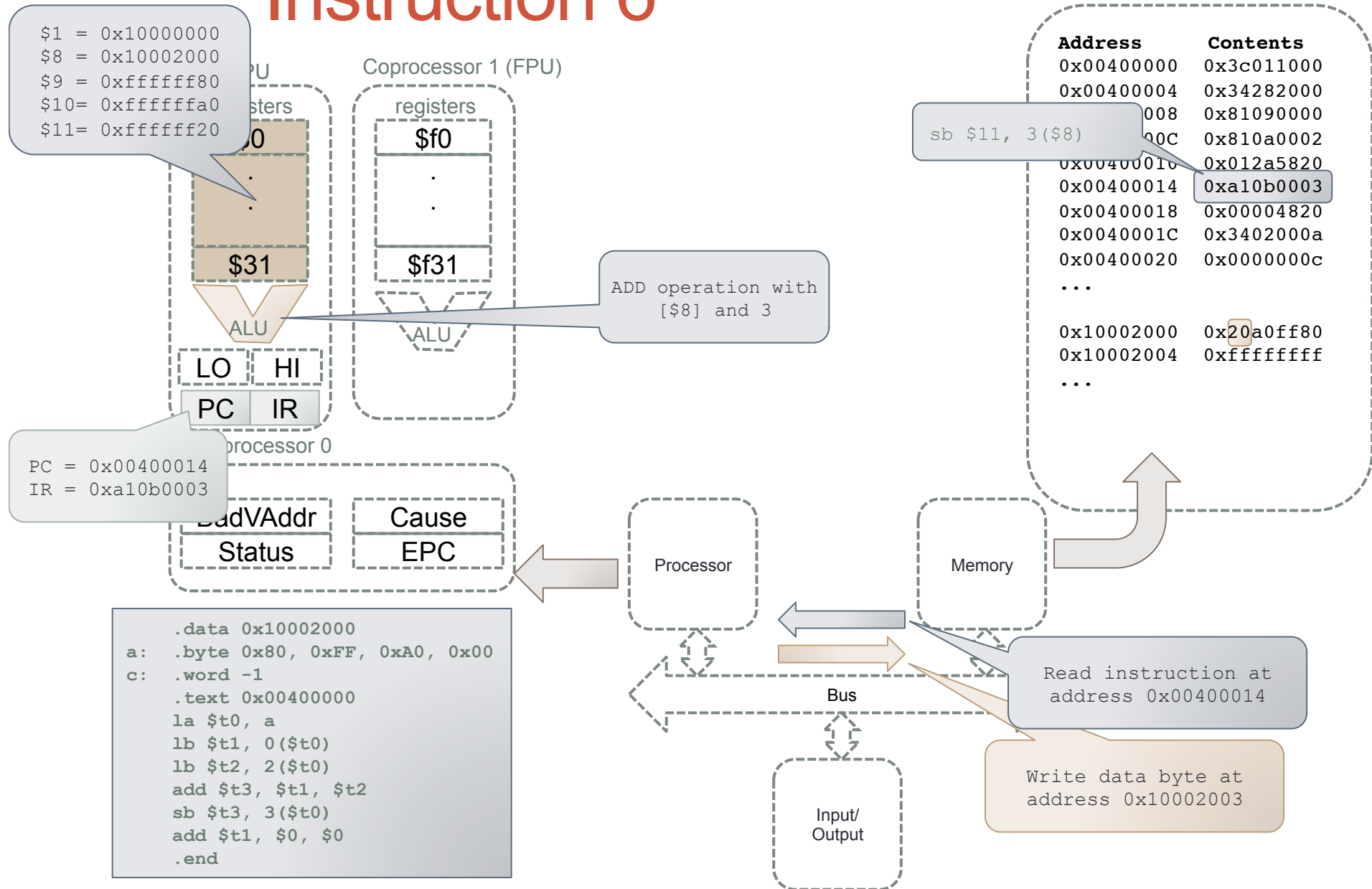

# Instruction 7

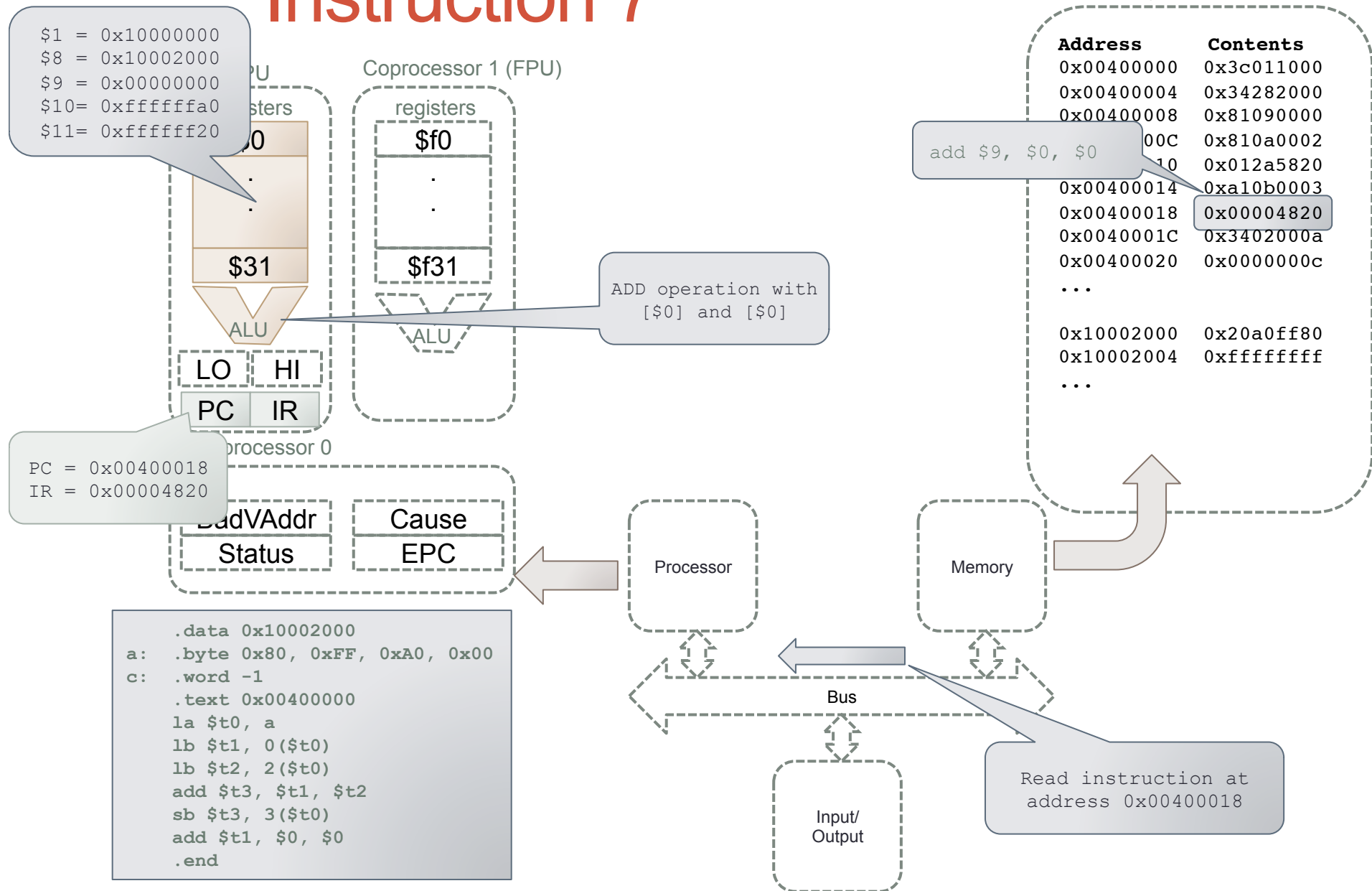


# Instruction 8

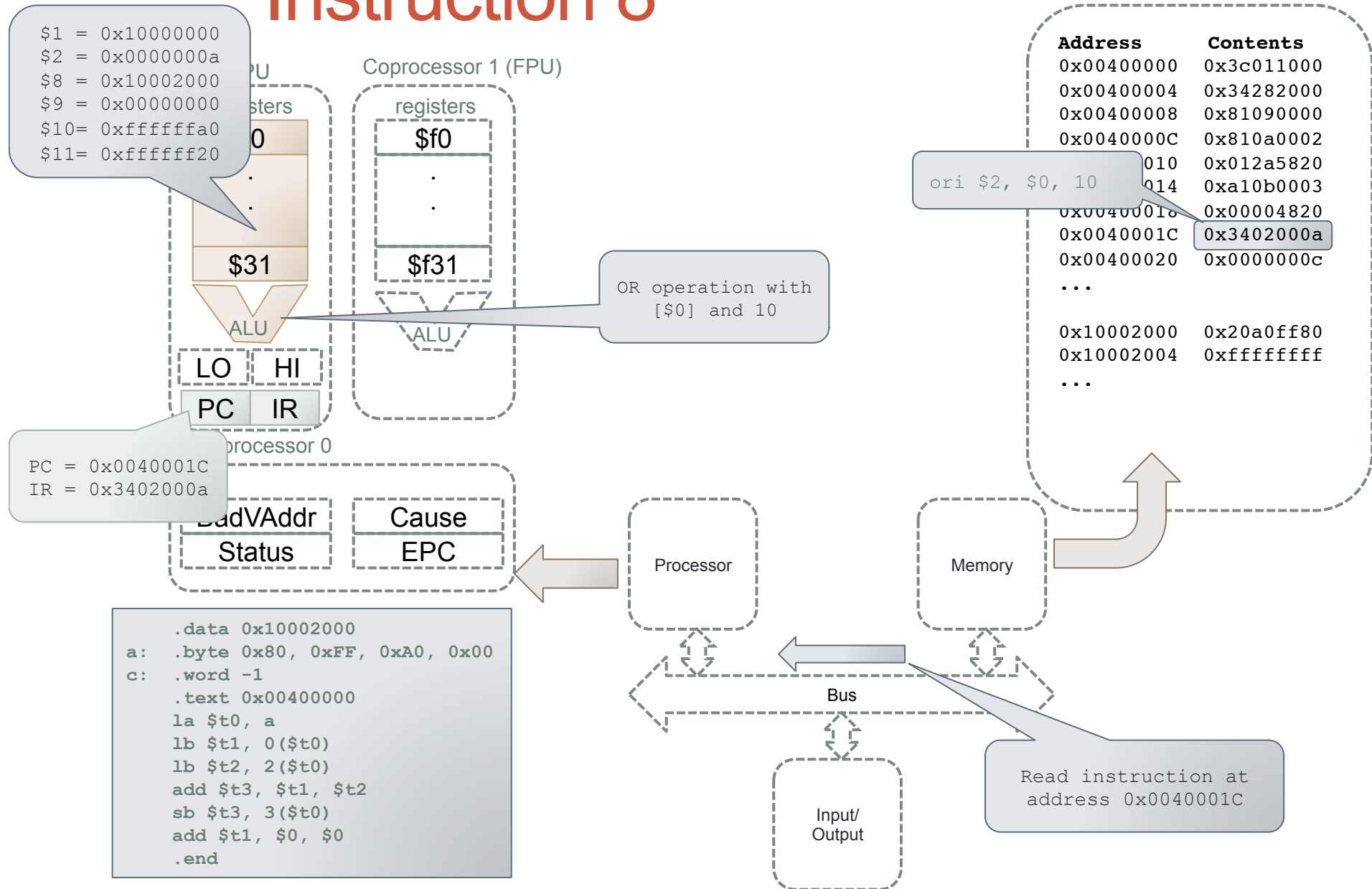




# Instruction 9

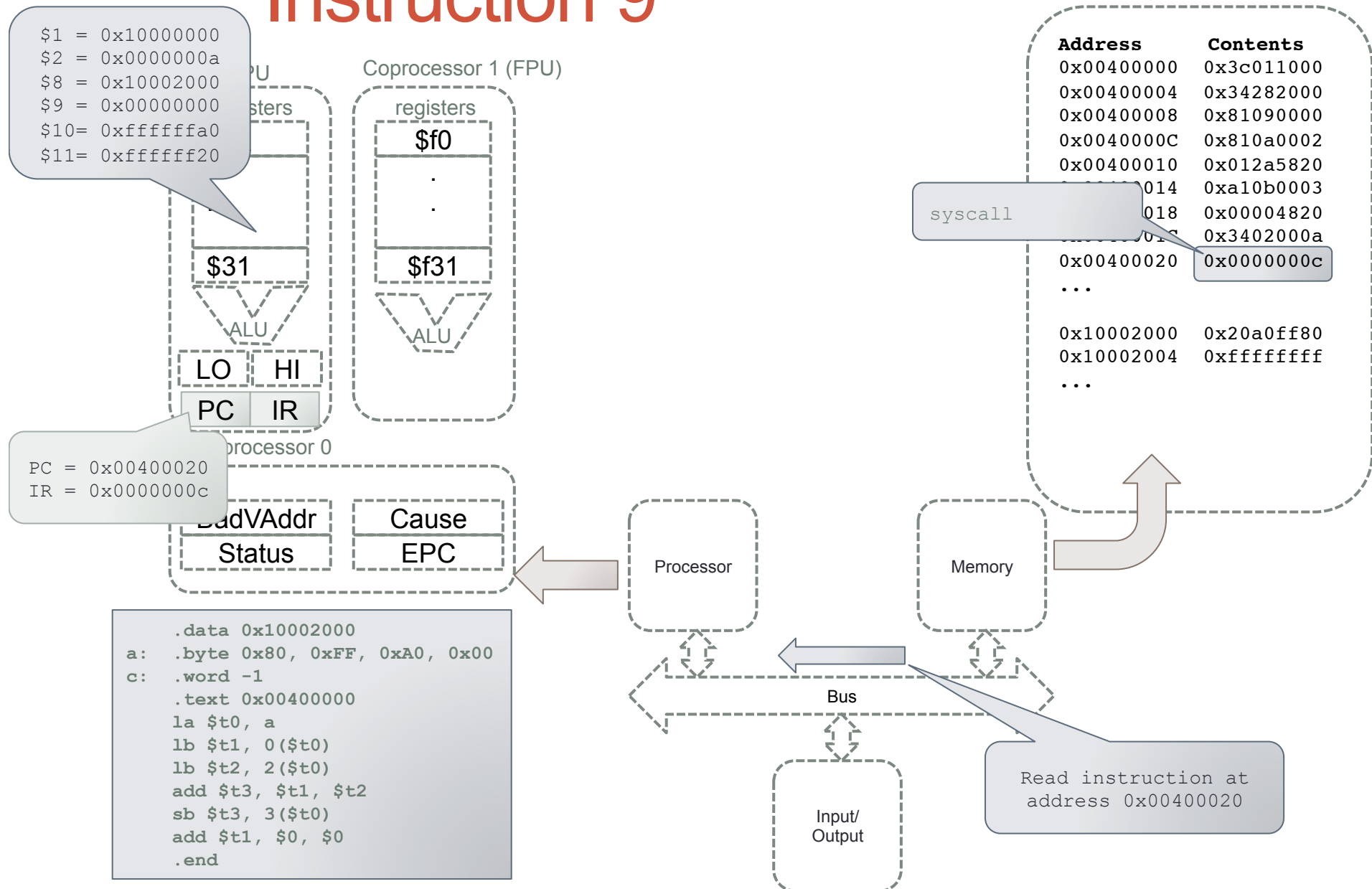

# MIPS32 this course

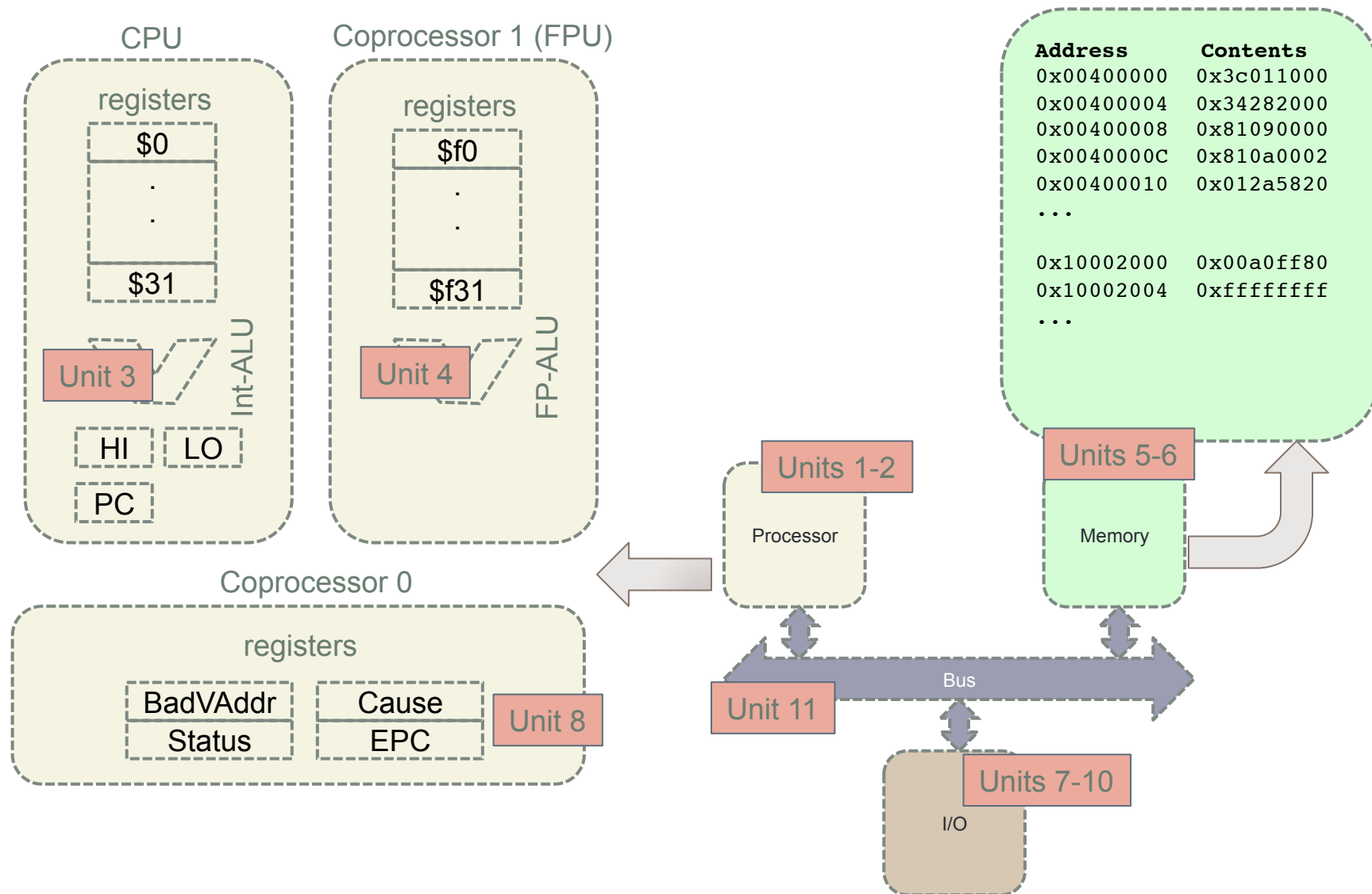


## 2 Datapath design – Introduction

- We will be visiting two processor designs:
  - A monocyte processor (this unit)
    - All instructions execute in a single CPU clock cycle
      - The clock period must accommodate the duration of the slowest instruction
      - The datapath connects functional units point-to-point, it has no *shared* busses
  - A pipelined processor (unit 2)
    - Instructions execute in multiple cycles, but the use of CPU resources is shared among several instructions executing at the same time
      - Hence we can have much shorter clock cycles
- The monocyte design will be the basis for the pipelined version
  - A bus-based datapath is not amenable to *pipelining* (see unit 2)

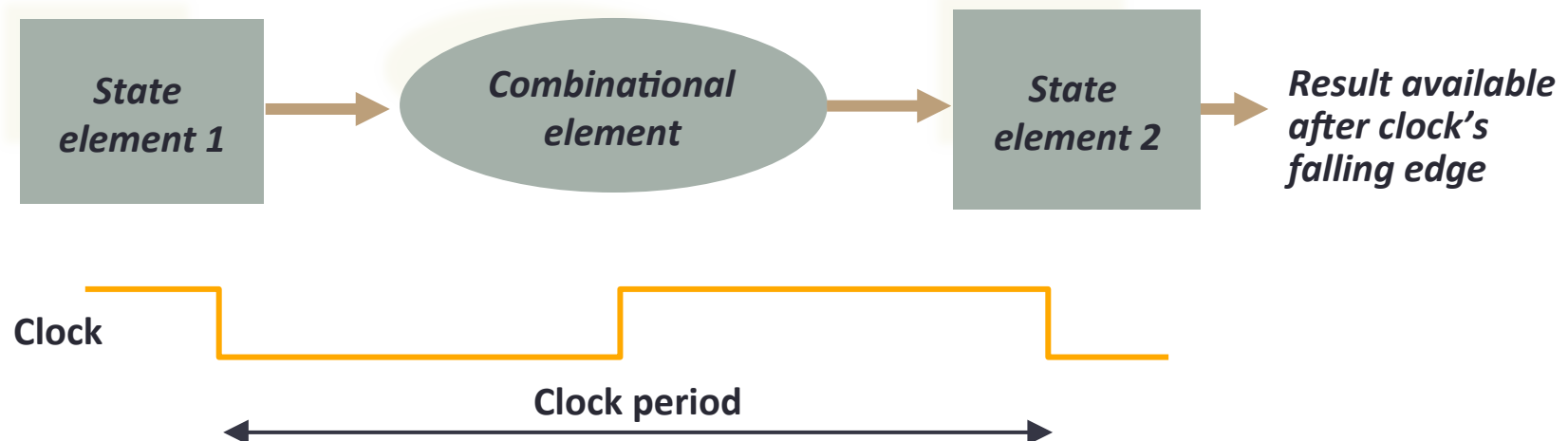
# Logic design conventions

- Two kinds of elements
  - Combinational – output depends on current inputs only
    - Eg., the ALU
  - State – output is kept until inputs change AND clock triggers AND write is enabled (if needed)
    - Eg., registers
- We'll consider edge-triggered clocking



 
# Logic design conventions

- Edge-triggered clocking enables reading and writing a state element in the same clock cycle (eg. a register in the register file)



- Example

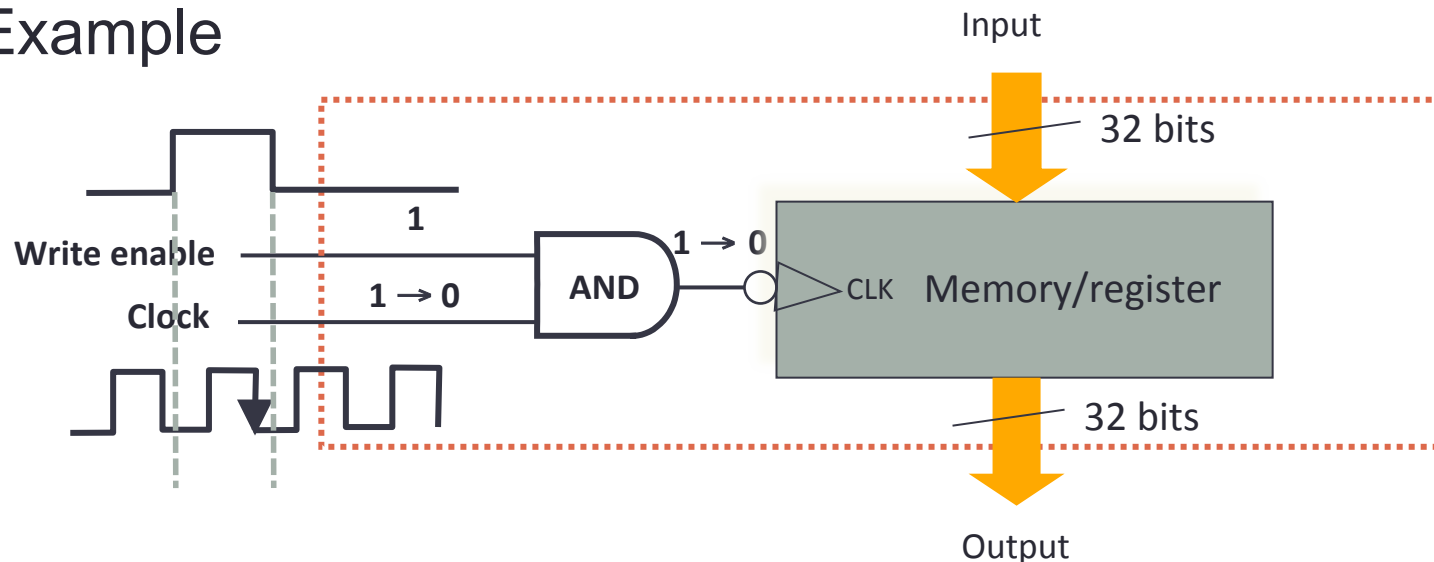


## 2 Datapath design

- Route to the design
  - Selection of the instruction subset
  - Selection of hardware components
  - Establishing execution phases
  - Complete datapath: putting it all together
    - R-type instructions
    - Memory access instructions
    - Conditional branch (`beq`)

# Instruction subset


- We will consider a minimal instruction subset:
  - Arithmetic and logic instructions
    - `add`, `sub`, `and`, `or`, `set on less than` (`slt`) – all in R and I format
  - Memory instructions
    - Load word and store word (`lw`, `sw`)
  - Conditional branch
    - Branch if equal (`beq`)
  - Unconditional branch
    - Jump (`j`) and register indirect jump (`jr`) – these will be considered in the lab

## Type R instructions

 


Instruction	Operation
<b>add rd,rs,rt</b>	$rd \leftarrow rs + rt$
<b>sub rd,rs,rt</b>	$rd \leftarrow rs - rt$
<b>and rd,rs,rt</b>	$rd \leftarrow rs \wedge rt$
<b>or rd,rs,rt</b>	$rd \leftarrow rs \vee rt$
<b>slt rd,rs,rt</b>	<b>if</b> $rs < rt$ <b>then</b> $rd \leftarrow 1$ <b>else</b> $rd \leftarrow 0$
<b>jr rs</b>	$PC \leftarrow rs$
 
## Type J instructions (to be used in a lab session)



Instruction	Operation
<b>j label</b>	$PC \leftarrow \text{label}$ ( $PC_{27-0} \leftarrow \text{target} * 4$ )

## Type I instructions

 

Instruction	Operation
<b>lw rt,offset(rs)</b>	$rt \leftarrow \text{mem}[rs + \text{offset}]$
<b>sw rt,offset(rs)</b>	$\text{mem}[rs + \text{offset}] \leftarrow rt$
<b>beq rs,rt,label</b>	<b>if</b> $rs = rt$ <b>then</b> $PC \leftarrow \text{label}$ ( $PC \leftarrow PC + 4 + \text{offset} * 4$ )
<b>Instructions with immediate operand</b>	
<b>&lt;op&gt; rt,rs,imm</b>	$rt \leftarrow rs \text{ op immediate}$



## Encoding

Instruction	Format	op	func (R-format)
<b>add</b>	R	000000	100000
<b>sub</b>	R	000000	100010
<b>and</b>	R	000000	100100
<b>or</b>	R	000000	100101
<b>slt</b>	R	000000	101010
<b>lw</b>	I	100011	
<b>sw</b>	I	101011	
<b>beq</b>	I	000100	
<b>j</b>	J	000010	
<b>jr</b>	R	000000	001000



  
# Memory

- Single-level hierarchy (ie. no cache), Harvard architecture
  - Instructions (read only)
    - The Instruction Register (IR) latches the current instruction
    - No need for READ signal: I-mem is always read
  - Data (read and write)
- Addressing space: 4 GB
- Bus width: 32 bits



 
# Program counter

- Instructions are fetched from the address pointed to by the *program counter* (PC)
- The PC needs to be incremented by 4 (except for branches)
- For branch instructions, the new PC is  $PC + 4 + (\text{offset} * 4)$ 
  - Offset is encoded in the instruction in 2'sC and must be sign-extended
- A multiplexer enables proper selection of the next PC



 
# Register file

- Thirty two 32-bit registers (\$0 to \$31)
- Three ports
  - Two read ports, simultaneous read of two registers
    - Always read two registers – discard if not needed
  - One write port
    - The written register may be one of the read registers


 
# ALU

- The ALU must support the operations of the subset
  - It will calculate addresses for memory instructions as well
- The operation is selected with bits **ALUOp**
- A zero flag (**Z**) indicates that the result is zero (for beq)




ALUOp	Operation
000	$A \wedge B$ (and)
001	$A \vee B$ (or)
010	$A + B$ (arithmetic add)
110	$A - B$ (subtraction)
111	$A < B$ (for slt)


# Additional multiplexers

- Three additional multiplexers are needed for selection in the following cases:
  - Operand 2 to ALU – it may be the 2<sup>nd</sup> source register (R format), or the sign-extended immediate (I format)
  - Destination register number – instruction bits 15..11 (R format) or 20..16 of the instruction (I format)
  - Written data to register file – it may be the ALU output (A/L instructions) or the data memory output (load instruction)


# Execution phases

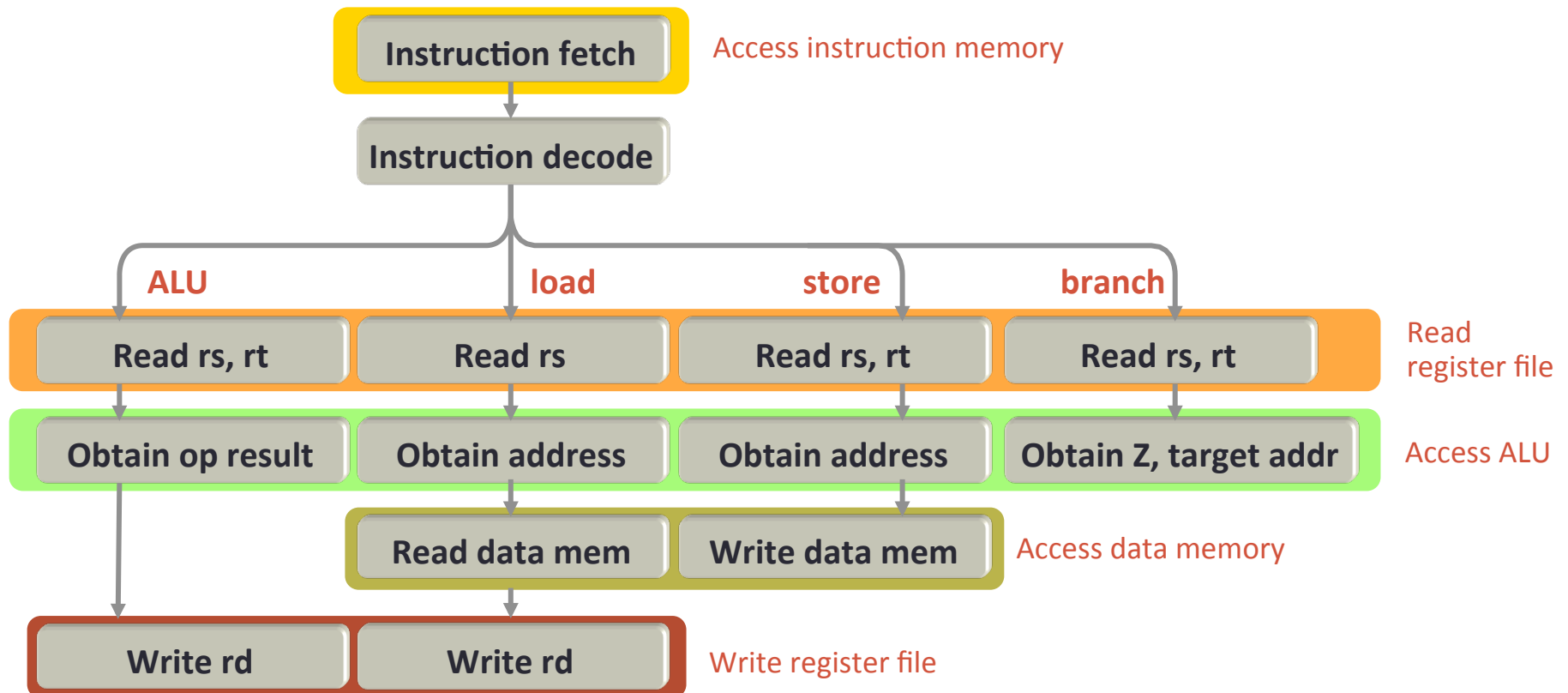

# Complete datapath

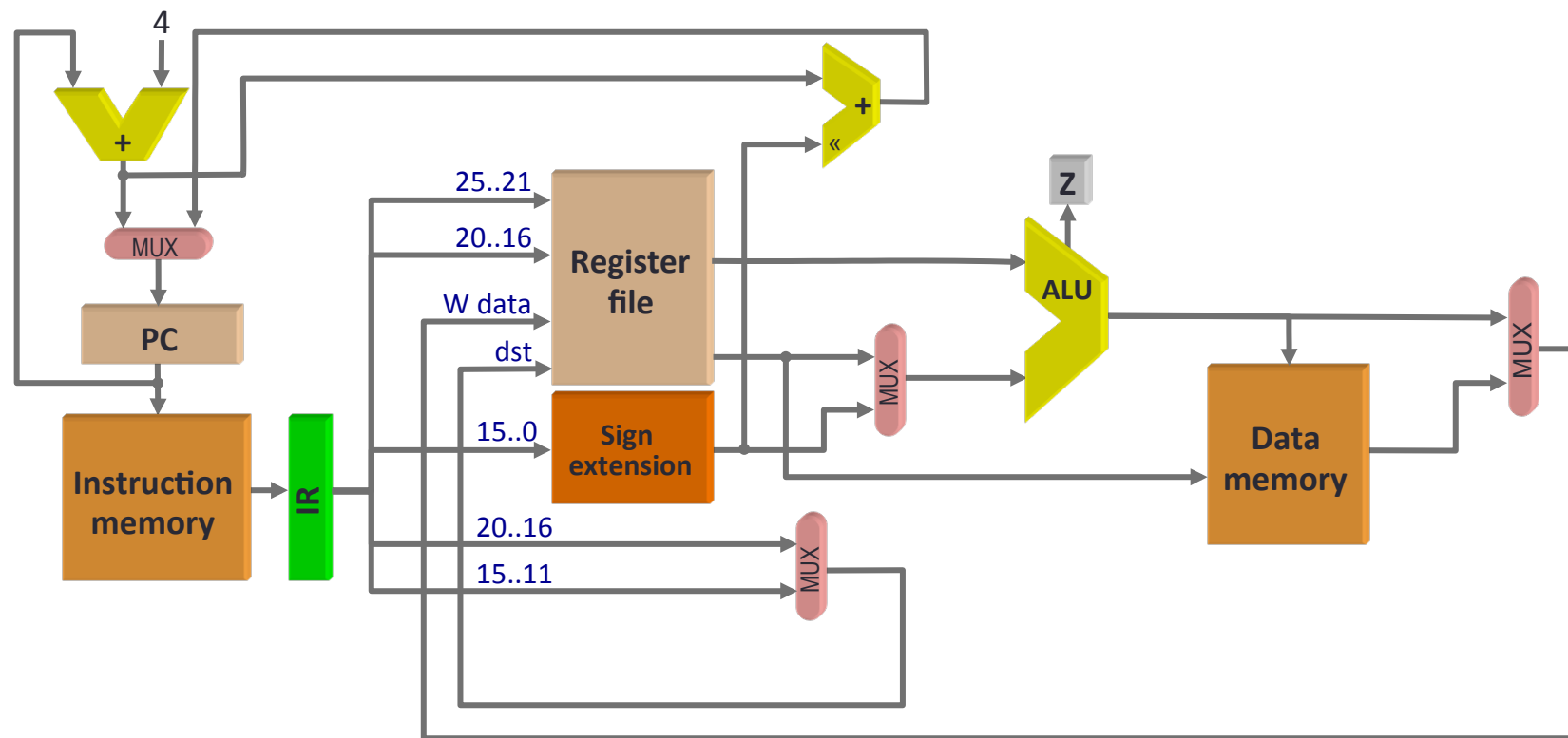


# R-type A/L instructions

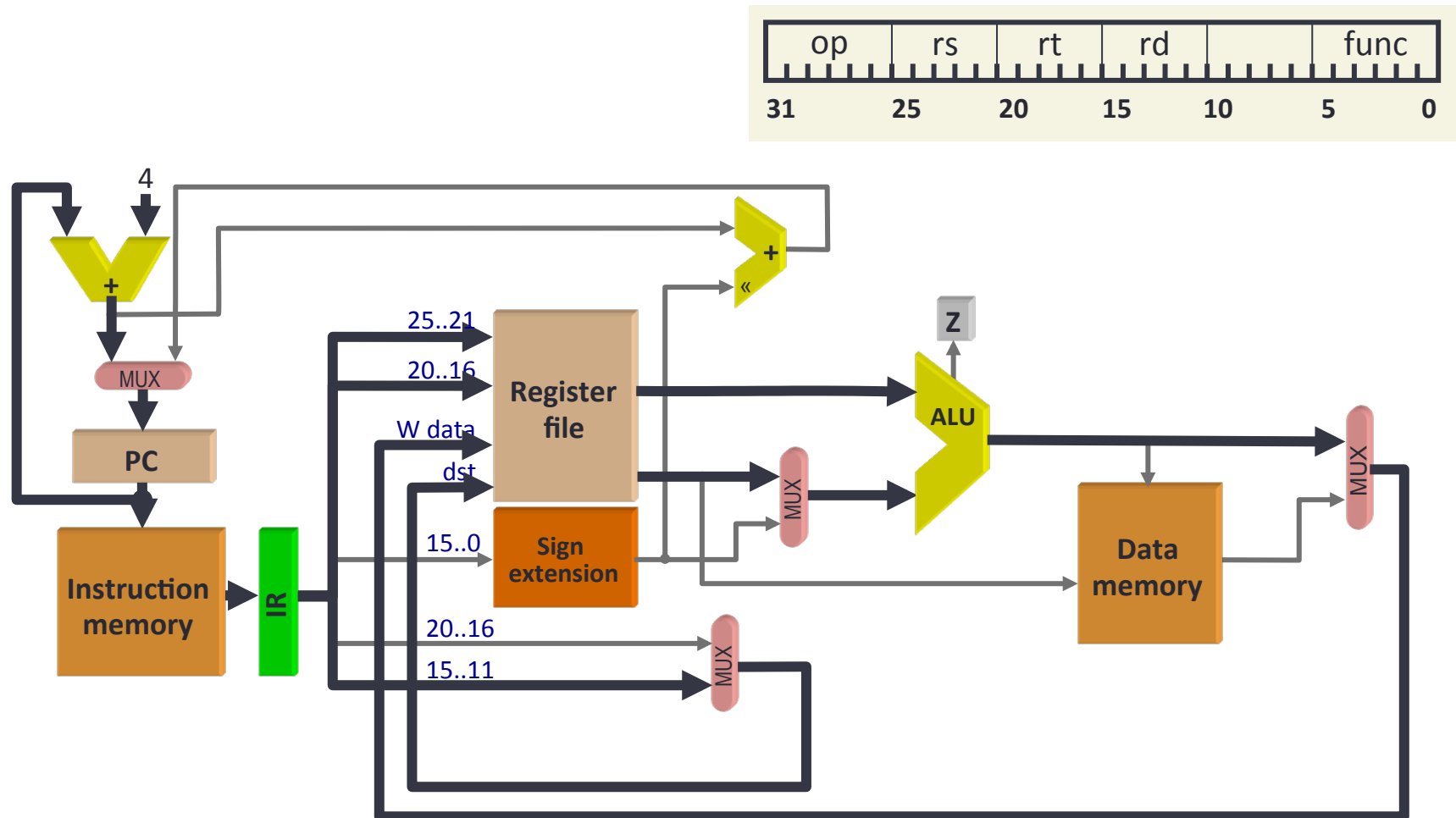





# I-type A/L instructions

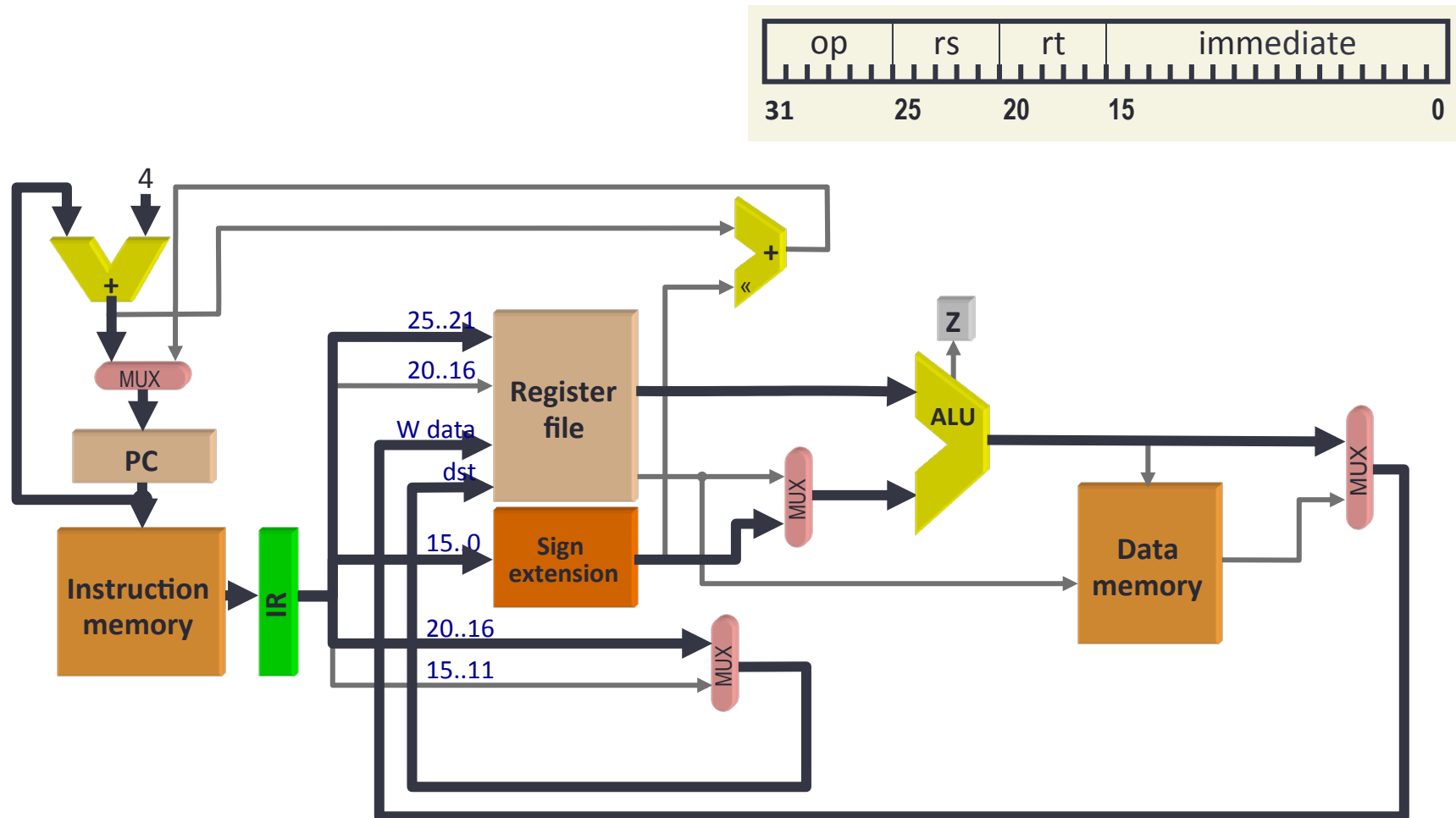



# Load word

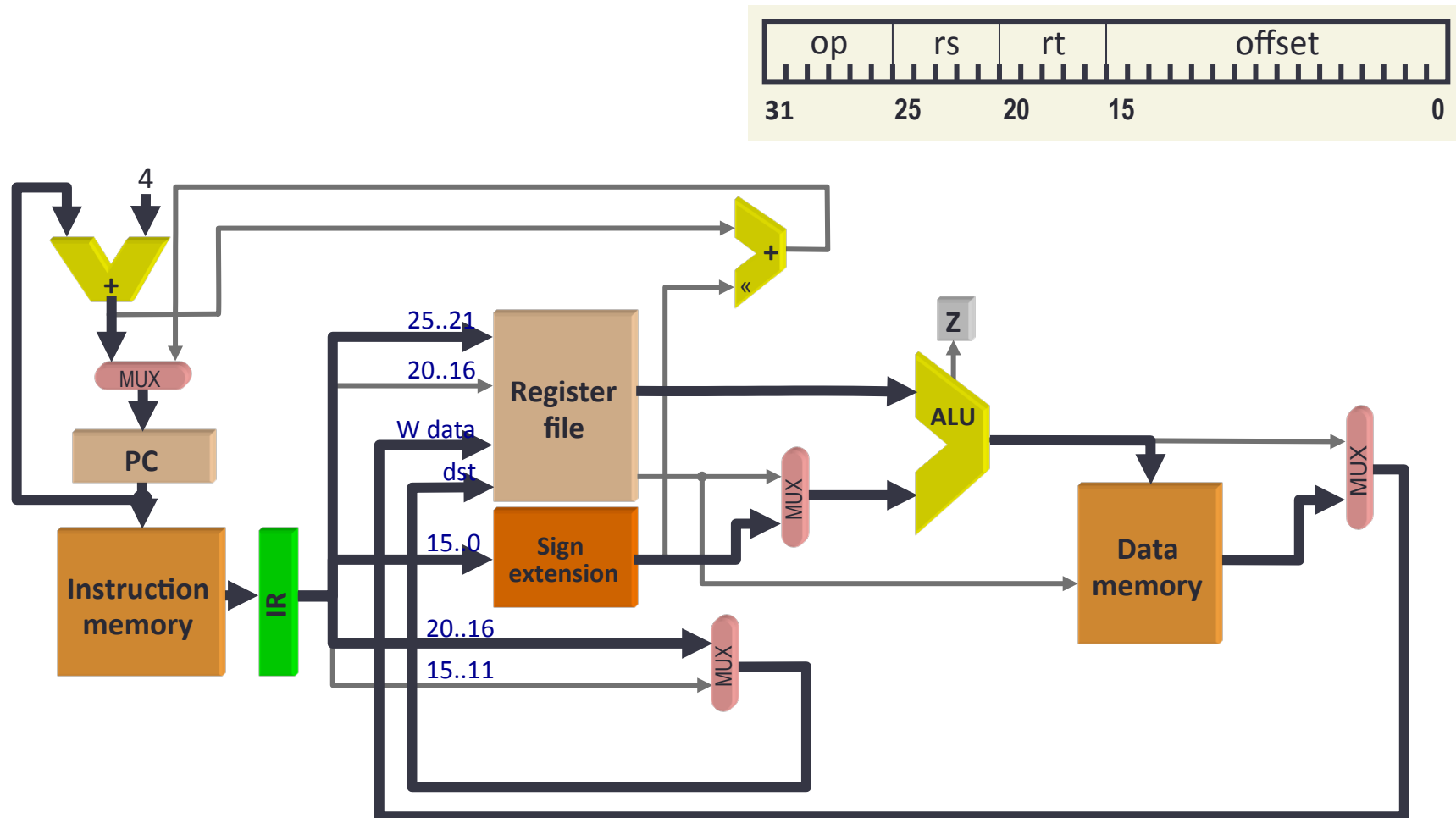

# Store word

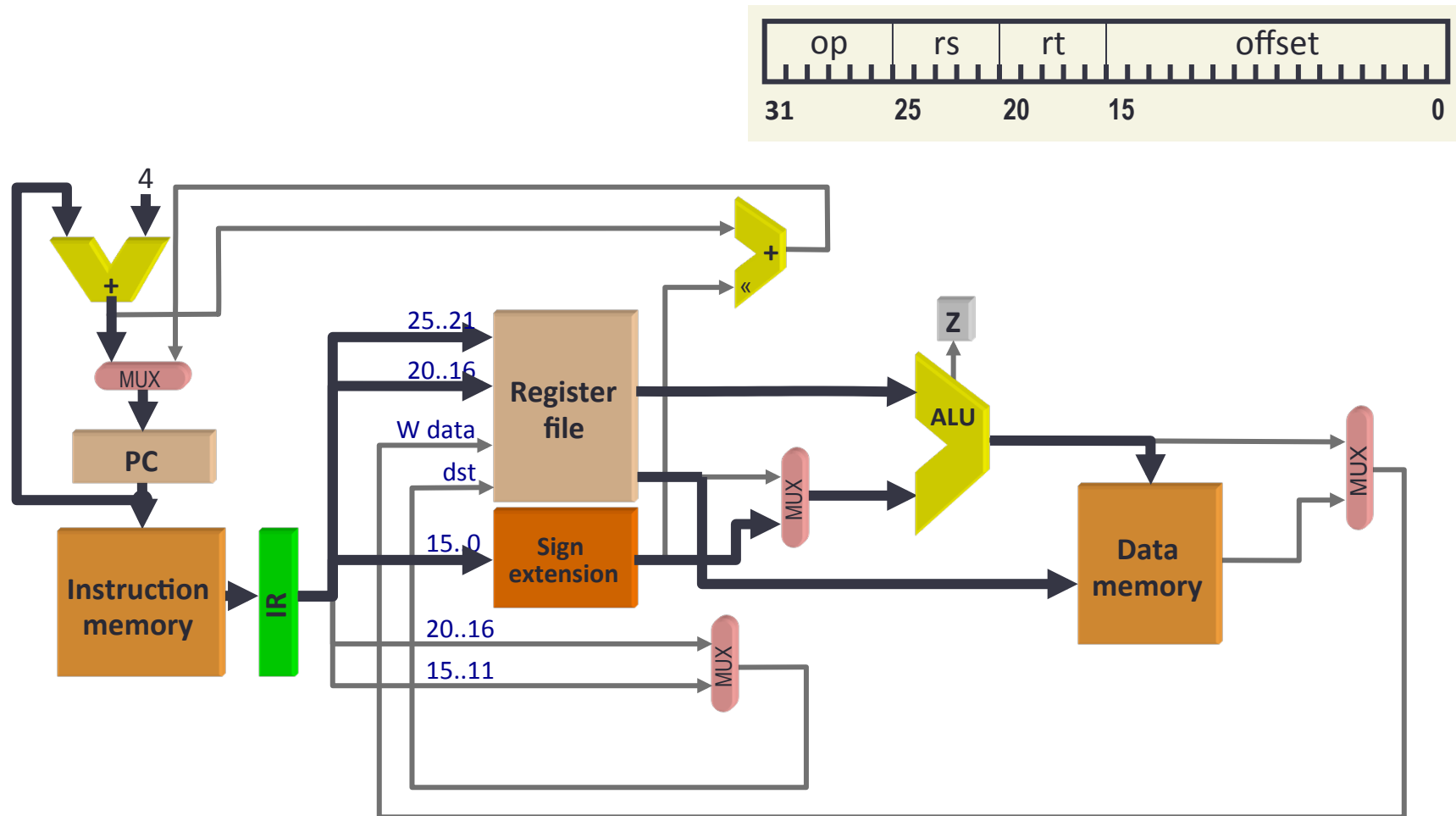

# Conditional branch (beq)

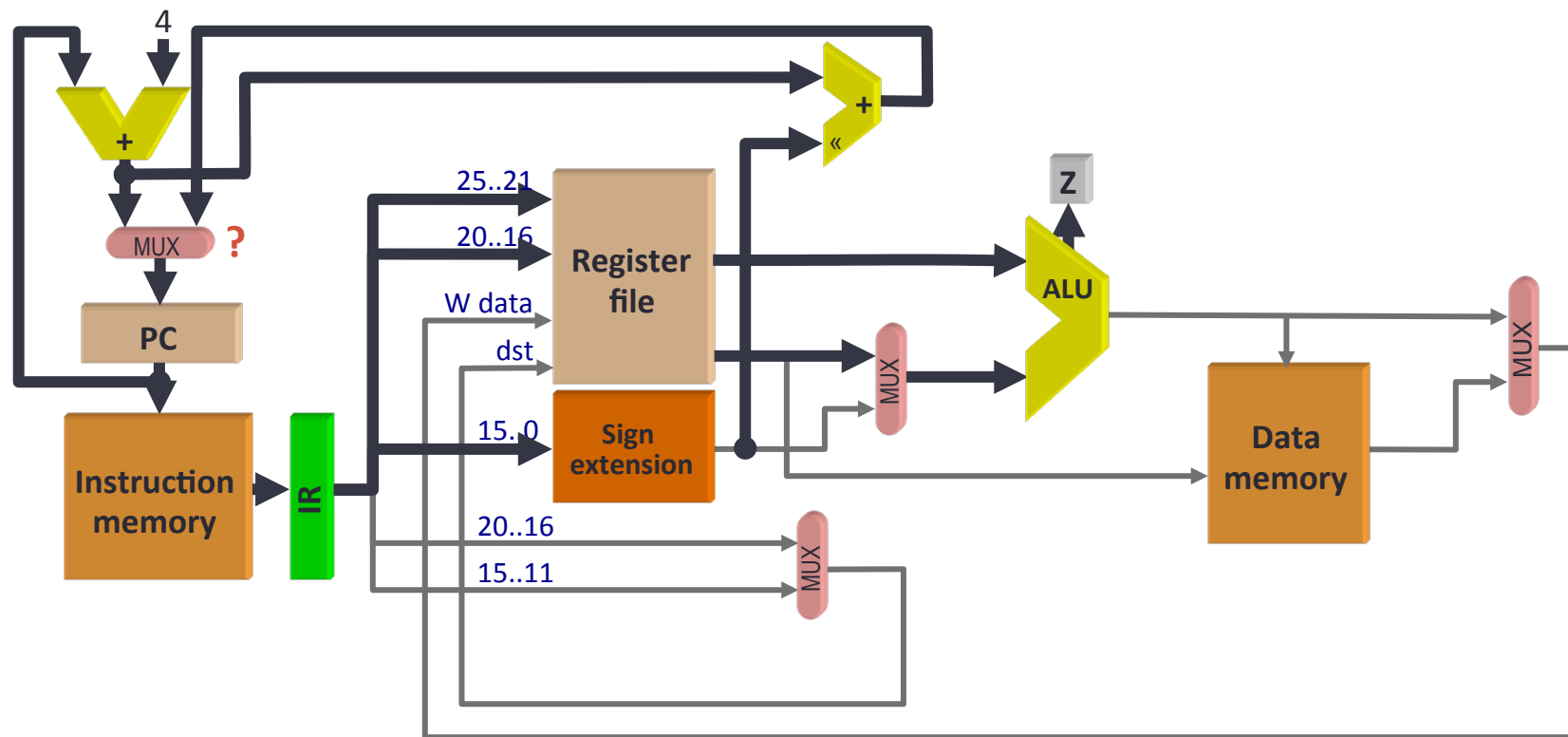 

# 3 Control Unit

- Hardwired CU
- Evaluation
- Other alternatives

# Hardwired CU

- The Control Unit (CU) must assert the needed signals in the datapath to enable proper execution of instructions
- The CU needs to **decode** the current instruction to determine which signals to assert
- The CU can be implemented by a combinational circuit (*hardwired* control unit)
  - Inputs:
    - Bits of IR that enable identification of current instruction (*opcode / func*)
    - For beq, the Z flag calculated by the ALU
  - Outputs:
    - All control signals defined so far
      - Mux control (4 signals), register write, memory read & write, ALUOp (3 signals)



# ALU control signals

## ALU specification

ALUOp	Operation
000	$A \wedge B$ (and)
001	$A \vee B$ (or)
010	$A + B$ (arithmetic add)
110	$A - B$ (subtraction)
111	$A < B$ (for slt)

## ALUOp table

		Inputs		Output
Instruction	Format	opcode	func (R)	ALUOp
<b>add</b>	R	000000	100000	0 1 0
<b>sub</b>	R	000000	100010	1 1 0
<b>and</b>	R	000000	100100	0 0 0
<b>or</b>	R	000000	100101	0 0 1
<b>slt</b>	R	000000	101010	1 1 1
<b>lw</b>	I	100011		0 1 0
<b>sw</b>	I	101011		0 1 0
<b>beq</b>	I	000100		1 1 0

Hands on: Complete the ALUOp table by including I-format A/L instructions  
(opcodes available in <http://www.mrc.uidaho.edu/mrc/people/jff/digital/MIPSir.html>)



# All control signals

Instr.	Format	Inputs		Outputs							
		opcode	func (R)	ALUSrc	ALUOp	RegDst	RegWrite	PCMux	MemRead	MemWrite	MemToReg
<b>add</b>	R	000000	100000	0	0 1 0	1	1	0	0	0	0
<b>sub</b>	R	000000	100010	0	1 1 0	1	1	0	0	0	0
<b>and</b>	R	000000	100100	0	0 0 0	1	1	0	0	0	0
<b>or</b>	R	000000	100101	0	0 0 1	1	1	0	0	0	0
<b>slt</b>	R	000000	101010	0	1 1 1	1	1	0	0	0	0
<b>lw</b>	I	100011		1	0 1 0	0	1	0	1	0	1
<b>sw</b>	I	101011		1	0 1 0	X	0	0	0	1	X
<b>beq</b>	I	000100		0	1 1 0	X	0	<b>Z</b>	0	0	X
<b>j</b>	J	000010									
<b>jr</b>	R	000000	001000								

Hands on: Complete this table for j and jr and include also I-format A/L instructions (opcodes available in <http://www.mrc.uidaho.edu/mrc/people/jff/digital/MIPSir.html>)

# Evaluation of the single-cycle design

- The datapath+CU is able to execute one instruction per clock cycle. How to determine the clock period?
- We need to know the delays involved in executing every instruction
- Example: assume that...
  - Reading or writing memory costs 2 ns
  - Reading or writing the register file costs 1 ns
  - ALU operates in 2 ns
  - Rest of delays are negligible
- 1. What elements are needed and what's the overall delay for the execution of each instruction?
- 2. What's the minimum clock period needed?

# Evaluation of the single-cycle design


- Answer (1)
  - A/L instructions
    - $T = 2 \text{ (fetch)} + 1 \text{ (reg read)} + 2 \text{ (ALU)} + 1 \text{ (reg write)} = 6 \text{ ns}$
  - Load instruction
    - $T = 2 \text{ (fetch)} + 1 \text{ (reg read)} + 2 \text{ (ALU)} + 2 \text{ (mem read)} + 1 \text{ (reg write)} = 8 \text{ ns}$
  - Store instruction
    - $T = 2 \text{ (fetch)} + 1 \text{ (reg read)} + 2 \text{ (ALU)} + 2 \text{ (mem write)} = 7 \text{ ns}$
  - Branch
    - $T = 2 \text{ (fetch)} + 1 \text{ (reg read)} + 2 \text{ (ALU)} = 5 \text{ ns}$
- Answer (2)
  - We need to select the largest delay as the clock period
    - $T_{\text{clk}} = 8 \text{ ns}$                        $f_{\text{clk}} = 1/8\text{ns} = 125 \text{ MHz}$

# Evaluation of the single-cycle design

- Although simple and intuitive, this design is inefficient
  - The slowest instruction imposes the clock period
  - No room for improvements in the average case (always assume worst case)
- Single-cycle design has been surpassed by
  - Multi-cycle design (next slide)
  - Pipelining (next unit)

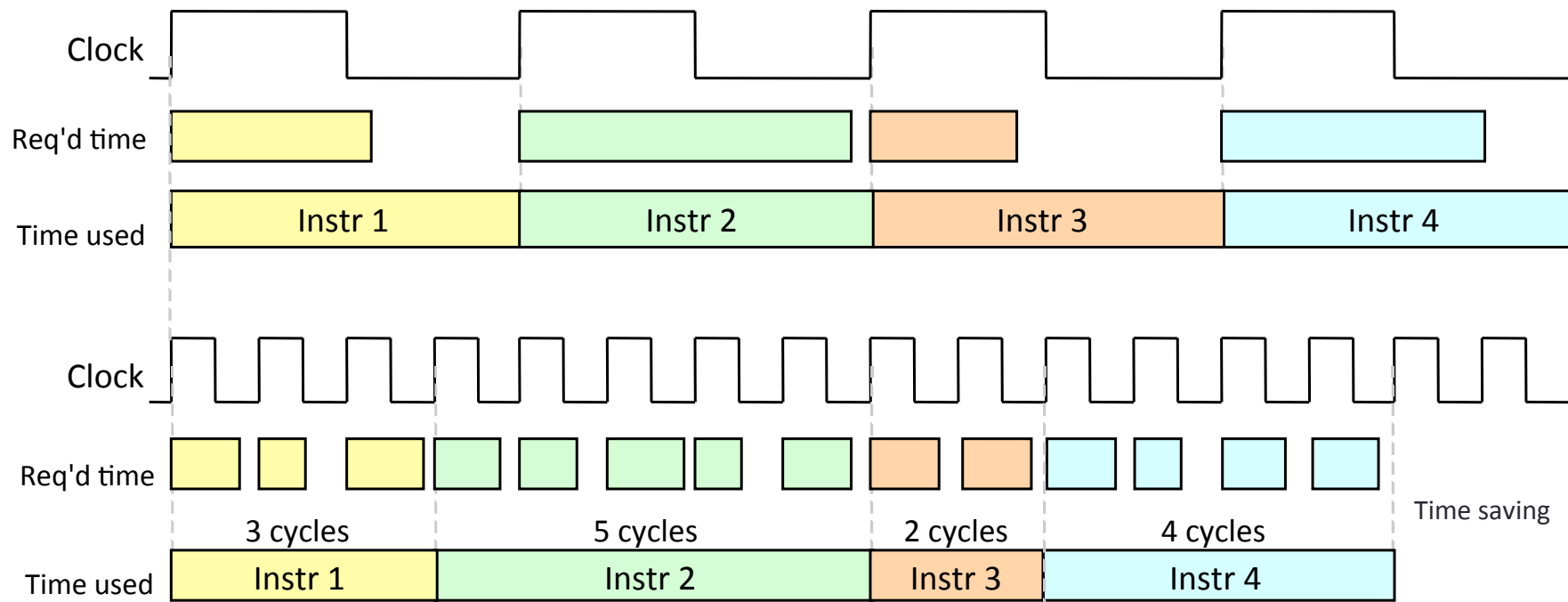
# Multi-cycle design

- Selecting the maximum period becomes a worse alternative with more complex instruction sets, exhibiting higher variability in the execution time of instructions
- The multi-cycle design accommodates this variability by giving each instruction the required number of cycles only


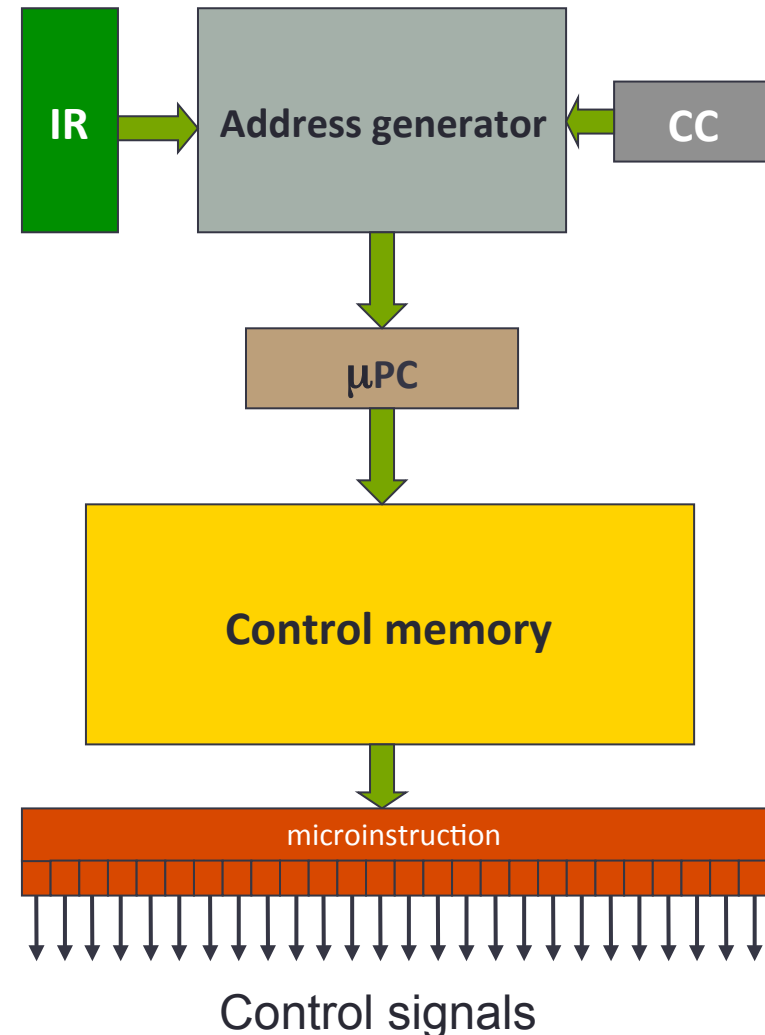
# Microprogrammed CU

- $\mu$ P CUs are an alternative when hardwired CUs become too complex, eg. multicycle
- A small, fast **control memory** contains all control signals for each instruction, for each cycle
  - Words encoding control signals are called **microinstructions**
- It's not faster than hardwired control, only more flexible
- Often used in the CISC days...



# Appendix

## • Transfer instructions and pseudoinstructions

- move, clear, mfhi, mflo, la, li, lui, li.s, li.d, mfc0, mtc0, mfc1, mtc1

```
.data 0x10000000
a: .byte 0
.text 0x00400000
```

```
move $t1, $t0      # $t1 = $t0
clear $t0          # $t0 = 0

li $t0, 23         # $t0 = 23
li.s $f0, 2.45e34  # $f0 = 2.45e34
li.d $f2, -2.33e11 # $f0|$f1 = -2.33e11

lui $t0, 0xAABB    # $t0 = 0xAABB0000

li $t0, 2          # $t0 = 2
li $t1, 4          # $t1 = 4
mult $t0, $t1      # hi|lo = 8 (2×4)
mflo $t0           # $t0 = 8 (low part of result)
mfhi $t1           # $t1 = 0 (high part of result)
```

```
li $t0, 45         # $t0 = 45
la $t0, a          # $t0 = 0x10000000 (addr of a)

li $t0, 0x33440000 # $t0 = 0x33440000

li.s $f0, 1.0      # $f0 = 1.0 (0x3F800000)
mfc1 $t0, $f0      # $t0 = 0x3F800000 (≠ 1)

li $t0, 1          # $t0 = 1
mtc1 $t0, $f0      # $f0 = 0x00000001 (≠ 1.0)

mfc0 $t0, $12      # $t0 = Status reg of coproc. 0

li $t0, 0          # $t0 = 0
mtc0 $t0, $12      # Status ← 0
```