

Unit 4: CMOS technology foundations

Objectives

At the end of this Unit, the student should:

- Know and understand the design of CMOS integrated circuits
 - Complementary CMOS logic
 - Logic design based on transmission gates
- Know a wide range of CMOS logic circuits
 - Combinational, sequential, RAM memory cells
- Know how to characterize electrically the CMOS integrated circuits
 - Parameters of voltage, current, delay and power consumption
 - Special outputs: open drain, tri-state.
- Know the main CMOS subfamilies
 - Buffered outputs, high speed, low voltage, etc.
- Understand the foundations of design and manufacture of VLSI chips

Contents

4.1 Introduction

4.1.1 Main features. Historical evolution. Moore's Law

4.2 Combinational Circuits

4.2.1 The inverter

4.2.2 Other basic gates

4.2.3 Design of general functions in CMOS Complementary Logic

4.2.4 Design with transmission gates. Multiplexers

4.3 Flip-flops: level and edge triggered

4.4 Special outputs

4.4.1 Open drain

4.4.2 Tri-state

4.5 Electrical characteristic parameters

4.6 CMOS Subfamilies

4.7 Compatibility between families

4.7.1 Level Converters

4.8 VLSI Design Basics

4.8.1 Fabrication Process. Masks.

4.8.2 Cells layout .

4.8.3 Design flow based on standard cells

4.8.4. Current and future trends

Bibliography

- Theory

- “Digital design”. Wakerly. Ed. Prentice-Hall. 2006. Chapter 3.
- “Electronics”. Hambley. Ed. Prentice-Hall. 2002. Chapter 6.
- “CMOS circuits”. R.M. Marston. Ed. Paraninfo. 1995.
- “Digital integrated circuits”. Jan Rabaey et al. Ed. Prentice-Hall. 2004.
- www.intel.com/technology
- “International Technology Roadmap for Semiconductors – ITRS09”

- Problems

- G.Benet; J.V.Benlloch; J.V.Busquets; D.Gil; P.Perez, *Ejercicios Resueltos de Tecnologia de Computadores, Cap.5*, SPUPV 2006.916


4.1. Introduction

- CMOS is the logic family with more looking forward to future.
- Application scope :
 - Most LSI and VLSI I.C.: Memories and Processors
 - SSI and MSI, together with TTL
- Relevant features
 - Low power consumption
 - Simple manufacturing process
 - Excellent noise immunity
 - Variable supply voltage
 - High Speed subfamilies.


*VLSI: Very Large Scale
of Integration*

 4.1. Introduction. Historical evolution

- In 1970's the manufacturing processes for processors and memories was typically based on NMOS transistors
 - Cheap, but have static consumption *(When Low level)*




Intel 1101 256-bit SRAM

 


Intel 4004 4-bit μ Proc

4.1. Introduction. Historical evolution


- From 1980's to present: CMOS technology: Low static power

 

Intel 286

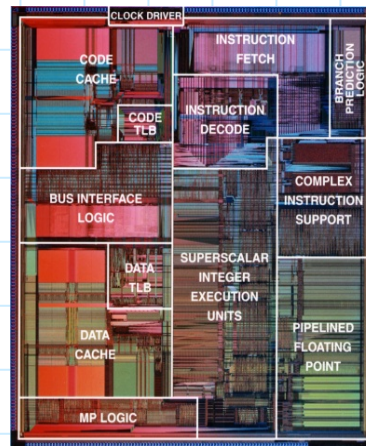

Intel Pentium

 


Intel-i7

*From 16 bits of data bus: Non-FUNCTIONAL parts
(e.g. fault detection)*

 4.1. Introduction. Moore's law

- 1965: Gordon Moore predicted the evolution of the number of transistors per chip
 - It fits a straight line in a semi-logarithmic scale
 - The number of transistors doubles every 18-24 months

Microprocessor Transistor Counts 1971-2011 & Moore's Law



Integration Levels

SSI: 10 gates


MSI:	1000 gates
-------------	------------

LSI: 10,000 gates

VLSI: > 10k gates

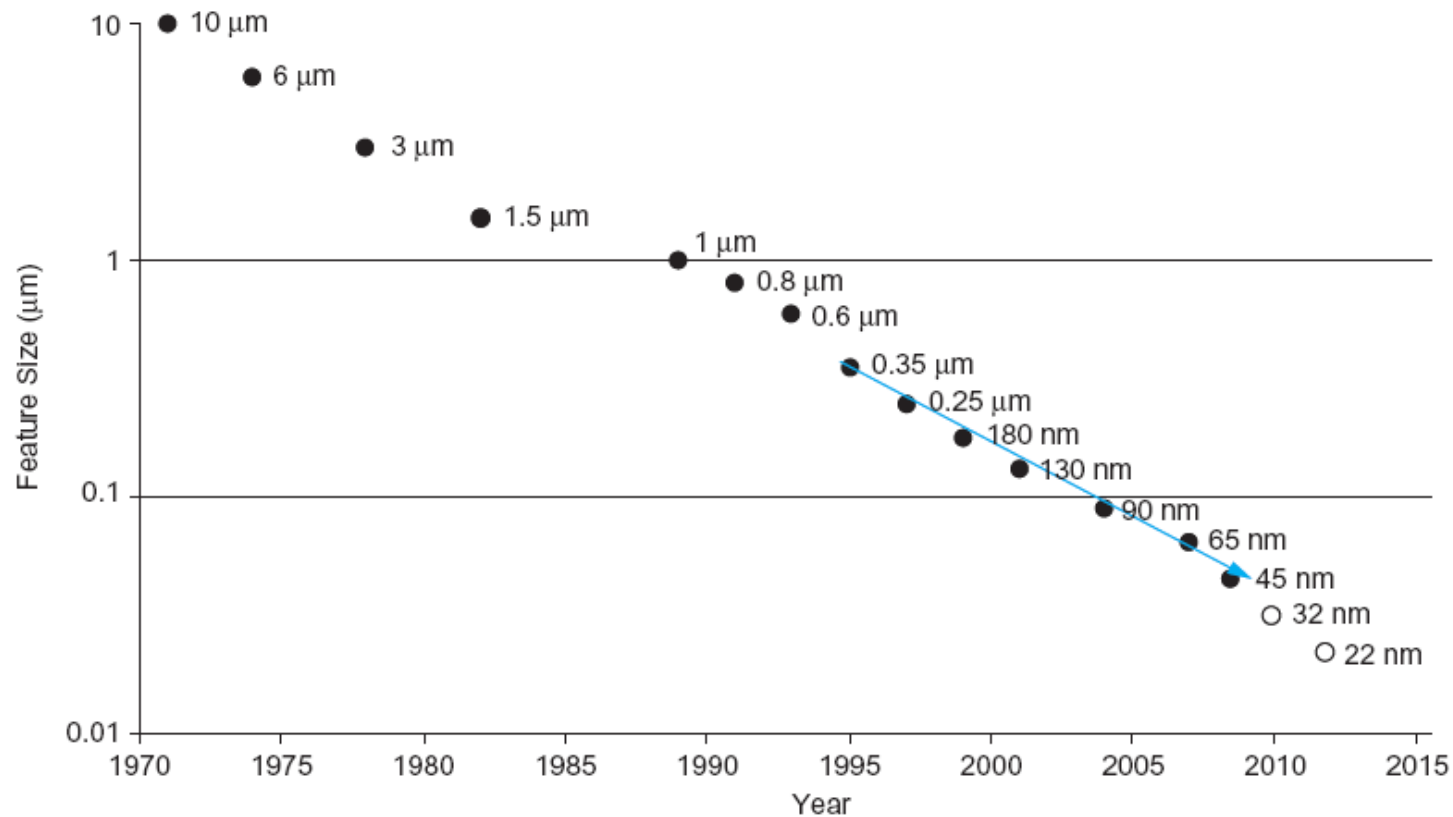
4.1. Introduction. Moore's law

- *Feature Size* brings down an 30% every 2-3 years



 4.1. Introducción. Ley de Moore


- Many other factors grow exponentially
 - Ex: clock frequency, processor performance




*Limit → 2010
(Power dissipation)*

 4.1 Introduction. Power

- The power consumed by chips has also grown exponentially, because:
 - Intensive integration, High frequency
- Power consumption is a key factor, as soon as:
 - Limits the integration density: Heat dissipation
 - It is specially important in systems powered with batteries









4.1 Introduction. Power density

 


Courtesy, Intel

      4.2. Combinational circuits

- MOS transistors as **ideal switches**: *(SW)*
 - MOS transistors can be seen as voltage-controlled switches (**model**); *$R_{ON} \approx 0$ (Closed SW); $R_{OFF} \approx \infty$ (open SW)*
 - The gate voltage controls the connection between drain and source terminals




4.2.1 The CMOS inverter (review)

 

Digital input: $V_I = 0V = \text{"0"}$ $V_I = V_{DD} = \text{"1"}$

4.2.1 The CMOS inverter (review)

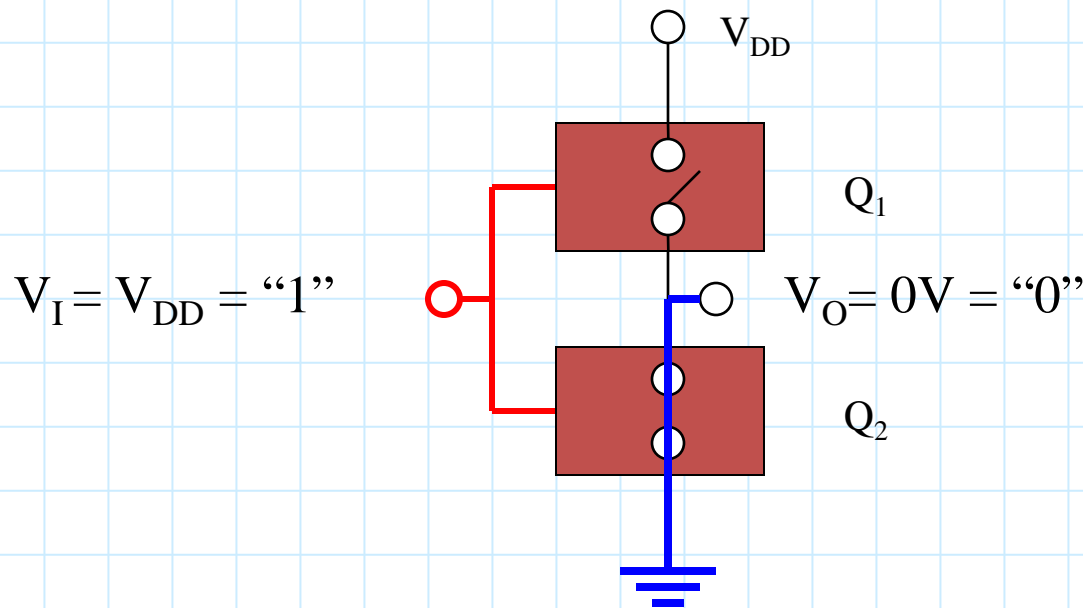


$$V_{GS1} = V_{DD} - V_{DD} = 0V > -V_T \Rightarrow \text{PMOS OFF}$$

$$V_{GS2} = V_{DD} - 0V = V_{DD} > V_T \Rightarrow \text{NMOS ON}$$

Static power consumption = 0 mW

(Except leakage)

4.2.1 The CMOS inverter (review)

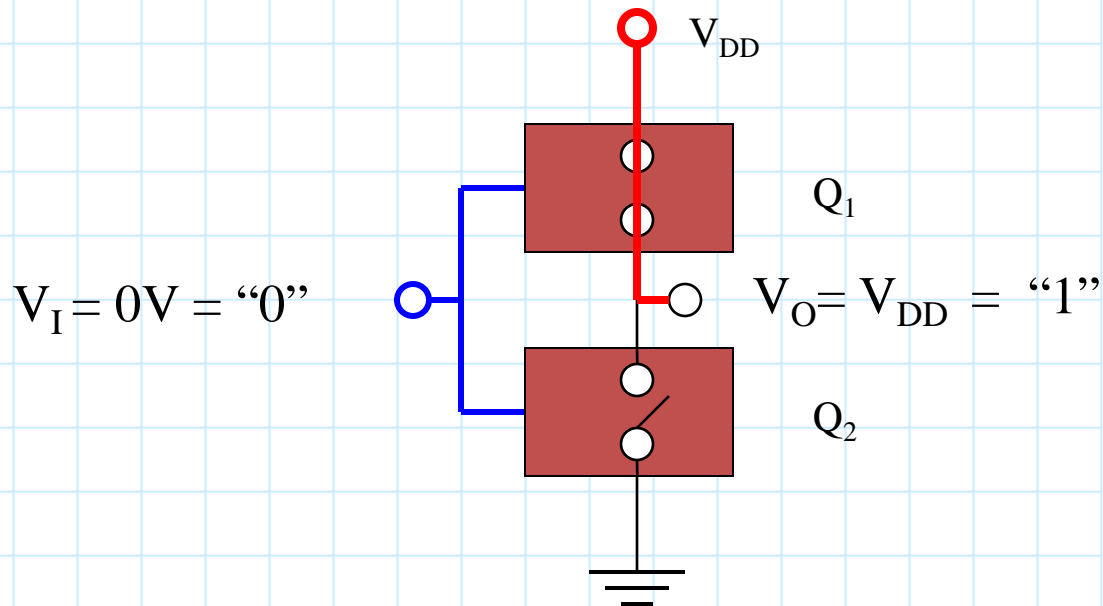


$$V_{GS1} = 0V - V_{DD} = -V_{DD} < -V_T \Rightarrow \text{PMOS ON}$$

$$V_{GS2} = 0V - 0V = 0V < V_T \Rightarrow \text{NMOS OFF}$$

Static power consumption = 0 mW
(Except leakage)

4.2.1 The CMOS inverter (review)

- An easier symbol for MOS transistors

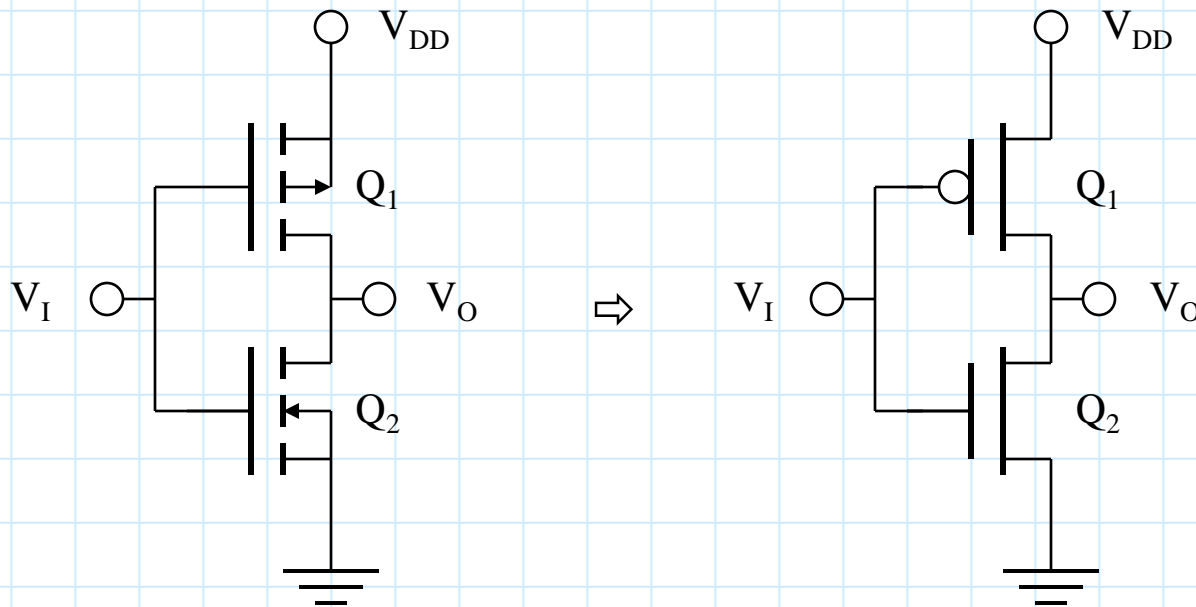


Substrates $\left\{ \begin{array}{l} p\text{-channel: Connected to } V_{DD} \\ n\text{-channel: Connected to GND.} \end{array} \right.$

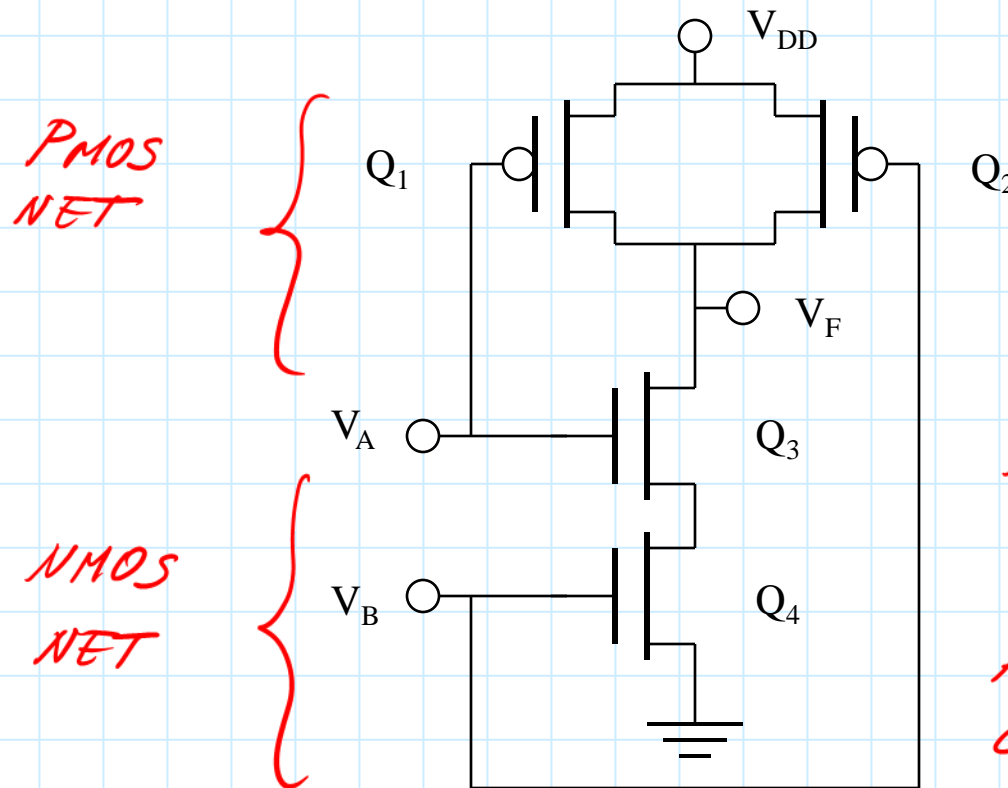4.2.2 Other logic gates.

NAND CMOS

- Structure: PMOS transistors in parallel and NMOS in series




NMOS: V_F will be "0" if both V_A AND V_B are "1": $\overline{F} = A \cdot B$
 $F = \overline{A \cdot B}$

PMOS: V_F will be "1" if V_A OR V_B are "0"
 $F = \overline{A + B} \Rightarrow F = \overline{A \cdot B}$

AND: SERIES transistors
OR: PARALLEL "

NMOS and PMOS nets are DUAL
NMOS series \longleftrightarrow PMOS parallel


4.2.2 Other logic gates. NAND CMOS

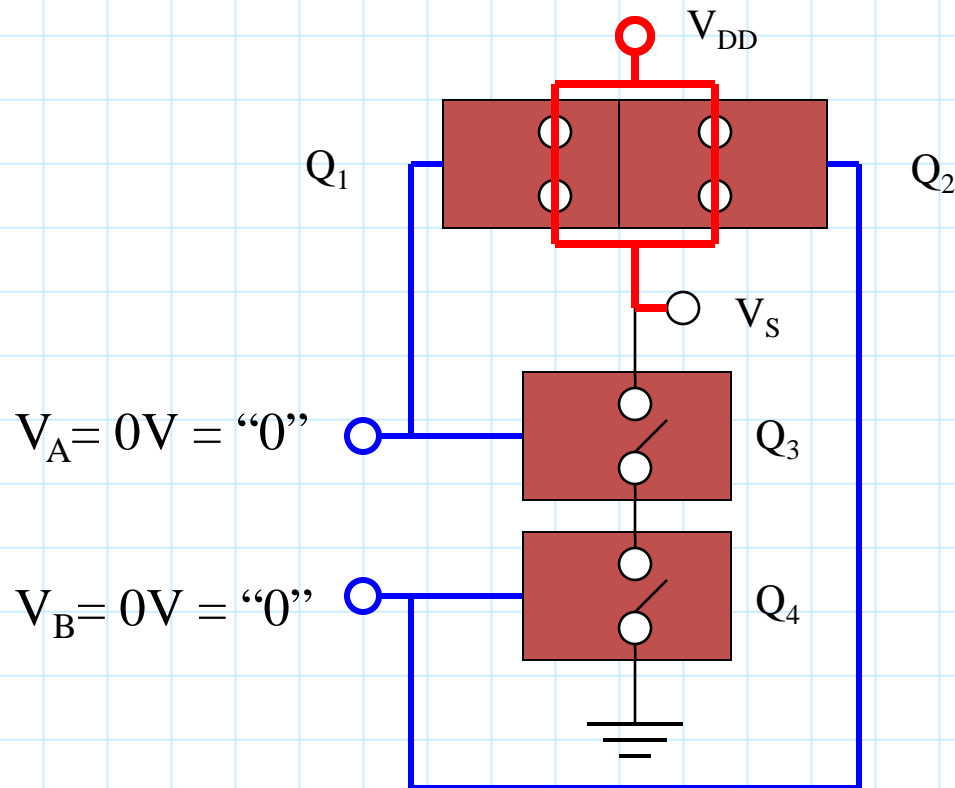

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	V_{DD}
V_{DD}	0V	V_{DD}
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW


4.2.2 Other logic gates. NAND CMOS

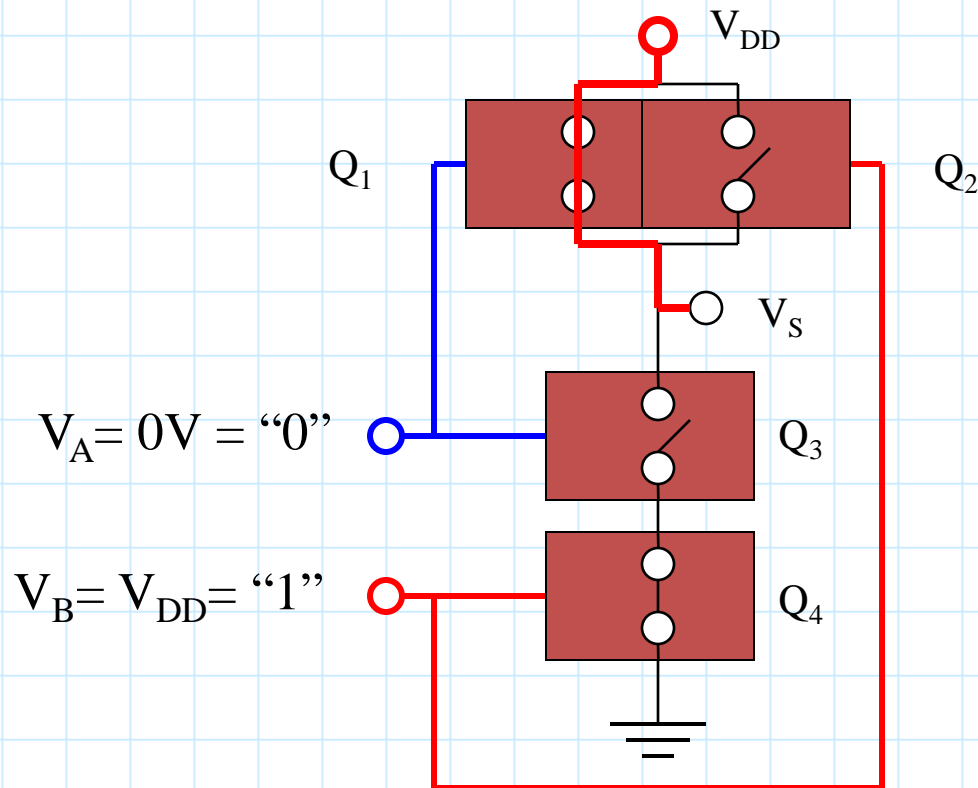

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	V_{DD}
V_{DD}	0V	V_{DD}
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW


4.2.2 Other logic gates. NAND CMOS

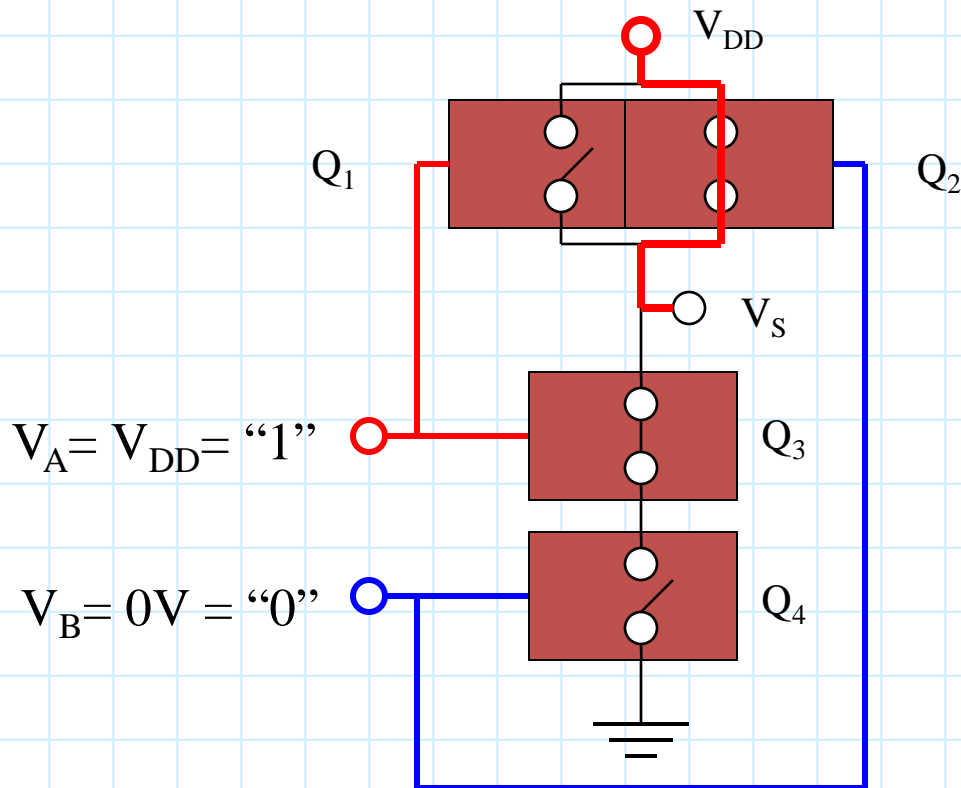

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	V_{DD}
V_{DD}	0V	V_{DD}
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW

5.2.2 Other logic gates. NAND CMOS

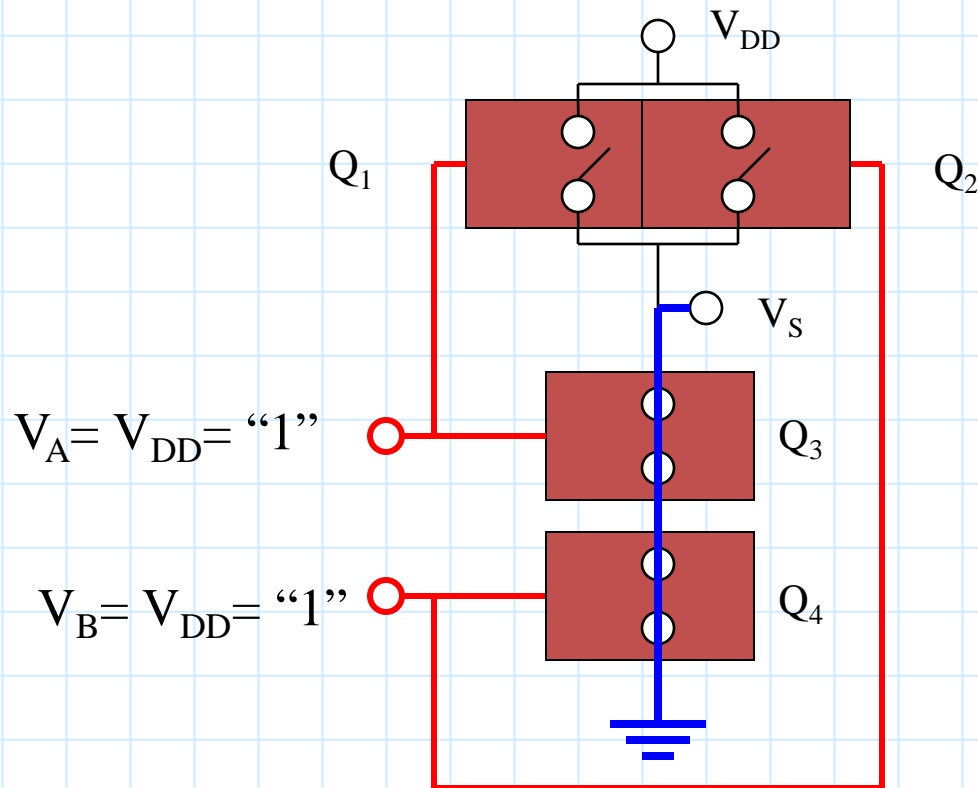


V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	V_{DD}
V_{DD}	0V	V_{DD}
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW

 4.2.2 Other logic gates. NOR CMOS

- Structure: NMOS transistors in parallel and PMOS in series




NMOS: V_F will be "0"
if V_A **OR** V_B
are "1": $\overline{F} = A + B$
 $F = \overline{A + B}$

PMOS: V_F will be "1"
if both V_A **AND** V_B are "0"
 $F = \overline{A} \cdot \overline{B} \Rightarrow F = \overline{A + B}$

AND: SERIES transistors
OR: PARALLEL "

NMOS and PMOS nets are DUAL
NMOS series \longleftrightarrow PMOS parallel


4.2.2 Other logic gates. NOR CMOS

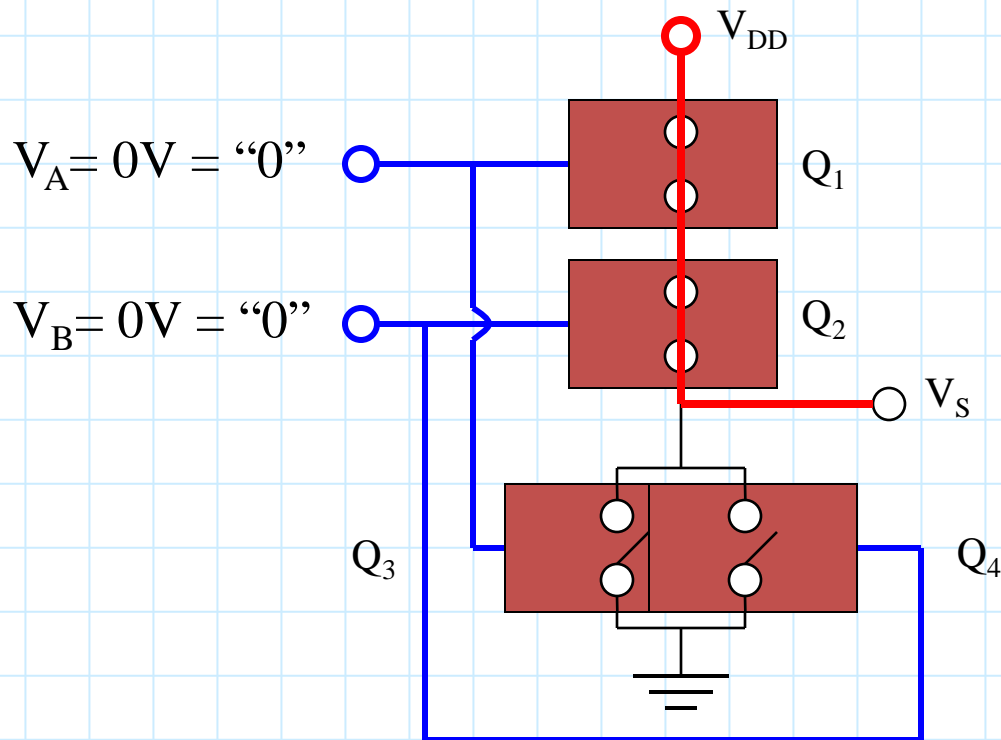

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	0V
V_{DD}	0V	0V
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW


4.2.2 Other logic gates. NOR CMOS

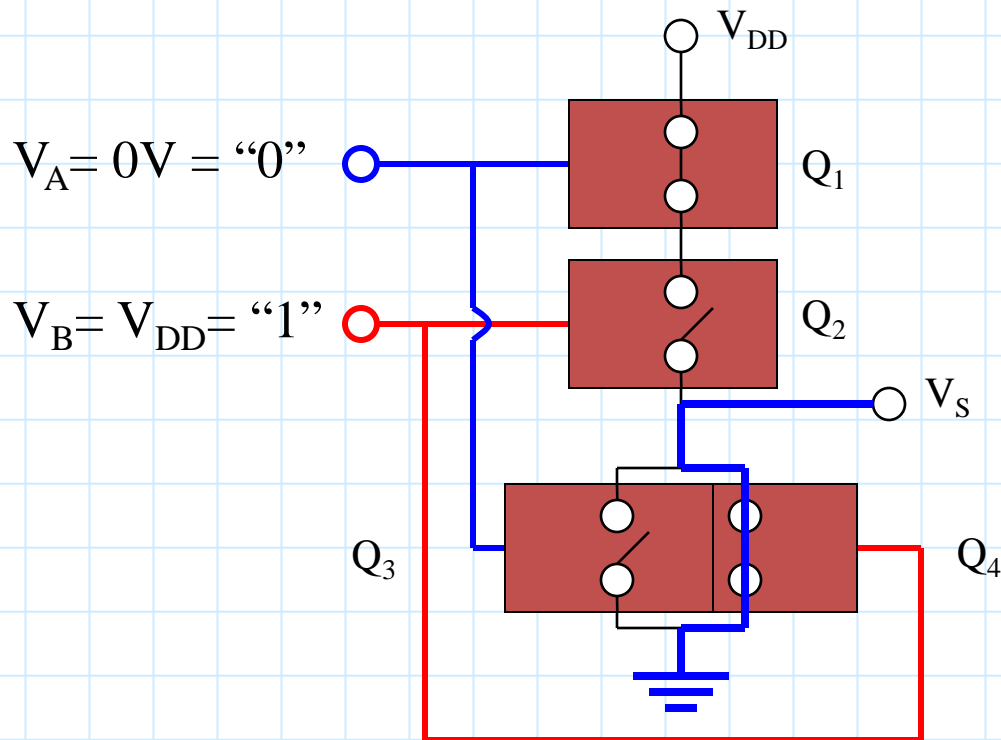

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	0V
V_{DD}	0V	0V
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW


4.2.2 Other logic gates. NOR CMOS

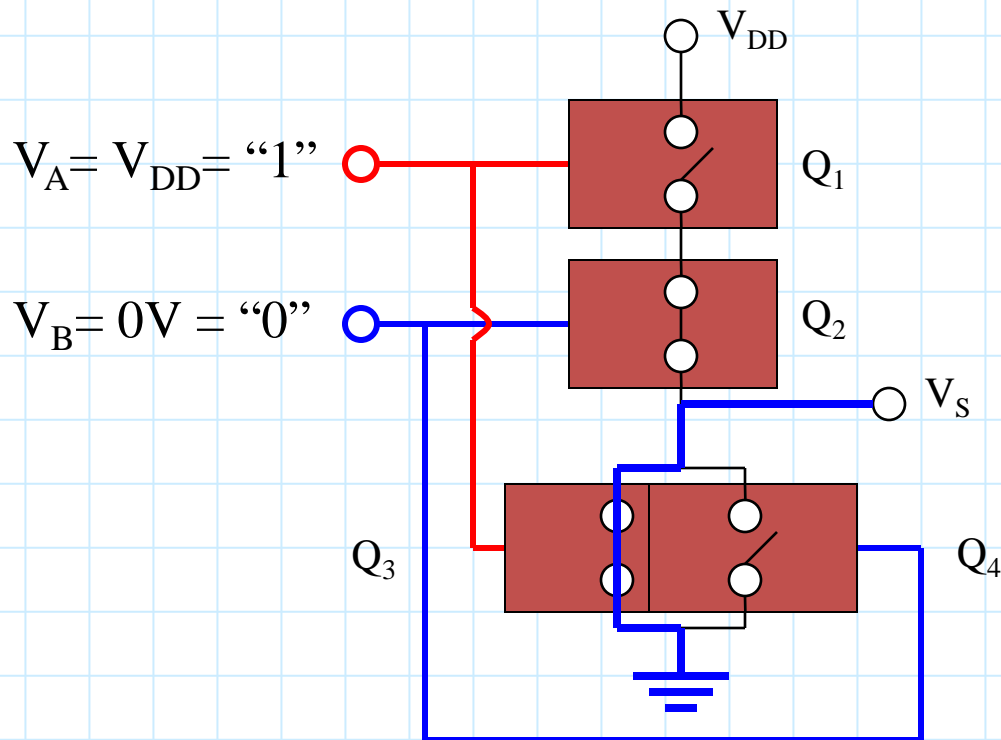

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	0V
V_{DD}	0V	0V
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW

4.2.2 Other logic gates. NOR CMOS

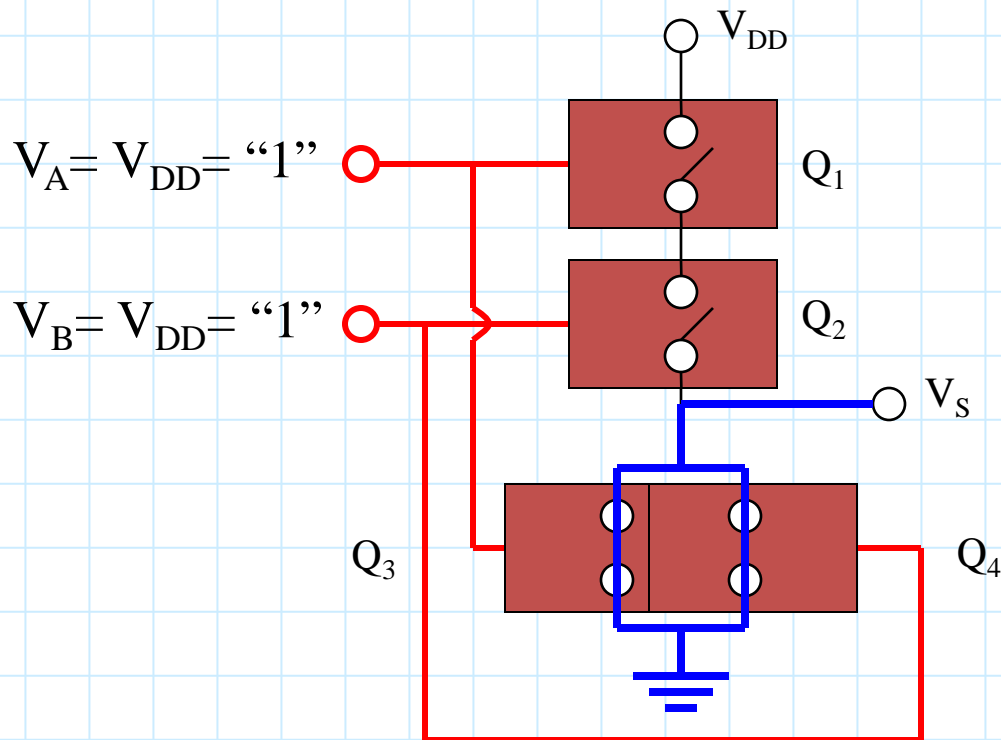

V_A	V_B	V_S
0V	0V	V_{DD}
0V	V_{DD}	0V
V_{DD}	0V	0V
V_{DD}	V_{DD}	0V

Static power consumption = 0 mW

4.2.2 Other basic gates

- Buffer = NOT + NOT → *Second NOT gives/sinks more current than usual*
- AND = NAND + NOT
- OR = NOR + NOT

