

CH1. BASIC SEMICONDUCTOR DEVICES


5. Given the following two-level clipping circuit, indicate the range of values that can be obtained at the output V_o . ($V_\gamma = 0.7V$ for both diodes).

[A] $0.7V \leq V_o \leq 5.7V$


[B] $-0.7V \leq V_o \leq 5.7V$

[C] $-0.7V \leq V_o \leq 4.3V$

[D] $0.7V \leq V_o \leq 4.3V$

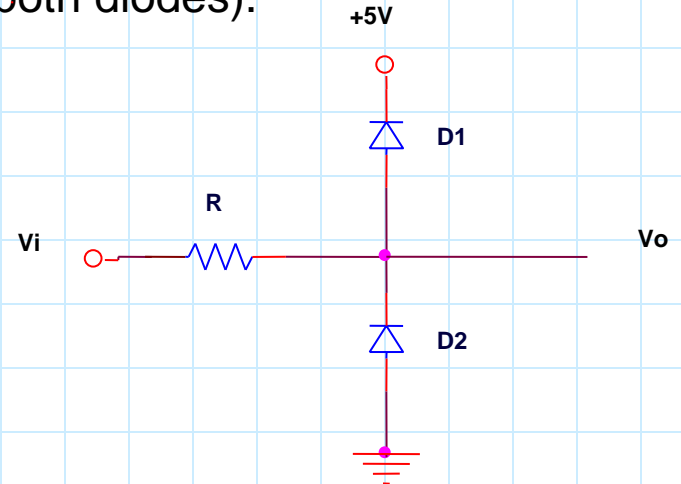


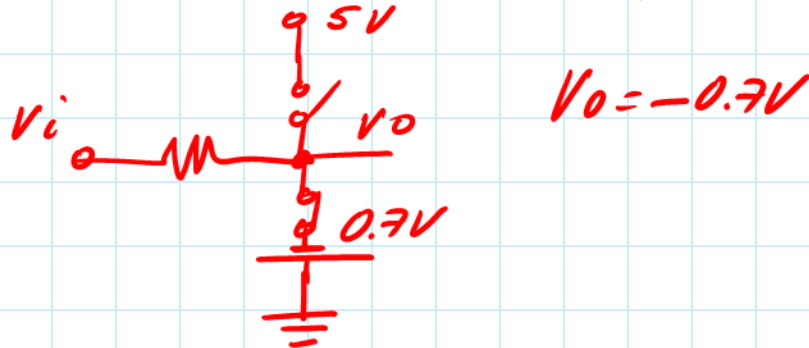$V_i < -0.7V \Rightarrow D_2 \text{ ON } D_1 \text{ OFF}$



$-0.7V \leq V_i \leq 5.7V \Rightarrow D_2 \text{ OFF } D_1 \text{ OFF}$
 $V_o = V_i$


$V_i > 5 + 0.7V \Rightarrow D_1 \text{ ON } D_2 \text{ OFF}$

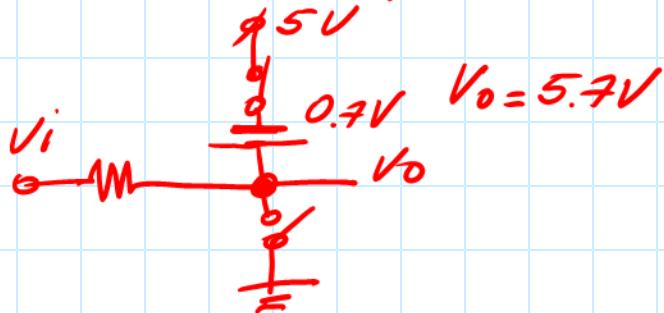


CH1. BASIC SEMICONDUCTOR DEVICES

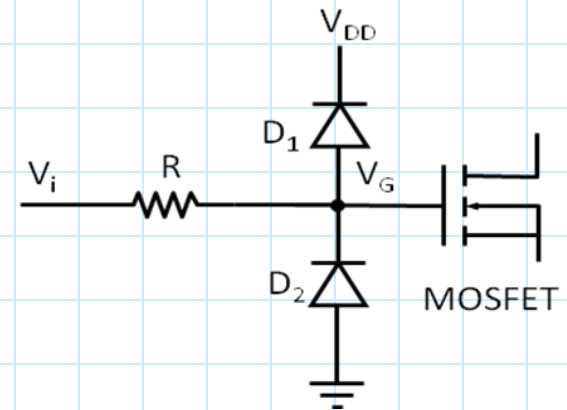6. Given the following input-protection circuit for MOSFETs, calculate the voltages at all points and currents at all branches, and the status of both diodes, when the input is a static voltage of 4000V DC, produced when a person who has stepped on a carpet touches V_i terminal.

DATA: $R = 200\Omega$; $V_{DD} = 5V$; Diodes: $V_\gamma = 0.7V$


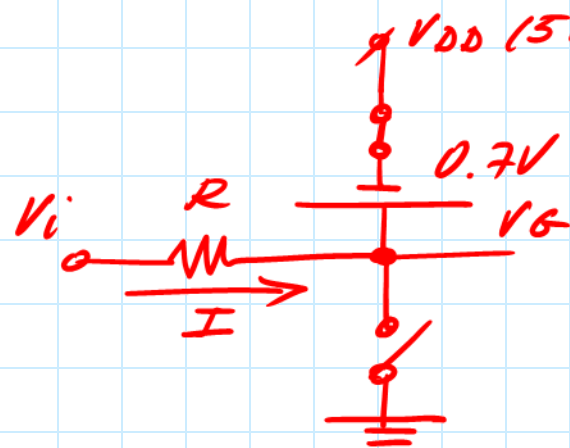
$$V_i > V_{DD} + 0.7 \Rightarrow D_1 \text{ ON} ; D_2 \text{ OFF}$$



$$V_G = V_{DD} + 0.7V = 5.7V$$
$$I = \frac{V_i - V_G}{R} = \frac{4000 - 5.7}{200} = \underline{\underline{19.97A}}$$

CH1. BASIC SEMICONDUCTOR DEVICES


7. Given the circuit with diodes of figure and assuming $A = "0"$ (0V) and $B = "1"$ (5V) point out the CORRECT answer of the following, considering $V_f = 0.7V$ for both diodes:

[A] $V_{AK} = -4.3V$ for the diode of input B. ✓

[B] This circuit implements a two-input OR logic gate. ✗


[C] The voltage at S output is 4.3V. ✗

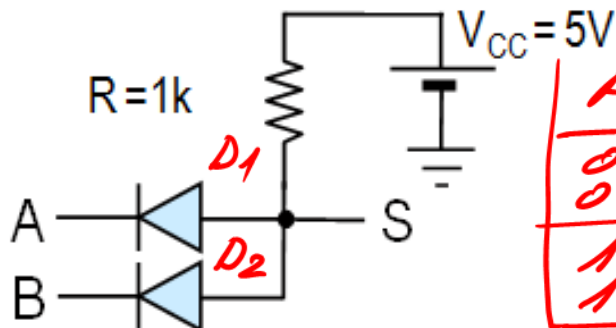[D] The current flowing through the resistor is divided equally in each diode. ✗




$$S = A \cdot B$$

AB	$D_1 D_2$	V_S	S
00	ON ON	0.7	0
01	ON OFF	0.7	0
10	OFF ON	0.7	0
11	OFF OFF	5	1

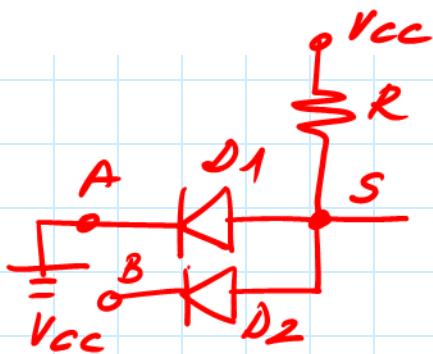


$D_1 ON$
 $D_2 OFF$

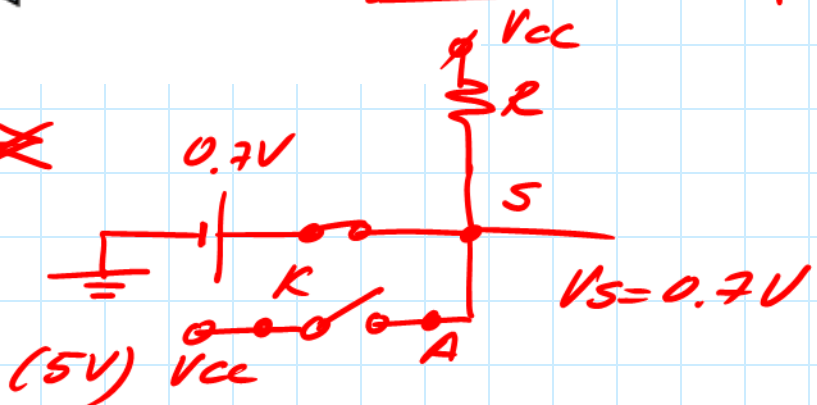

$$V_{AK D_2} = V_A - V_K = 0.7 - 5 = -4.3V$$


CH1. BASIC SEMICONDUCTOR DEVICES

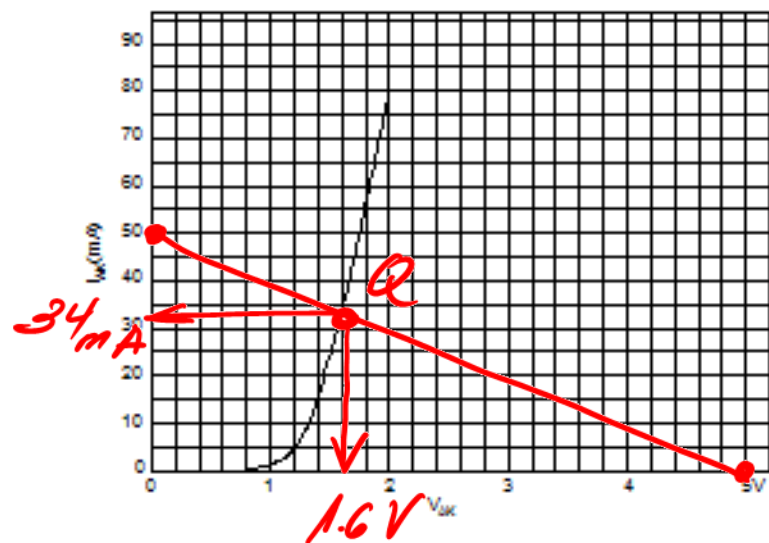13. Indicate the operating point of LED of the following circuit whose characteristic curve can be seen on the right. NOTE: We recommend using the load line.



Load line equation:
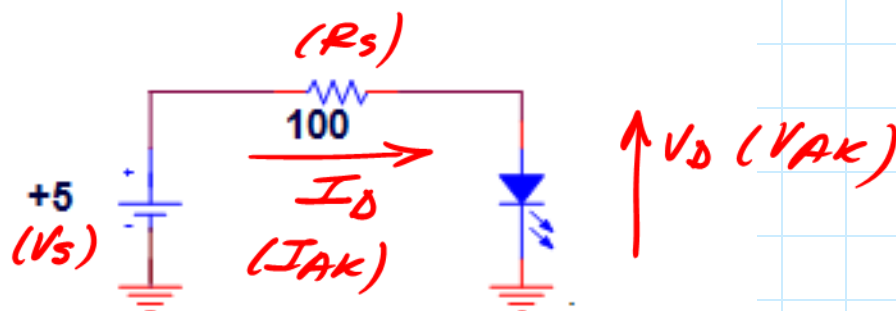
$$I_D = \frac{V_S}{R_S} - \frac{V_D}{R_S}$$



- [A] The operating point can not be calculated because of missing data.
[B] 1.4V, 15mA
[C] 1.6V, 35mA
[D] 1.8V, 55mA

Crossing points:

x axis: $I_D = 0 \Rightarrow V_{AK} = V_S = 5V$

y axis: $V_D = 0 \Rightarrow I_D = \frac{V_S}{R_S} = \frac{5}{0.1} = 50mA$

$Q (1.6V, 34mA)$