

CH1. BASIC SEMICONDUCTOR DEVICES


15. Given the following circuit with LEDs, signal the CORRECT answer between the following, taking into account the following parameters: For LEDs, $V_{LED}=1.5V$ and $I_{LED}=10mA$, and for NAND gate, $V_{OL}=0.15V$ y $V_{OH}=4.5V$ ($V_{CC}=5V$).

[A] The LEDs will shine properly with a resistor higher than 150Ω . *✗ Perhaps don't shine*

[B] The LEDs will shine properly with a resistor lesser or equal than 150Ω . *✗ We can destroy LEDs*

☒ [C] The LEDs will shine properly with a resistor of 150Ω . *✓*

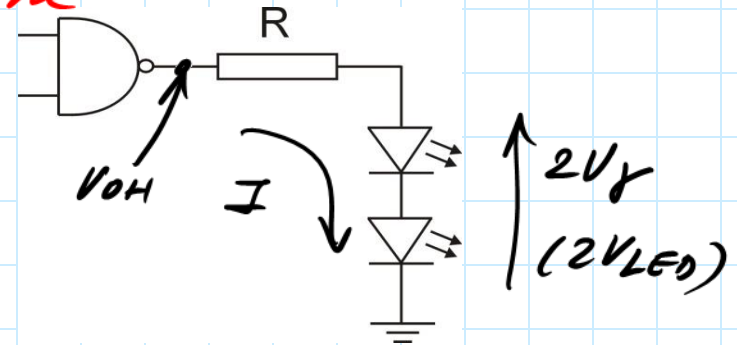[D] The LEDs will not shine for any of the logic level outputs of the NAND gate. *✗*




$$I_{LED} = \frac{V_{OH} - 2V_{LED}}{R} \Rightarrow R = \frac{V_{OH} - 2V_{LED}}{I_{LED}}$$

$$\underline{R} = \frac{4.5 - 3}{10m} = 0.15K = \underline{150\Omega}$$

CH1. BASIC SEMICONDUCTOR DEVICES

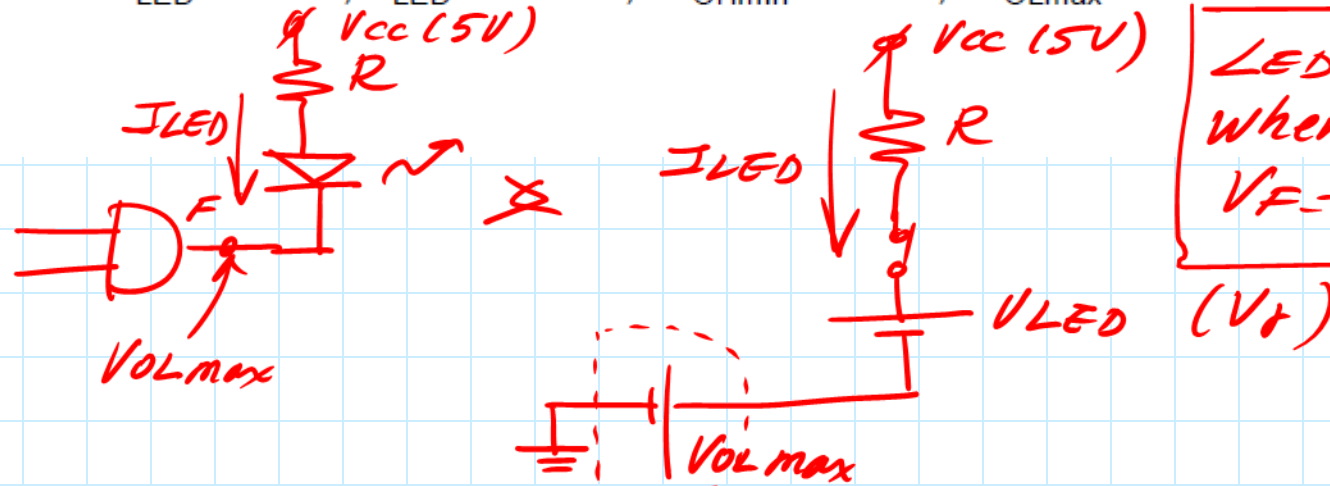16. We have a TTL circuit (for example, an AND gate) that performs a generic function F . We want to light a LED when $F = "0"$. Design a circuit for this purpose..

DATA: $V_{LED} = 1.5V$; $I_{LED} = 10mA$; $V_{OHmin} = 2.4V$; $V_{OLmax} = 0.5V$




$$R = \frac{V_{cc} - V_{LED} - V_{OLmax}}{I_{LED}} = \frac{5 - 1.5 - 0.5}{10mA} = 0.3K = \underline{\underline{300\Omega}}$$


CH1. BASIC SEMICONDUCTOR DEVICES

10. Given the following clipping circuit, and for $V_f = 0.7V$ for all diodes, calculate V_s when $V_e = 6V$.


- [A] 7.3V
- [B] 3V
- [C] 3.7V
- [D] 6V

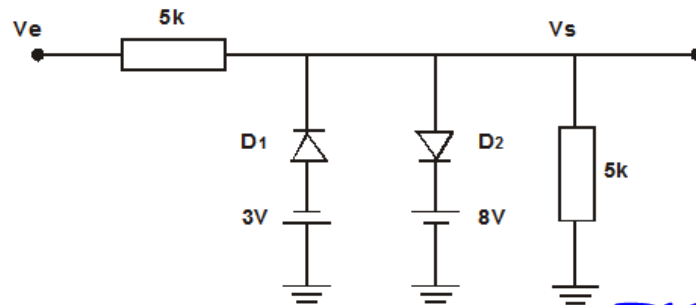

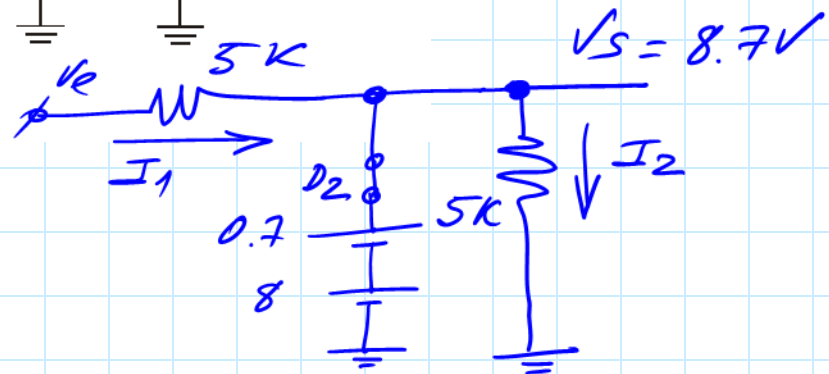a) $V_s > 8 + 0.7 \Rightarrow D_2 \text{ ON} \Rightarrow D_1 \text{ OFF}$



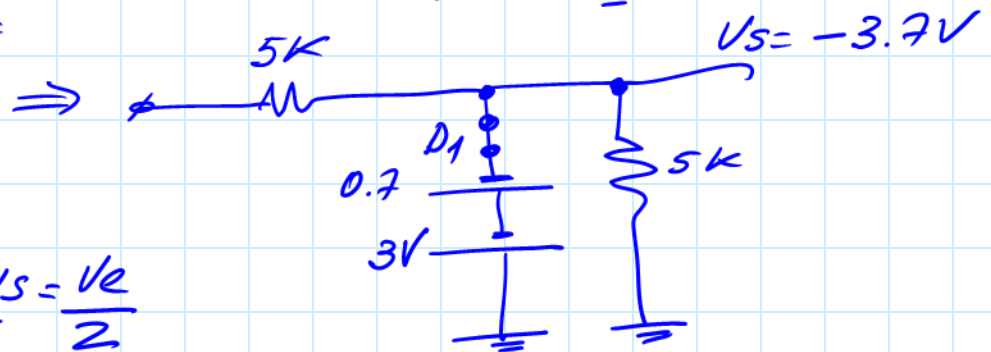b) $V_s < -3 - 0.7 \Rightarrow D_2 \text{ OFF} \Rightarrow D_1 \text{ ON}$



c) $-3.7 \leq V_s \leq 8.7 \Rightarrow D_2 \text{ OFF} \Rightarrow D_1 \text{ OFF}$



Resistor divider \Rightarrow

$-7.4V \leq V_e \leq 17.4V \Rightarrow D_2 \text{ OFF} \Rightarrow D_1 \text{ OFF}$

CH1. BASIC SEMICONDUCTOR DEVICES


10. Given the following clipping circuit, and for $V_\gamma = 0.7V$ for all diodes, calculate V_s when $V_e = 6V$.

[A] 7.3V

[B] 3V

[C] 3.7V

[D] 6V

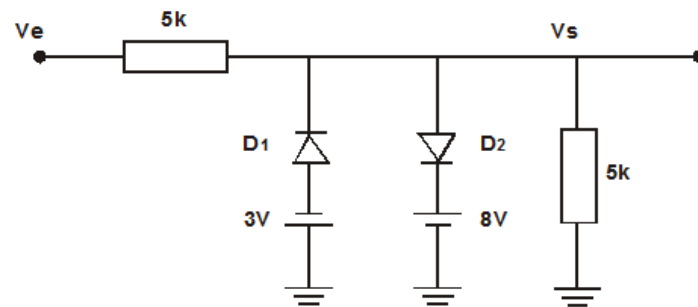

Then :

$$-7.4 \leq V_e \leq 17.4 \rightarrow V_s = V_e / 2 \quad (D_1 \text{ OFF}, D_2 \text{ OFF})$$

$$V_e < -7.4 \rightarrow V_s = -3.7 \quad (D_1 \text{ ON}, D_2 \text{ OFF})$$

$$V_e > 17.4 \rightarrow V_s = 8.7 \quad (D_1 \text{ OFF}, D_2 \text{ ON})$$

Then sol is **B** : $V_e = 6V \rightarrow V_s = \frac{V_e}{2} = 3V$

CH1. BASIC SEMICONDUCTOR DEVICES


8. a) Implement, using logic gates composed only by diodes and resistors, the logic equation $F = AB + CD$.

b) Calculate the output voltage of the designed circuit, for the following input combinations (assume all resistors value as R and ideal diodes):


b1. $A = B = C = D = 0$

b2. $A = B = 1; C = D = 0$

b3. $A = B = C = D = 1$

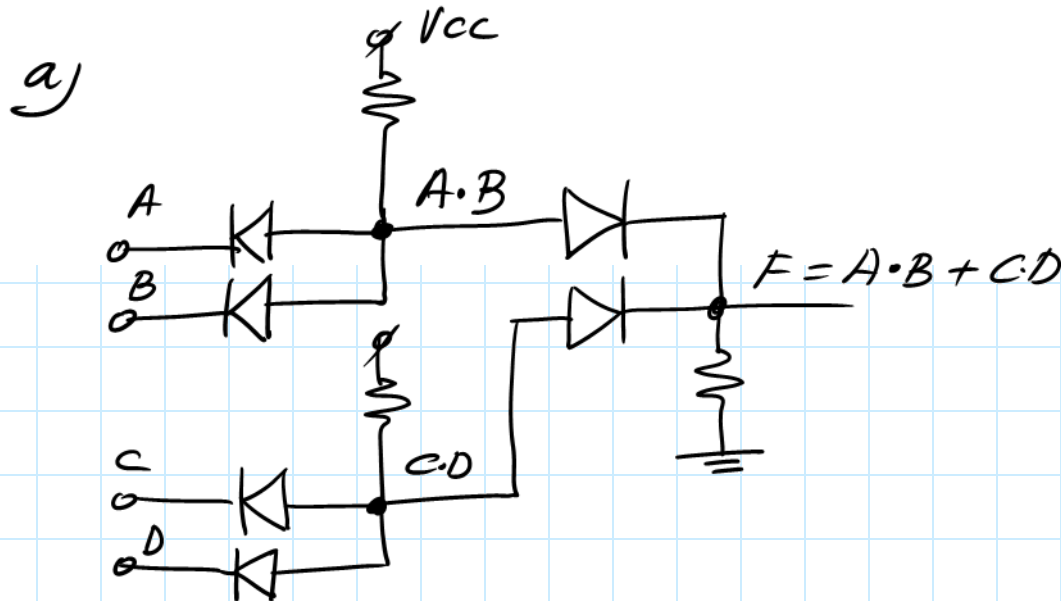

b1)

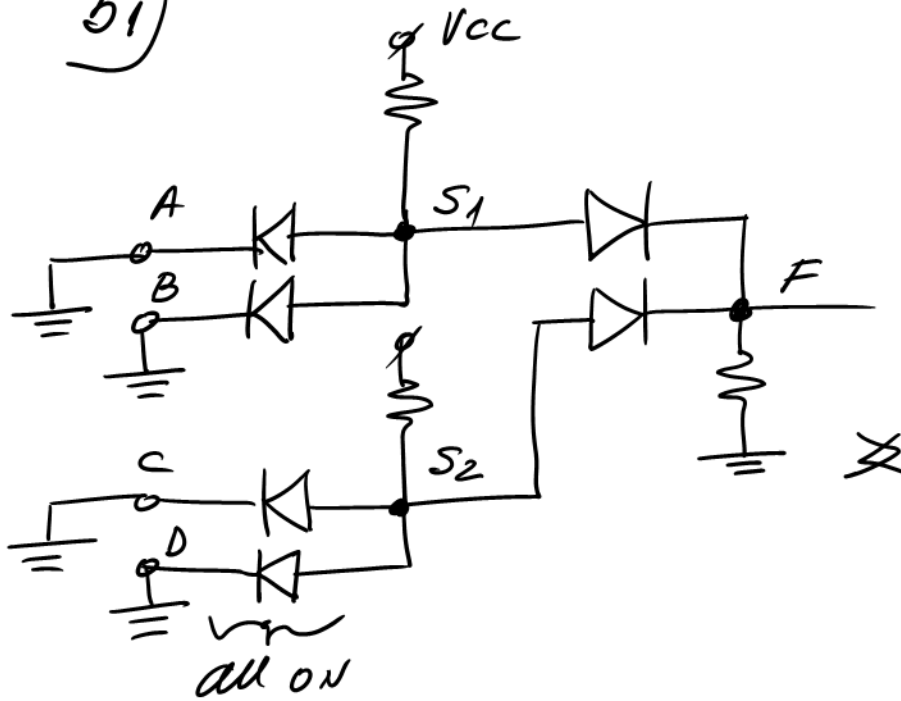


all AND gates diodes on


$$\Rightarrow V_{S1} = V_{S2} = 0V \Rightarrow$$

Diodes OR gate OFF

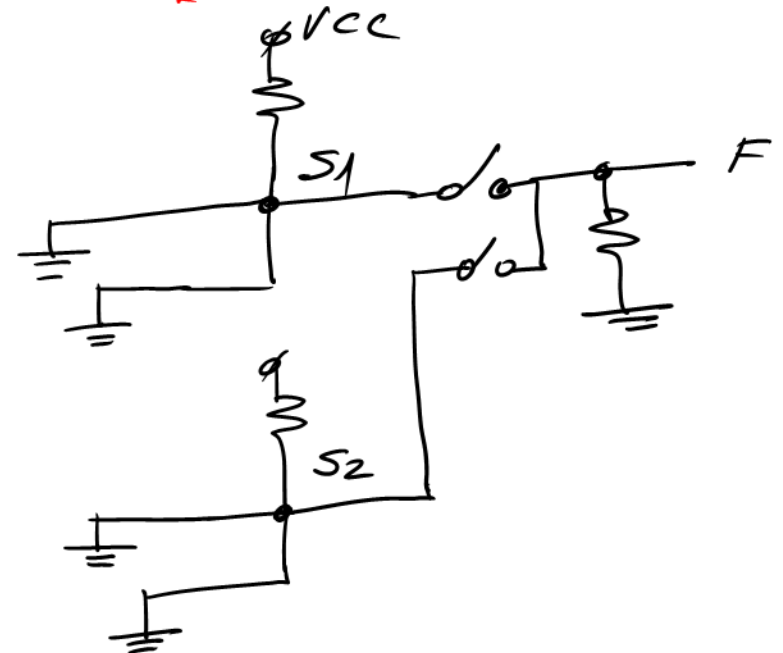
$$\Rightarrow V_F = 0V \Rightarrow F = 0$$



b2)

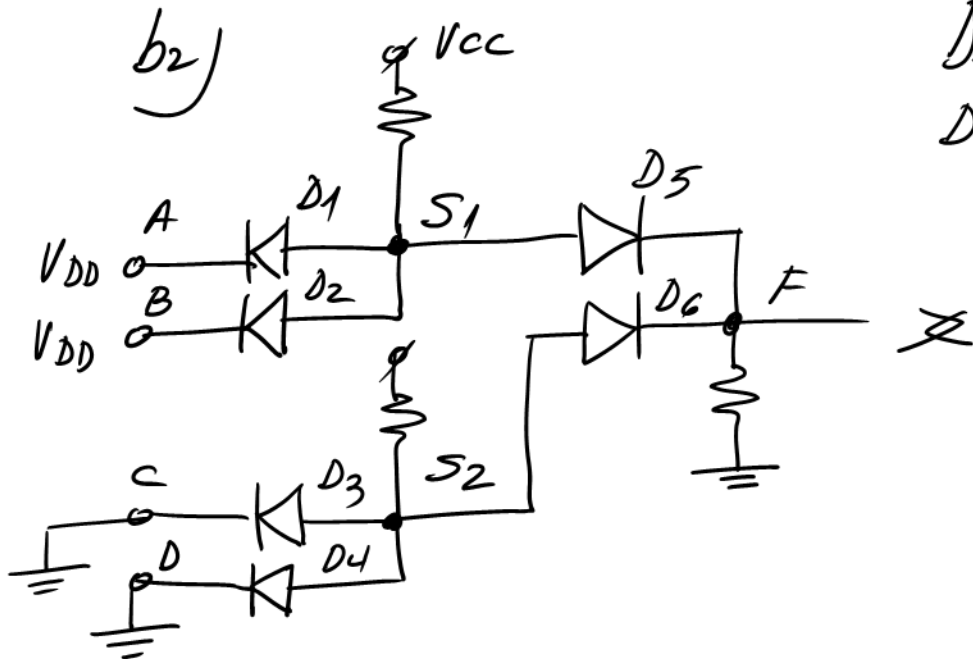

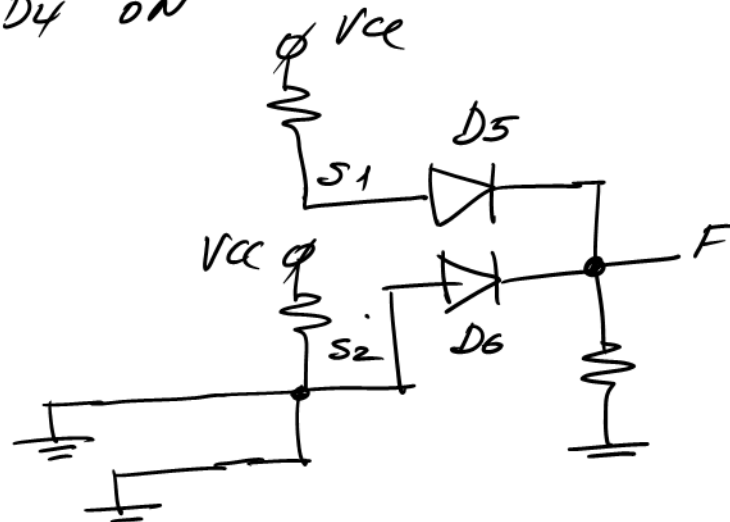D_1, D_2 OFF $\Rightarrow V_{S1} = V_{cc}$; $S_1 = 1$
 D_3, D_4 ON




$V_{S2} = 0V \Rightarrow D_6$ OFF

D_5 ON \Rightarrow



$$I = \frac{V_{cc}}{2R}$$

$$V_F = RI = \frac{V_{cc}}{2}$$

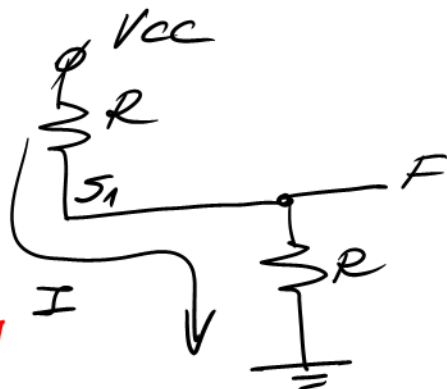


$F = 1$, but we have $1/2 V_{cc}$ at the output !!

b3)

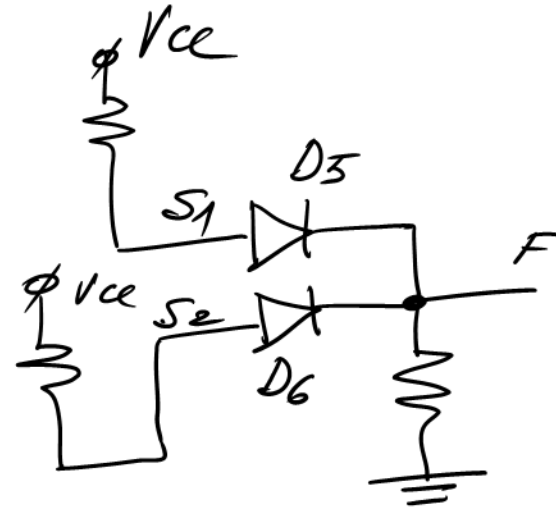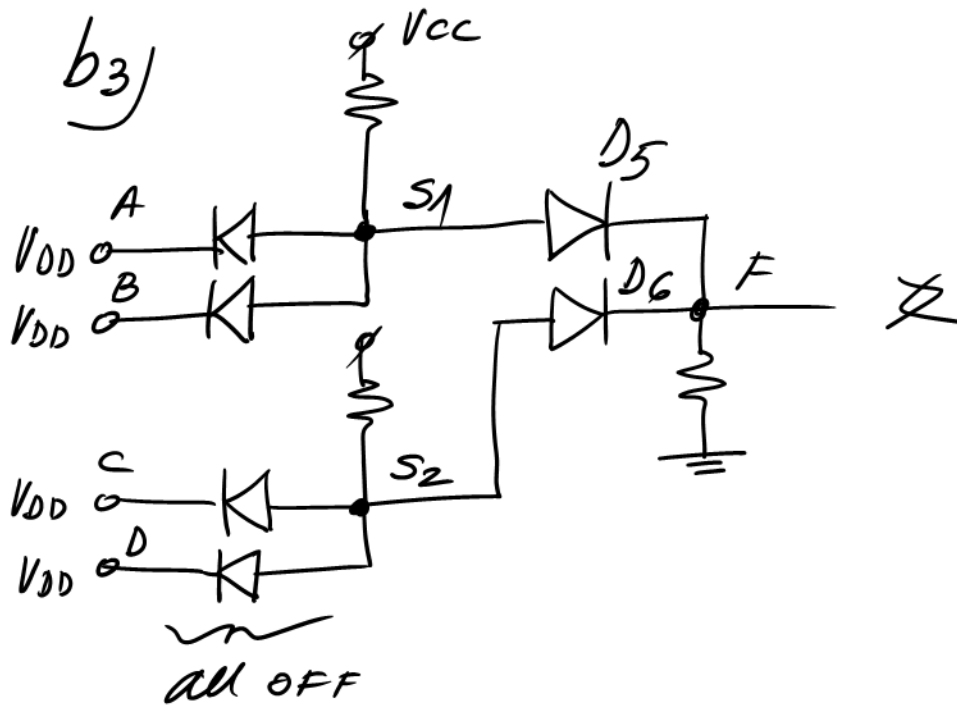

D_5, D_6 ON:





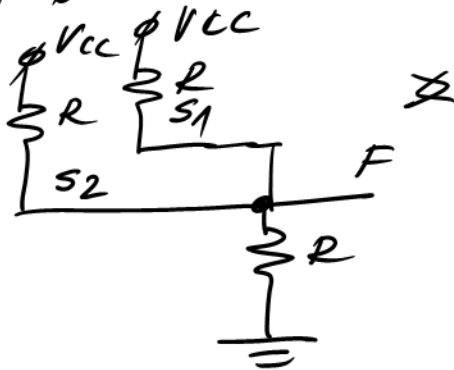


$$F; \boxed{V_F = V_{CC} \frac{R}{R + R/2} = \frac{2}{3} V_{CC}}$$



$F = 1$; but we have also voltage drop at the output $V_F \Rightarrow$ We need an active element!

CH1. BASIC SEMICONDUCTOR DEVICES

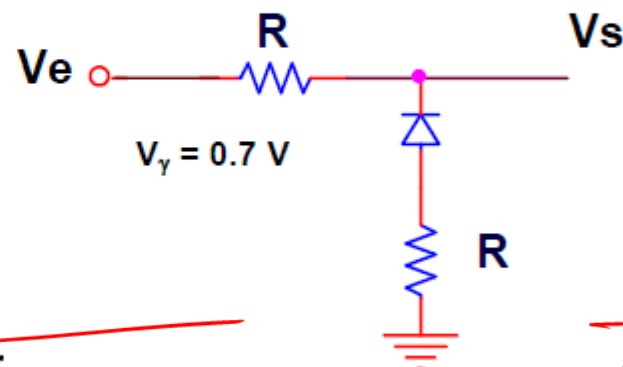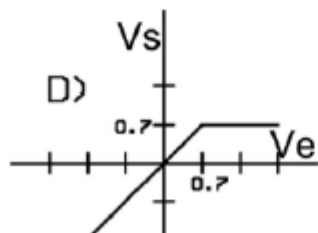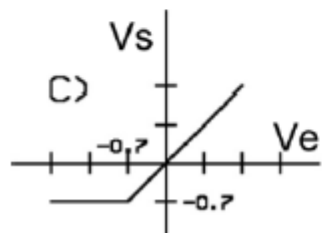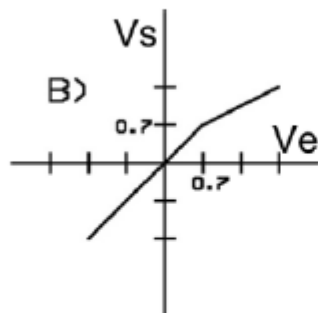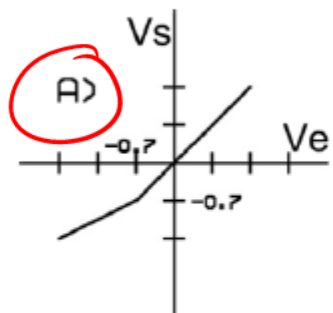11. Given the circuit of the figure, determine which of the following curves (A,B,C,D) is its corresponding transference curve.


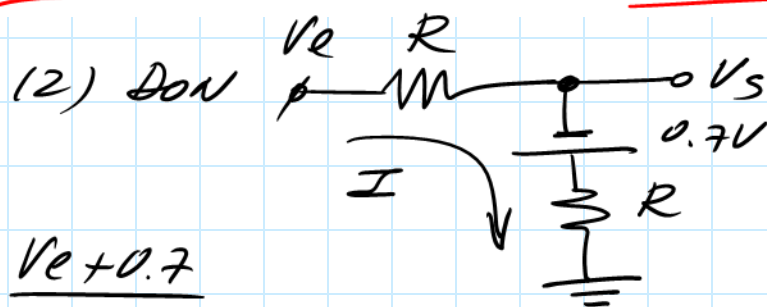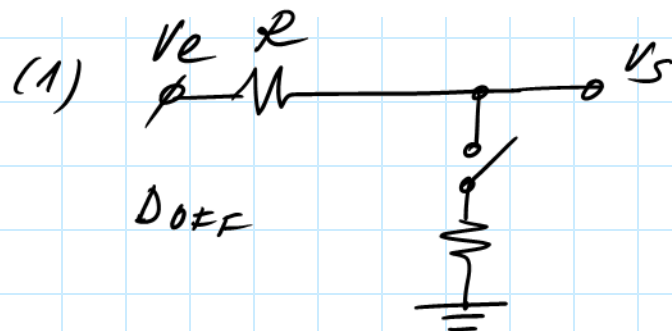
$$\begin{aligned} V_e \geq -0.7V &\Rightarrow \text{DOFF} \Rightarrow V_s = V_e \quad (1) \\ V_e < -0.7V &\Rightarrow \text{DON} \Rightarrow V_s = \frac{V_e - 0.7}{2} \quad (2) \end{aligned}$$



$$I = \frac{V_e + 0.7}{2R}$$

$$V_s = V_e - RI = V_e - \frac{V_e + 0.7}{2} = \frac{V_e - 0.7}{2}$$