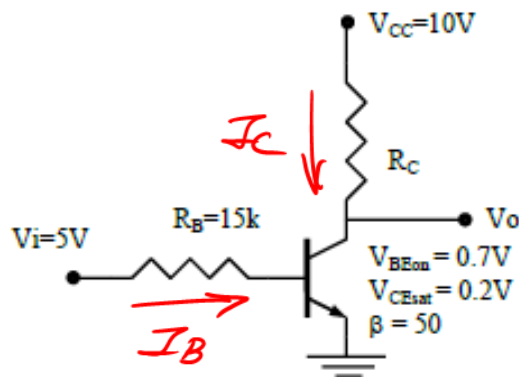


CH1. BASIC SEMICONDUCTOR DEVICES

31. In the following circuit with transistor of the figure, which R_C value will get the transistor in the limit among active and saturation regions?



Conditions in the limit:

a) $V_{CE} = V_{CE(sat)} = 0.2V$

b) $I_C \leq \beta I_B$

→ (=) in the limit

a) $I_B = \frac{V_i - V_{BE(on)}}{R_B} = 0.29mA$; $I_C = I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{9.8}{R_C}$

b) $I_C \leq \beta I_B = 14.33mA$; $14.33 \geq I_{C(sat)} = \frac{9.8}{R_C}$

$$R_C \geq \frac{9.8}{14.33} = 0.68K$$


$R_C = 0.68K \Rightarrow$ limit } active
sat.

$R_C > 0.68K \Rightarrow$ saturation

CH1. BASIC SEMICONDUCTOR DEVICES

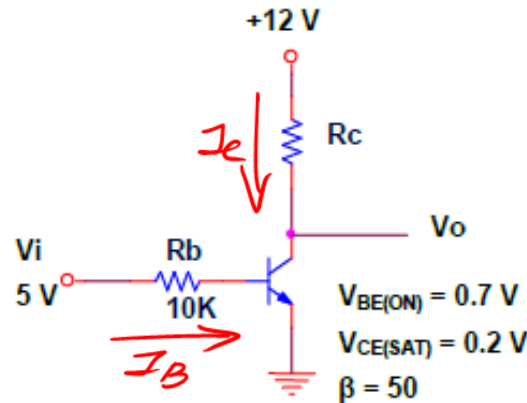(32) In the BJT transistor circuit of figure, what is the minimum resistance R_C which leads the transistor to saturation?

- [A] $R_C = 549\Omega$
- [B] $R_C = 558\Omega$
- [C] $R_C = 472\Omega$
- [D] None of the above.



$$\text{Sat} \Rightarrow V_{CE} = V_{CE(SAT)} = 0.2 \text{ V}; \quad I_C = I_E(SAT) = \frac{12 - V_{CE(SAT)}}{R_C} = \frac{11.8}{R_C}$$

$$I_B = \frac{5 - 0.7}{10 \text{ K}} = 0.43 \text{ mA}$$

$$\text{Sat} : \quad I_C < \beta I_B \Rightarrow \frac{11.8}{R_C} < 50 \cdot 0.43 = 21.5 \text{ mA}$$

$$\boxed{R_C > \frac{11.8}{21.5} = 0.549 \text{ K}}$$

CH1. BASIC SEMICONDUCTOR DEVICES


37. Given the circuit of the figure, calculate the value of the limits of the input voltage V_i that lead the transistor to switching mode (V_{iOFF} , V_{iSAT})

DATA:

$$V_{CE(SAT)} = 0.2V$$

$$V_{BE(ON)} = 0.7V$$

$$\beta = 50;$$

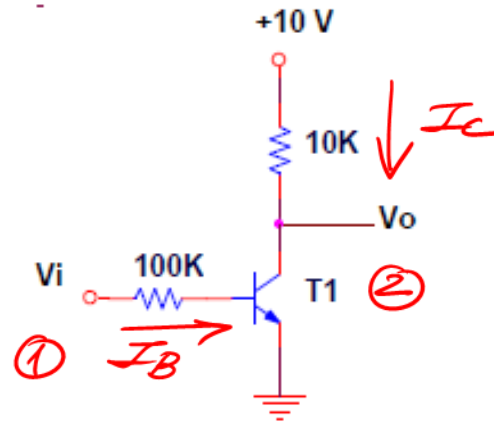

a) V_{iOFF} (T_1 OFF)

$$V_i \leq V_{BE(ON)} = 0.7V \Rightarrow T_1 \text{ OFF};$$

$$V_i \leq 0.7 \Rightarrow T_1 \text{ OFF}$$

b) V_{iSAT} (T_1 ON)

$$\text{Input loop} \Rightarrow I_B = \frac{V_i - V_{BE(ON)}}{100K} = \frac{V_i - 0.7}{100K}$$

$$\text{Output loop} \Rightarrow I_C = \frac{10 - V_{CE(SAT)}}{10K} = \frac{10 - 0.2}{10K} = 0.98 \text{ mA}$$

$$\text{SAT} \Rightarrow I_C < \beta I_B \Rightarrow 0.98 < \frac{50(V_i - 0.7)}{100} = \frac{V_i - 0.7}{2}$$

$$V_i > 0.7 + 2 \cdot 0.98 = 1.26V$$

$$V_i > 2.66V \Rightarrow T_1 \text{ SAT}$$

CH1. BASIC SEMICONDUCTOR DEVICES

(35) The circuit of figure is a logic inverter. ¿What will be the minimum voltage at the input for output saturation? ($V_{e\text{MIN(SAT)}}$)

[A] $V_{e\text{MIN(SAT)}} = 2.5\text{V}$

[B] $V_{e\text{MIN(SAT)}} = 2.7\text{V}$

[C] $V_{e\text{MIN(SAT)}} = 3.1\text{V}$

[D] $V_{e\text{MIN(SAT)}} = 5\text{V}$

Data:


$\beta: 100$

$R1 = 100\text{k}$

$R2 = 2\text{k}$

$V_{CC} = 5\text{V}$

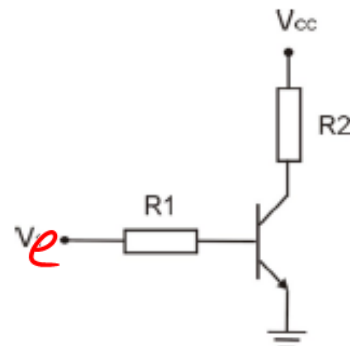$V_{BE(ON)} = 0.7, V_{CESAT} = 0.2\text{V}$



$$SAT: V_{CE} = V_{CE(SAT)} = 0.2\text{V}; I_C = I_C(SAT) = \frac{V_{CC} - V_{CE(SAT)}}{R2} = \frac{5 - 0.2}{2} = 2.4\text{mA}$$

$$I_B = \frac{V_e - V_{BE(ON)}}{R1} = \frac{V_e - 0.7}{100}$$

$$SAT: I_e < \beta I_B \Rightarrow 2.4\text{mA} < 100 \frac{V_e - 0.7}{100\text{k}}$$

$$\Rightarrow V_e > 2.4 + 0.7 = 3.1\text{V}$$

CH1. BASIC SEMICONDUCTOR DEVICES


39. What will be the output of the following circuit if the input is a square wave with amplitude from 0V to 2V? (Data: $\beta = 100$; $V_{CE\text{ SAT}} = 0.2\text{V}$; $V_{BE\text{ ON}} = 0.7\text{V}$).

[A] A square wave with an amplitude from 0.7V to 5V. \times

[B] A sine wave of same frequency and reverse phase. \times

[C] A square wave with an amplitude from 0.2V to 5V. \checkmark

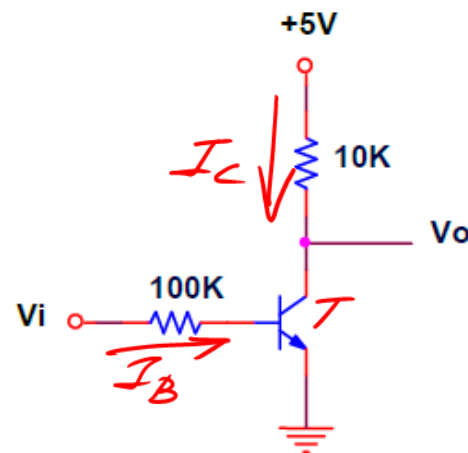[D] A square wave with an amplitude from 2V to 5V. \times



a)

$$V_i = 0\text{V} < V_{BE(\text{ON})} \Rightarrow T \text{ OFF} \Rightarrow I_B = I_C = 0\text{mA} \Rightarrow \boxed{V_o = V_{CE} = V_{CC} = 5\text{V}}$$

$$b) V_i = 2\text{V} > V_{BE(\text{ON})} \Rightarrow T \text{ ON}; \quad I_B = \frac{V_i - V_{BE(\text{ON})}}{100\text{K}} = \frac{5 - 0.7}{100\text{K}} = 0.043\text{mA}$$

Assume saturated


$$I_C = I_{C(\text{SAT})} = \frac{V_{CC} - V_{CE(\text{SAT})}}{10\text{K}} = \frac{5 - 0.2}{10\text{K}} = 0.48\text{mA}$$

$$\text{as } 0.48\text{mA} = I_C < \beta I_B = 4.3\text{mA} \Rightarrow T \text{ saturated}$$

$$\text{an } \boxed{V_o = V_{CE(\text{SAT})} = 0.2\text{V}}$$

CH1. BASIC SEMICONDUCTOR DEVICES

40. Given the circuit of the figure:

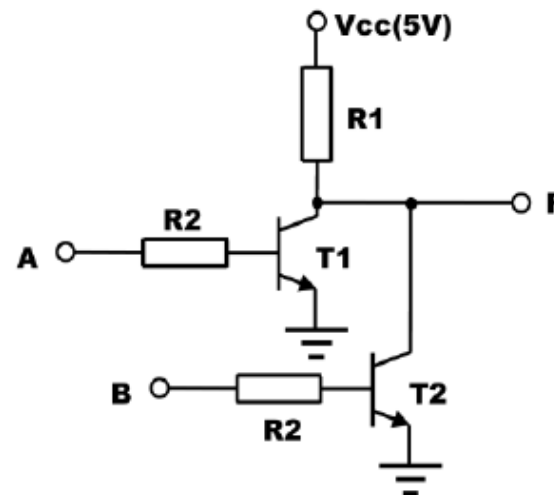

DATA: $V_{BE(ON)} = 0.6V$; $V_{CE(SAT)} = 0.2V$; $R1 = 1k$; $R2 = 200k$; $\beta = 500$.
Inputs ("1" \rightarrow 5V; "0" \rightarrow 0V)

A) Truth table and state of T_1 and T_2 for all input combinations:


A	B	T_1	T_2	F	V_F (Volts)
0	0	OFF	OFF	1	$V_{CC} (5V)$
0	1	OFF	ON	0	0.2 V
1	0	ON	OFF	0	0.2 V
1	1	ON	ON	0	0.2 V

} $\rightarrow V_{CE(SAT)}$, but we have to check (See C)

B) Logic function

$$F = \overline{A+B} \quad (\text{NOR})$$


CH1. BASIC SEMICONDUCTOR DEVICES

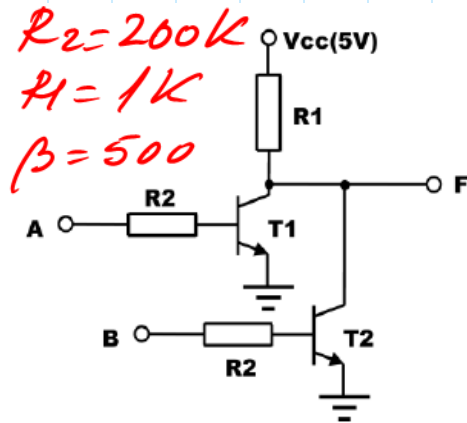

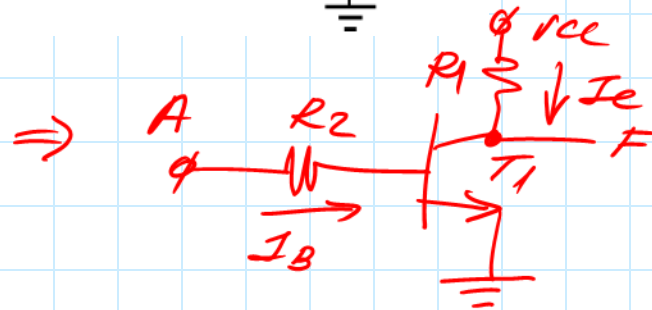c) Voltage in F for all combinations

Case c1) $A = B = 0 \Rightarrow T1 \text{ OFF} \Rightarrow T2 \text{ OFF} \Rightarrow \boxed{V_F - V_{CC} = 5V}$

Case c2) $A = 1; B = 0$ } One trans. ON and
 $A = 0; B = 1$ } another OFF



Minimum voltage of V_A for saturation:

$$I_{C(SAT)} = \frac{V_{CC} - V_{CE(SAT)}}{R_1} = \frac{5 - 0.2}{1k} = 4.8mA$$


$$I_B = \frac{V_A - V_{BE(ON)}}{R_2} \quad \left\{ \begin{array}{l} \frac{500 (V_A - 0.7)}{200} > 4.8mA \Rightarrow - \\ V_A > 0.7 + \frac{4.8 \cdot 2}{5} = 2.62V \end{array} \right.$$

$V_A > 2.62V \Rightarrow T_1$ saturated

as $V_A = 5V$ (High level) $\Rightarrow T_1$ saturated \Rightarrow

$$\boxed{V_F = V_{CE(SAT)} = 0.2V}$$

CH1. BASIC SEMICONDUCTOR DEVICES

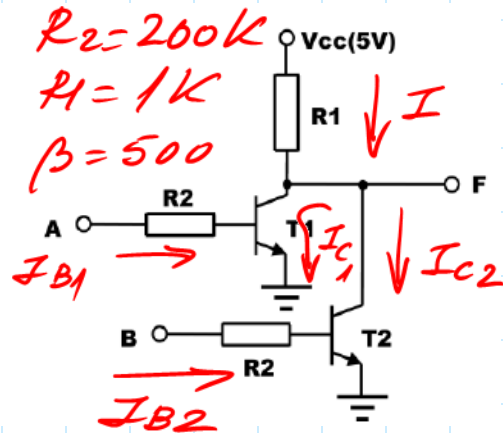

Case a) $A = B = 1 \Rightarrow T1 \text{ ON}$
 $T2 \text{ off}$

$I = I_{C1} + I_{C2}$ (Current through R_1 is split in two) Assuming both transistors

equal: $I_{C1} = I_{C2} = \frac{I}{2} = I_C$ (also $I_{B1} = I_{B2} = I_B$)

Minimum V_A (or V_B) for saturation \Rightarrow Assume saturated both transistors $\Rightarrow I = \frac{V_{CC} - V_{CE(SAT)}}{R_1} = 4.8 \text{ mA}$

$$\begin{aligned}
 I_C &= \frac{I}{2} = 2.4 \text{ mA} = I_{C(SAT)} \\
 I_B &= \frac{V_A - V_{BE(ON)}}{R_B} \\
 \beta I_B &> I_{C(SAT)}
 \end{aligned}
 \left\{
 \begin{aligned}
 &500 \frac{V_A - 0.7}{200} > 2.4 \text{ mA} \Rightarrow
 \end{aligned}
 \right.$$

$$V_A > 0.7 + 2.4 \frac{2}{5} = 1.66 \text{ V for sat. (The same for } V_B)$$

$$\text{As } \begin{cases} V_A = 5V \\ V_B = 5V \end{cases} \left\{ \begin{array}{l} T1 \\ T2 \end{array} \right\} \text{ saturated} \Rightarrow \boxed{V_F = 0.2 \text{ V}}$$