

5.2.3 Design of general functions in CMOS Complementary Logic (1)

General case:

- NMOS and PMOS blocks are dual

Series structures $\rightarrow \cdot$ (AND)

Parallel structures $\rightarrow +$ (OR)

\rightarrow Intermediate function G

- NMOS block

connected to ground


$$F = \overline{G} \text{ (use inverted function)}$$

- PMOS block

connected to V_{DD}

$F = G$, but inverted inputs

(use direct function)



 


CMOS complementary logic

5.2.3 Design of general functions in CMOS Complementary Logic (2)


- Any inverted function can be implemented
- Ex: $Y = \overline{(A.B) + (C.D)}$ (AND-OR-INVERT-22)

$\hookrightarrow G = AB + CD$

   

8 transistors

Chip area and power reduction

 

16 transistors (double!)

5.2.3 Design of general functions in CMOS Complementary Logic (3)


Example: OAI-31

$Y = \overline{(A + B + C) \cdot D} \rightarrow$ Take $G = (A + B + C) \cdot D$
and draw first NMOS network

5.2.3 Design of general functions in CMOS Complementary Logic (4)

Example: OAI-31

$$Y = \overline{(A + B + C).D}$$

 

5.2.3 Design of general functions in CMOS Complementary Logic (5)

- If the function is not inverted:
- We have two solutions:
 1. Transform it to an equivalent inverted function, applying involution and De Morgan laws:
 - NMOS block design
 - PMOS block design with dual structure of NMOS block.
 2. Design from PMOS block, inverting the inputs. NMOS block is designed with the dual structure of the PMOS.
- Example: design the carry out function of a full-adder:

$$F = AB + AC + BC$$

5.2.3 Design of general functions in CMOS Complementary Logic (3)


Example: OAI-31

$$Y = \overline{(A + B + C) \cdot D}$$

5.2.3 Design of general functions in CMOS Complementary Logic (4)

Example: OAI-31

$$Y = \overline{(A + B + C).D}$$

 


5.2.3 Design of general functions in CMOS Complementary Logic (5)

- If the function is not inverted:
- We have two solutions:
 1. Transform it to an equivalent inverted function, applying involution and De Morgan laws:
 - NMOS block design
 - PMOS block design with dual structure of NMOS block.
 2. Design from PMOS block, inverting the inputs. NMOS block is designed with the dual structure of the PMOS.
- Example: design the carry out function of a full-adder:

$$F = AB + AC + BC$$

 $Y = AB + AC + BC$; $G = AB + AC + BC$ and
draw first PMOS net inverting inputs



Note: Applying de Morgan Laws:

$$Y = \overline{AB + AC + BC} = \overline{AB} \cdot \overline{AC} \cdot \overline{BC} = (\overline{A+B}) \cdot (\overline{A+C}) \cdot (\overline{B+C})$$

and we can design before NMOS net

5.2.4 Transmission gates (1): NMOS

- Bi-directional switch that opens or closes controlled by an external signal

- NMOS transmission gate:

- If $V_G = 0V \rightarrow$ Open Switch $\rightarrow V_O = 0V$

- If $V_G = V_{DD} \rightarrow$ Closed Switch $V_O = V_I?$


The transmission of "1" degrades V_T volts

The transmission of "0" is not degraded

$$\begin{aligned} T_{ON} &\Rightarrow \\ V_G > V_T &\Rightarrow \\ V_G - V_S > V_T &\Rightarrow \end{aligned}$$


$$V_S < V_G - V_T$$

$$V_O < V_G - V_T$$

 

Bidirectional
 $V_I \leftrightarrow V_O$
analog switch


5.2.4 Transmission gates (2): NMOS

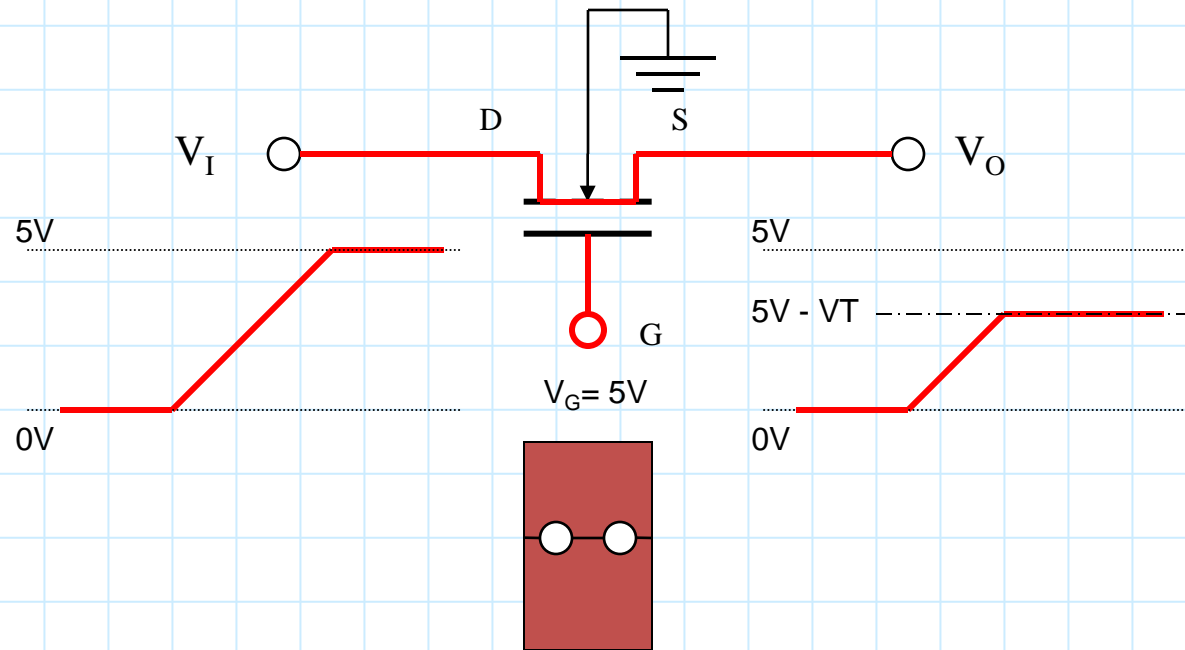

-




11

 

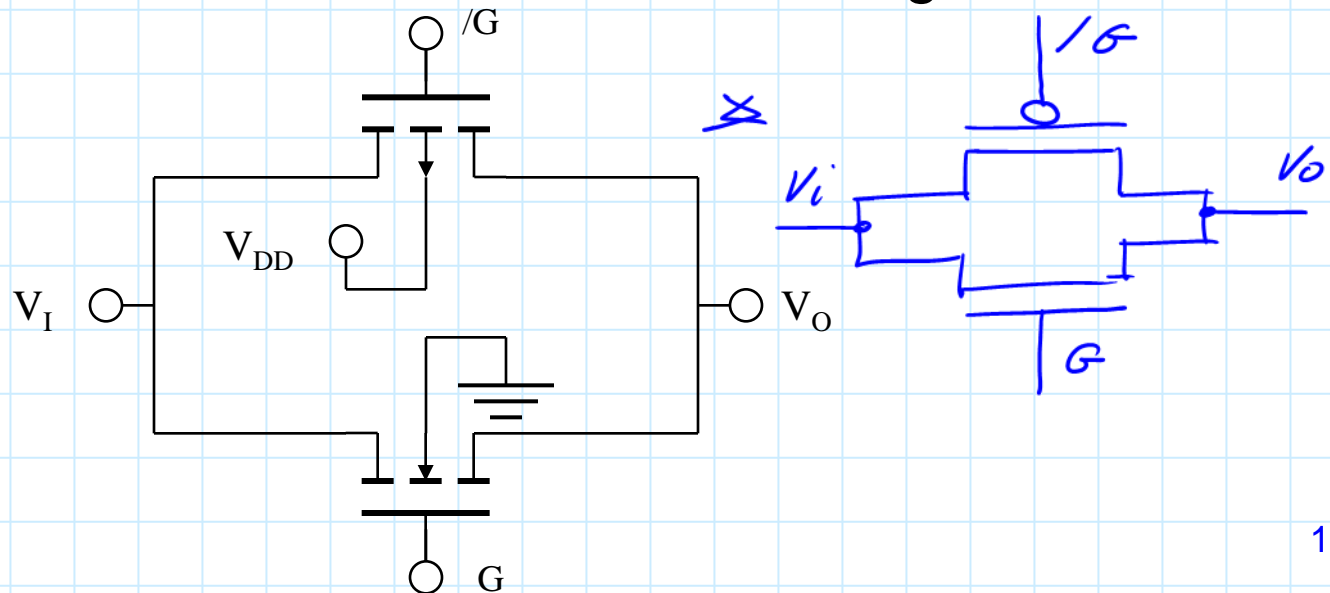
5.2.4 Puertas de transmisión (5): CMOS

- They join the characteristics of the two gates (NMOS and PMOS), not degrading the output
 - If $V_G = 0V \rightarrow$ NMOS and PMOS **OFF** $\rightarrow V_O = 0V$
 - If $V_G = V_{DD} \rightarrow$ NMOS and PMOS **ON**
The NMOS transmits the "0" without degradation
The PMOS transmits the "1" without degradation




 5.2.4 Transmission gates (6): Multiplexer

- Analog multiplexer
 - Inputs V_A , V_B , selection Sel, output V_F




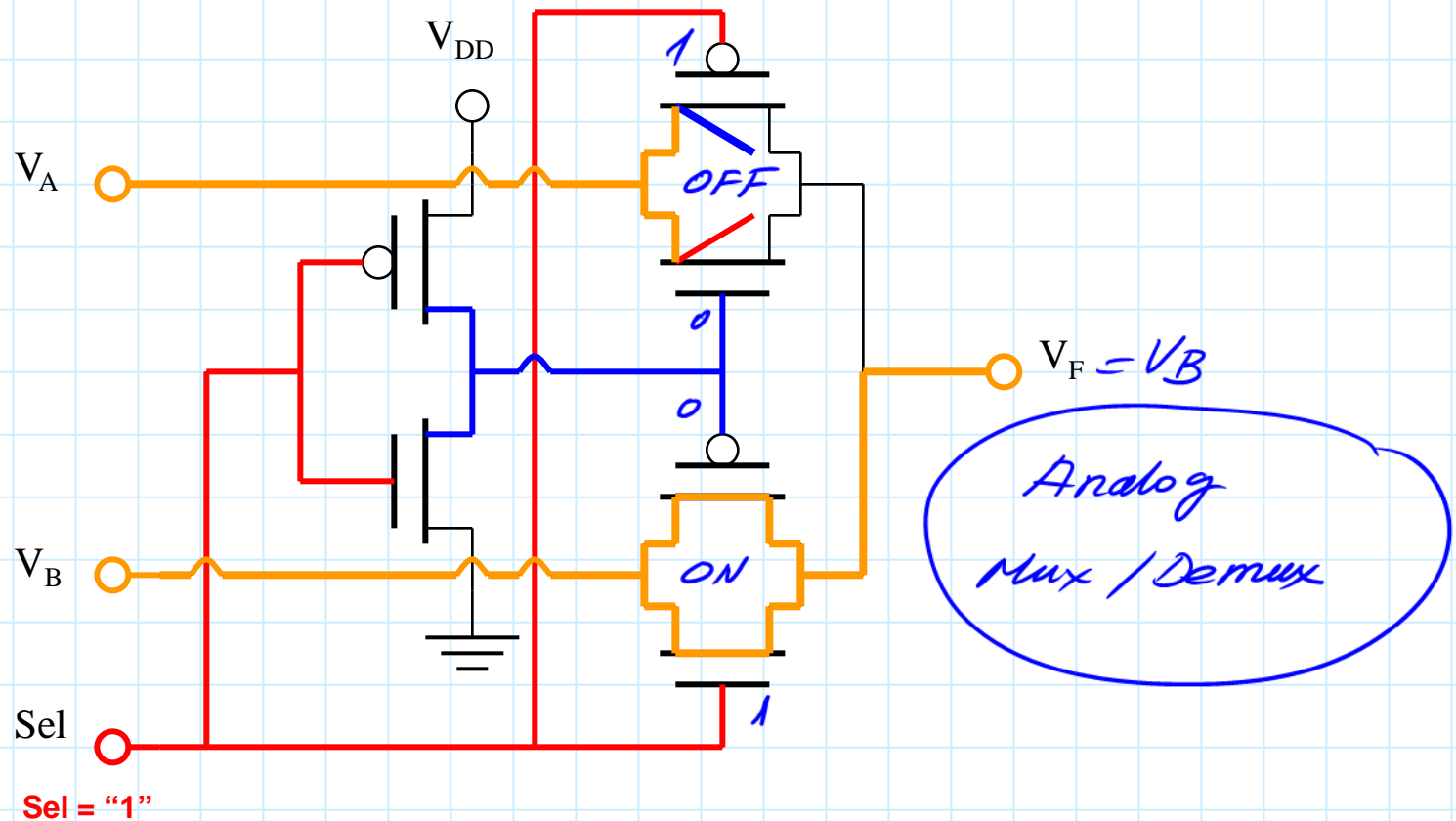5.2.4 Transmission gates (7): Multiplexer



 5.2.4 Transmission gates (8): Multiplexer

- Digital multiplexer: CMMOS inverter at the output




- 8 transistors \rightarrow area and consumption saving, compared to a traditional design

 5.2.4 Transmission gates (9): Multiplexer

- Design of the multiplexer with basic gates:
- How many transistors do we need?
(exercise)

$$F = B \cdot Sel + A \cdot \overline{Sel}$$



Total: 20 transistors!