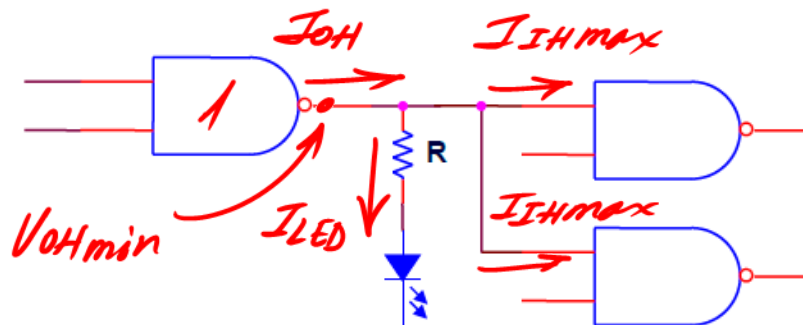


# UNIT 3. LOGIC FAMILIES

23. The LED of figure with a resistor R of 50  $\Omega$ , is inserted in the digital circuit to display an internal variable. Taking into account the specifications of the logic gates as detailed in the following table, and  $V_{Y(LED)}=1.8V$ , a) Is this connection correct? If it is correct, how many inputs can be connected in total? If not, what is the value of R which allows connecting up to four inputs?



$$I_{OH} = I_{LED} + 2I_{IHmax} \leq |I_{OHmax}|$$

$V_{IHmin}$	$V_{ILmax}$	$V_{OHmin}$	$V_{OLmax}$
2.5V	0.8 V	2.3 V	0.2 V
$I_{IHmax}$	$I_{ILmax}$	$I_{OHmax}$	$I_{OLmax}$
1 mA	-3.5 mA	-16 mA	25 mA

Led on when gate 1 to HIGH level

$$I_{LED} = \frac{V_{OHmin} - V_{LED}}{R} = \frac{2.3 - 1.8}{50} = 0.01A = 10mA$$

$$I_{LED} + 2I_{IHmax} = 12mA$$

as  $|I_{OHmax}| = 16mA > 12mA$   
 $\Rightarrow$  Correct connection

How many inputs?

$$|I_{OHmax}| \geq I_{LED} + n \cdot I_{IHmax}$$

$$16 \geq 10 + n \cdot 1 \Rightarrow \underline{\underline{n \leq 6}}$$

## UNIT 3. LOGIC FAMILIES

25. We want to connect the outputs of 2 standard components of a logic family with a voltage supply of 5V, to 3 inputs of components of the same family. The specifications of the family are shown in the following table:

$V_{IHmin}$	$V_{ILmax}$	$V_{OHmin}$	$V_{OLmax}$
2 V	0.8 V	2.4 V	0.4 V
$I_{IHmax}$	$I_{ILmax}$	$I_{OHmax}$	$I_{OLmax}$
40 $\mu$ A	-1.6 mA	-400 $\mu$ A	16 mA

To make correctly this connection:

- [A] We do not need to add anything more.  
[B] It should be added a pull-up resistor between the output and the voltage supply, with a range of possible values between 0.41 k $\Omega$  and 8.12 k $\Omega$ .  
[C] It cannot be done the connection of the outputs, since it would cause an undetermined voltage and the degradation of the output transistors.  
[D] It should be added a pull-up resistor between the output and the voltage supply, with a range of possible values between 0.41 k $\Omega$  and 11.82 k $\Omega$ .

*Voltage:*

$$V_{OHmin} \geq V_{IHmin} ? \Rightarrow OK$$

2.4                      2

$$V_{OLmax} \leq V_{ILmax} ? \Rightarrow OK$$

0.8                      0.4

*Voltage compatible*  $\leftarrow$

*Currents:*

$$I_{OLmax} \geq 3 |I_{ILmax}| ? \Rightarrow OK$$

16                      1.6

$$|I_{OHmax}| \geq 3 I_{IHmax} ? \Rightarrow OK$$

400  $\mu$                       40  $\mu$

*Current compatible.*


## UNIT 3. LOGIC FAMILIES

31. We want to connect a TTL open collector output with an input of a CMOS logic circuit powered to + 9V. Indicate the CORRECT answer:


Family A (TTL open collector)			Family B (CMOS +9V)			
$V_{OLmax}$	$I_{OHmax}$ (fugas)	$I_{OLmax}$	$V_{IHmin}$	$V_{ILmax}$	$I_{IHmax}$	$I_{ILmax}$
0.4 V	100 $\mu A$	16 mA	6.3 V	2.7 V	0.1 $\mu A$	-0.1 $\mu A$

- leakage*
- [A] It is necessary to connect a pull-up resistor between the output and the power supply. of + 9V. The value of the resistance must be between 0.54K $\Omega$  and 26.97K $\Omega$ .
- [B] We can connect both families directly.
- [C] It is necessary to insert a TTL buffer to make the current compatible at low level.
- [D] It is necessary to connect a pull-up resistor between the output and the power supply. of + 9V. The value of the resistance must be between 2.1K $\Omega$  y 41.4K $\Omega$ .

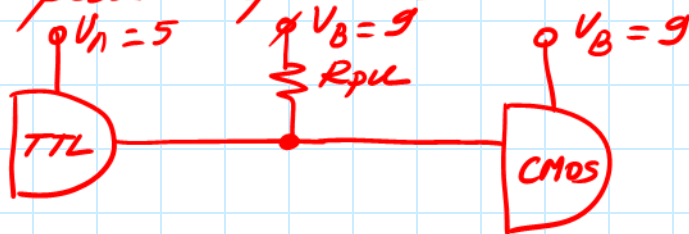*TTL is open collector  $\Rightarrow$  Need a pull-up resistor*



a) High level

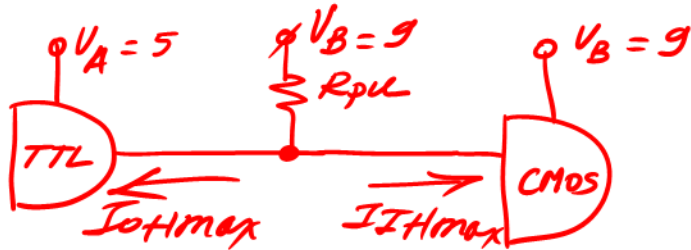


$$R_{pu} \leq \frac{V_B - V_{IHmin}}{I_{OHmax} + I_{IHmax}} = \frac{9 - 6.3}{0.1 + 0.0001}$$

$$R_{pu} \leq 26.97K$$

(No noise margin)

b) Low level

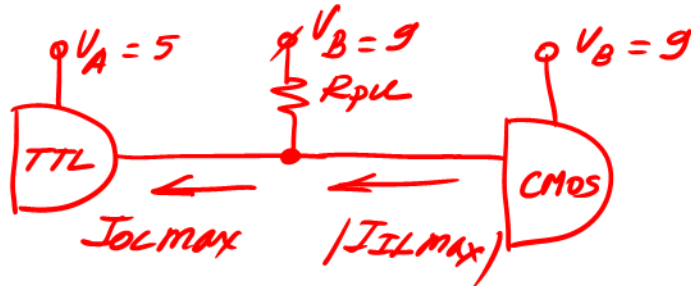


$$R_{pu} \geq \frac{V_B - V_{OLmax}}{I_{OLmax} - |I_{ILmax}|}$$

$$R_{pu} \geq \frac{9 - 0.4}{16 - 0.0001} = 0.538K$$

$$0.538K \leq R_{pu} \leq 26.97K$$

# UNIT 3. LOGIC FAMILIES

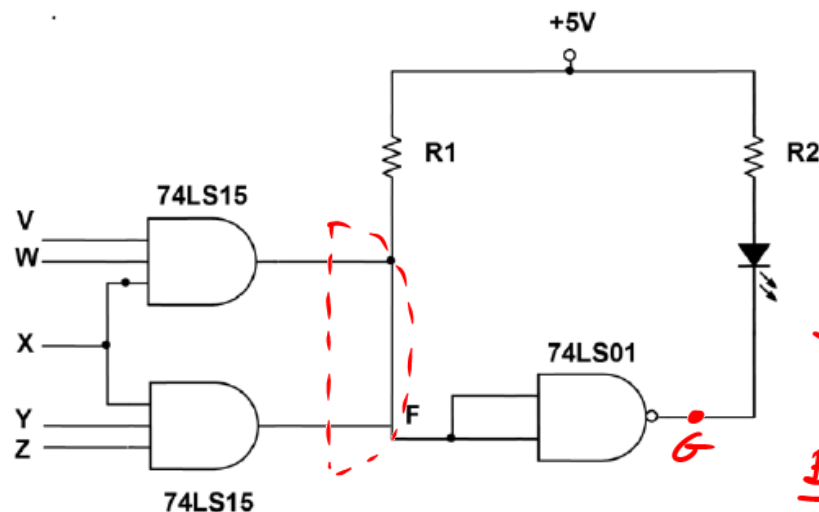32. The following circuit uses logic gates with open collector output (within the 74LS01 and 74LS15 integrated circuits) to implement a "wired AND", and to activate the LED output.



A)  $F = (V \cdot W \cdot X) \cdot (X \cdot Y \cdot Z) = VWXYZ$


B)  $F = 1 \Rightarrow G = 0 \Rightarrow V_G = V_{OL}$   
and LED is ON, as cathode has a low voltage

- A. Write a logical expression for the function implemented by the circuit in the signal F.  
 B. When  $F = '1'$ , Is the LED on or off?  
 C. Design R2, assuming that the current through the LED when it lights is  $I_{LED(on)} = I_{OLmax}$  and  $V_{LED(on)} = 1.2V$ .  
 D. Taking into account the following features for 74LS01 and 74LS15 integrated circuits, calculate the range of values allowed for R1:

Vcc	V <sub>IHmin</sub>	V <sub>ILmax</sub>	V <sub>OLmax</sub>	I <sub>IHmax</sub>	I <sub>OHmax</sub> (Leakage)	I <sub>OLmax</sub>	I <sub>ILmax</sub>
5 V	2.5V	0.8 V	0.5 V	20 $\mu$ A	100 $\mu$ A	7 mA	-0.36 mA

# UNIT 3. LOGIC FAMILIES

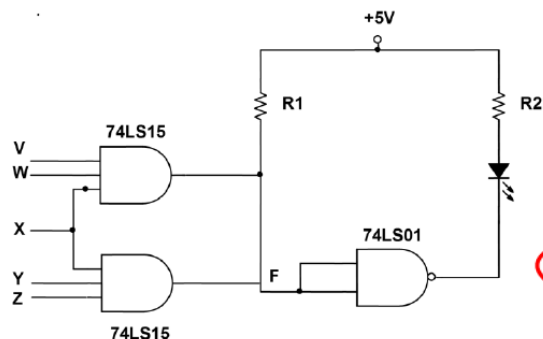32. The following circuit uses logic gates with open collector output (within the 74LS01 and 74LS15 integrated circuits) to implement a "wired AND", and to activate the LED output.



- Write a logical expression for the function implemented by the circuit in the signal F.
- When  $F = '1'$ , Is the LED on or off?
- Design  $R_2$ , assuming that the current through the LED when it lights is  $I_{LED(on)} = I_{OLmax}$  and  $V_{LED(on)} = 1.2V$ .
- Taking into account the following features for 74LS01 and 74LS15 integrated circuits, calculate the range of values allowed for  $R_1$ :

$V_{CC}$	$V_{IHmin}$	$V_{ILmax}$	$V_{OLmax}$	$I_{IHmax}$	$I_{OHmax}$ (Leakage)	$I_{OLmax}$	$I_{ILmax}$
5 V	2.5V	0.8 V	0.5 V	20 $\mu A$	100 $\mu A$	7 mA	-0.36 mA

$$C) R_2 = \frac{5 - V_{OLmax} - V_{LED}}{I_{LED}}$$

$$\frac{5 - 0.5 - 1.2}{7} = 0.471K \quad (471\Omega)$$

$$\frac{V_{CC} - V_{OLmax}}{I_{OLmax} - 2|I_{ILmax}|} = \frac{5 - 0.5}{7 - 2 \cdot 0.36}$$

$$R_1 \geq 0.717K$$

(HIGH)

$$R_1 \leq \frac{V_{CC} - V_{IHmin}}{2I_{OHmax} + 2I_{IHmax}} =$$


$$\frac{5 - 2.5}{2 \cdot 0.1 + 2 \cdot 0.02} = 10.417K$$

No noise margin

$$0.717K \leq R_1 \leq 10.417K$$

# UNIT 3. LOGIC FAMILIES

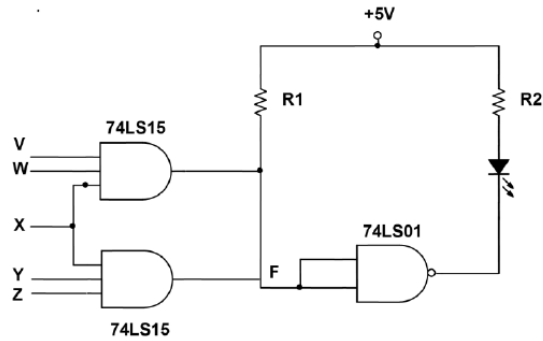32. The following circuit uses logic gates with open collector output (within the 74LS01 and 74LS15 integrated circuits) to implement a "wired AND", and to activate the LED output.



- Write a logical expression for the function implemented by the circuit in the signal F.
- When  $F = '1'$ , Is the LED on or off?
- Design R2, assuming that the current through the LED when it lights is  $I_{LED(on)} = I_{OLmax}$  and  $V_{LED(on)} = 1.2V$ .
- Taking into account the following features for 74LS01 and 74LS15 integrated circuits, calculate the range of values allowed for R1:

Vcc	V <sub>IHmin</sub>	V <sub>ILmax</sub>	V <sub>OLmax</sub>	I <sub>IHmax</sub>	I <sub>OHmax</sub> (Leakage)	I <sub>OLmax</sub>	I <sub>ILmax</sub>
5 V	2.5V	0.8 V	0.5 V	20 $\mu A$	100 $\mu A$	7 mA	-0.36 mA