



UNIVERSIDAD
POLITECNICA
DE VALENCIA



Computers Fundamentals

Subject 4. Sequential Circuits

- The study of basic sequential circuits
- The concept of timing diagram
- Basic operation of bistables: flip-flops and latches

1. Introduction

- Sequential circuits definition
- Clock
- timing diagram
- logical symbols


2. Bistables

- Latches (asynchronous) and Flip-Flops (synchronous)
- D flip-flop
- J-K Flip-flop
- Flip-flops with asynchronous inputs
- T Flip-flop

 3. Basic sequential blocks

- Storage registers
- Memory Bank
- Shift registers
- Counters

- **Sequential circuits** are divided into two main types:
 - **Synchronous** and **asynchronous** (Their classification depends on the timing of their signals)
- **Synchronous sequential circuits** change their states and output values at discrete instants of time, which are specified by the rising and falling edge of a free-running **clock signal**




- In **Asynchronous sequential circuits**, the transition from one state to another is initiated by the change in the primary inputs; there is no external synchronization.


- Sequential Circuits:

- The circuit outputs at the current instant $S(t)$ depends not only on the present value of the circuit inputs $E(t)$, but also on its "memory" or "stored state" $Q(t)$
- Are formed by
 - A combinational block
 - A block of memory elements to store the state Q
 - A clock input used to change the internal state of the circuit


Clock

 

 - A bistable circuit has two stable states 'high' and 'low'. It can be switched from one stable state to another other stable by applying a signal–level or a trigger pulse.
- Clock signal is used to synchronize the time at which bistable circuits switch from one state to other (memory-elements store the state of the circuit)




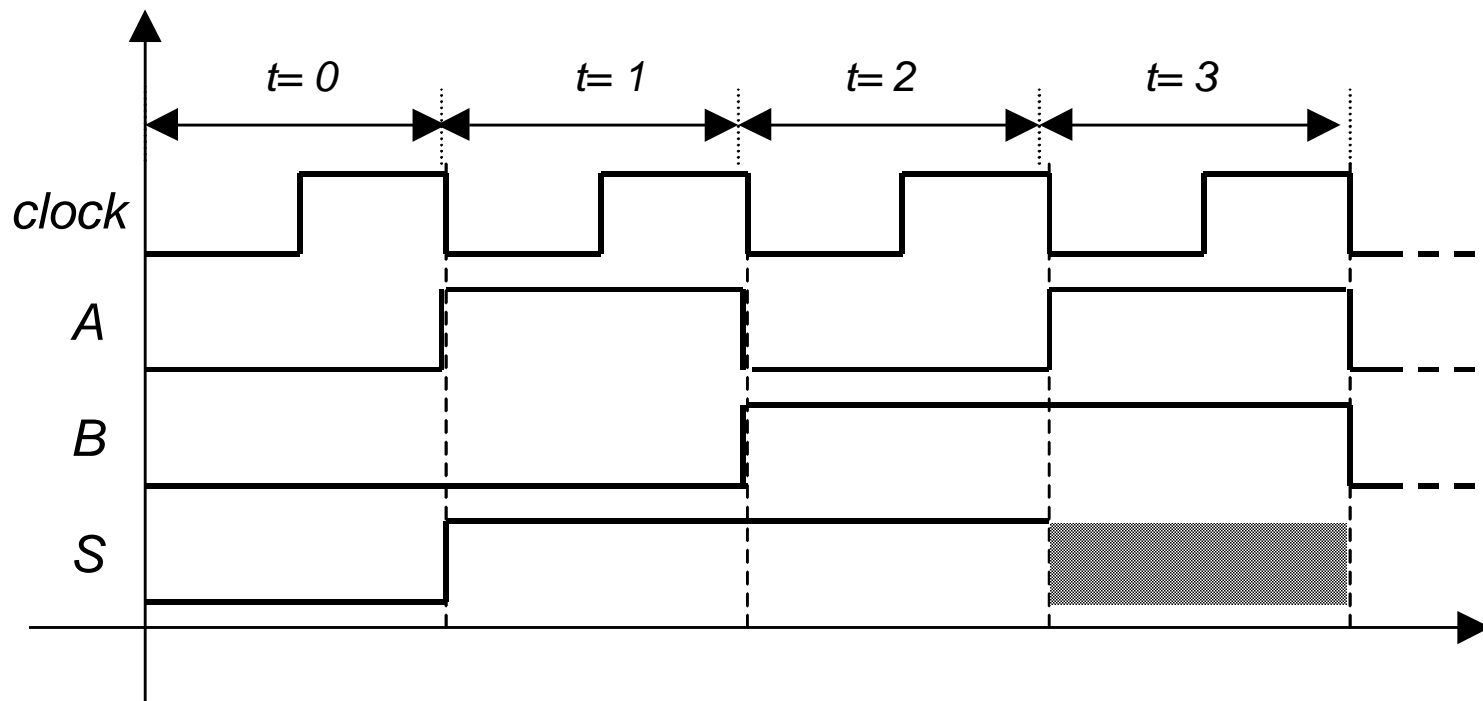- Timing diagram: Representation of the temporal evolution of the inputs and outputs of a circuit.
 - The undefined-value is shown shaded




- Logical Symbols


- Inputs y Outputs

 

Active high inputs

 


Low level active inputs

 


Outputs Q y /Q


- Clock

 


Active low

 

Active high

 



rising edge triggered

 

triggered by falling edge

- Bistable: Sequential circuit with two stable states (0 and 1). It can be switched from one stable state to another other stable by applying a signal-level or a trigger pulse.

  Doing that the information re-circulates indefinitely allowing us to store a bit in a circuit





Problem: We can not change the value stored!

Asynchronous bistables: Latches

FCO

How to change
the state of the
bistable?

  

Latch SR

Latch S-R

- Analysis: $Q(t+1) = \overline{R} + \overline{Q(t)}$ y $\overline{Q}(t+1) = \overline{S} + Q(t)$

	S	R	Q(t)	$\overline{Q}(t)$	Q(t+1)	$\overline{Q}(t+1)$	
0	0	0	0	0	1	1	→ 3 (Oscillate)
1	0	0	0	1	0	1	→ 1 (Stable)
2	0	0	1	0	1	0	→ 2 (Stable)
3	0	0	1	1	0	0	→ 0 (Oscillate)
4	0	1	0	0	0	1	→ 5
5	0	1	0	1	0	1	→ 5 (Stable)
6	0	1	1	0	0	0	→ 4
7	0	1	1	1	0	0	→ 4
8	1	0	0	0	1	0	→ 10
9	1	0	0	1	0	0	→ 8
10	1	0	1	0	1	0	→ 10 (Stable)
11	1	0	1	1	0	0	→ 8
12	1	1	0	0	0	0	→ 12 (Stable)
13	1	1	0	1	0	0	→ 12
14	1	1	1	0	0	0	→ 12
15	1	1	1	1	0	0	→ 12


Q(t+1)	$\overline{Q}(t+1)$
Q(t)	$\overline{Q}(t)$
0	1
1	0
0*	0*

Asynchronous Bistables: SR-NOR-Latch

FCO

Latch SR with NOR

Symbol

 


Truth table

* =undesirable situation

S	R	Q(t)	Q(t+1)	/Q(t+1)
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0*	0*
1	1	1	0*	0*

Logic Diagram

 


Reduced truth table

* =undesirable situation


S	R	Q(t+1)	/Q(t+1)
0	0	Q(t)	/Q(t)
0	1	0	1
1	0	1	0
1	1	0*	0*

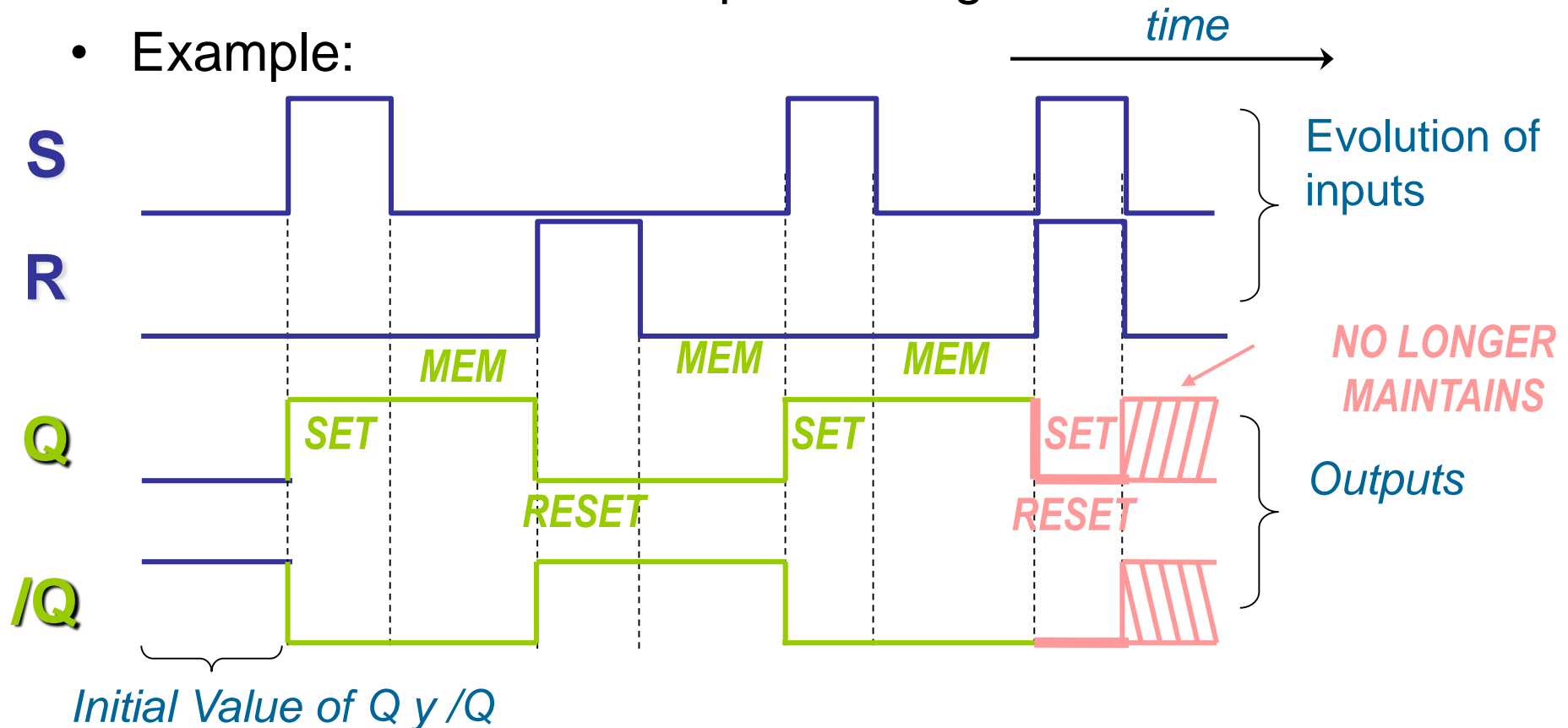- The timing diagram is used to determine the temporal evolution of the state when their inputs change
- Example:



- Used to implement memory elements, whose purpose is to store one bit of information

Symbol

 

Truth table

C	D	$Q(t+1)$	$/Q(t+1)$
0	X	$Q(t)$	$/Q(t)$
1	1	1	0
1	0	0	1


- We can build a D Latch from a SR Latch.

C	D	Q(t+1)	/Q(t+1)	R	S
0	X	Q(t)	/Q(t)	0	0
1	1	1	0	0	1
1	0	0	1	1	0


- The state is maintained when $C = 0$ ($R = S = 0$)
- $Q(t+1)=1$ if $C=1$ and $D=1$ ($R=0$ y $S=1$)
- $Q(t+1)=0$ if $C=1$ and $D=0$ ($R=1$ y $S=0$)

$$R=CD$$
$$S=C\overline{D}$$

 - One possible implementation of the D Latch:




 - Another possible implementation of the D Latch:



- A pair of synchronous-bistables can be used to implement an edge-triggered bistable
- The configuration is known as master / slave


Symbol

 

Truth table


CLK	D	Q(t+1)	/Q(t+1)
0	X	Q(t)	/Q(t)
1	X	Q(t)	/Q(t)
↓	1	1	0
↓	0	0	1

Master/Slave Configuration

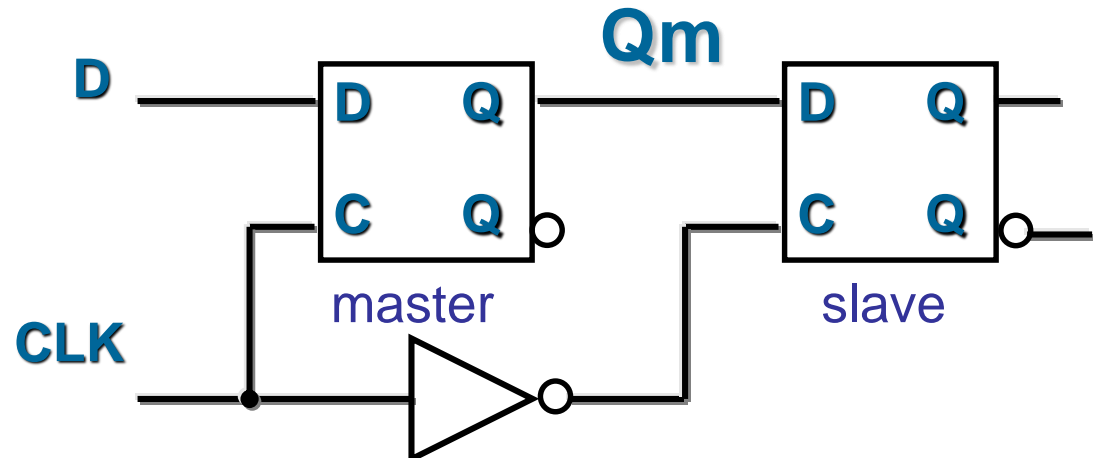

D Flip-Flop falling-edge triggered


FCO

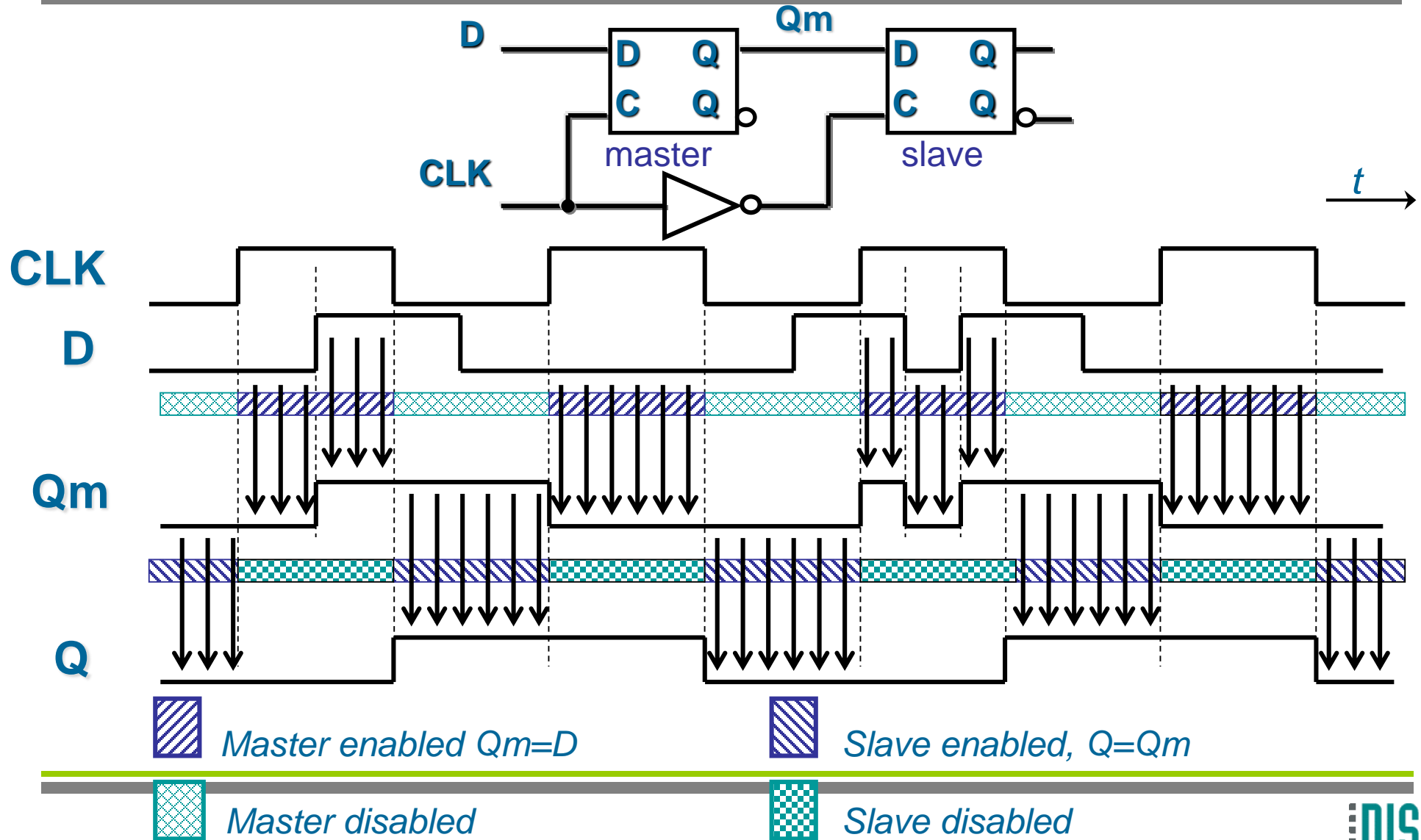

D Flip-Flop falling-edge triggered

FCO

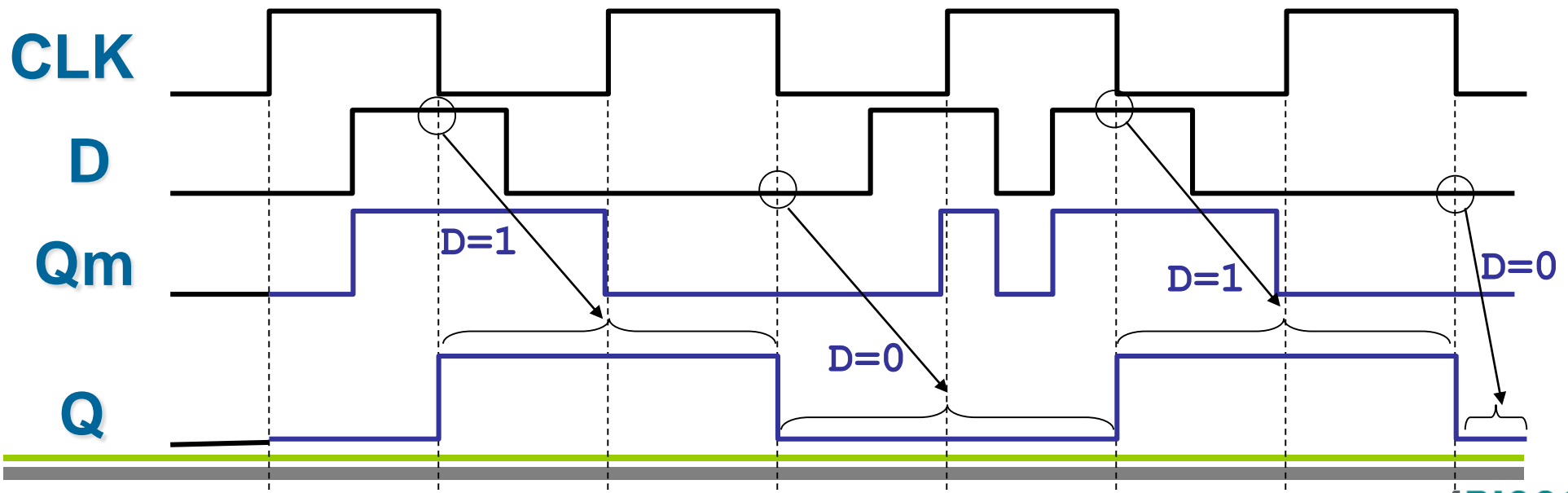
- Note:
 - Qm Signal changes when CLK = 1, following the evolution of the input D.
 - Q output only changes with the falling-edges of CLK-signal




D Flip-Flop rising-edge triggered

FCO

Symbol

 


Implementation

 


Truth table

CLK	D	Q(t+1)	/Q(t+1)
0	X	Q(t)	/Q(t)
1	X	Q(t)	/Q(t)
↑	1	1	0
↑	0	0	1

 - D Flip-Flop with asynchronous inputs for clear and reset operations
 - /CLEAR
 - /PRESET
- Asynchronous inputs have more priority than clock–input



 

- $/\text{CLEAR} = / \text{PRESET} = 1 \Rightarrow Q = Q', /Q = /Q'$
- $/\text{CLEAR} = 0, / \text{PRESET} = 1 \Rightarrow Q = 0, /Q' = 1, /Q = 1$
- $/\text{CLEAR} = 1, / \text{PRESET} = 0 \Rightarrow /Q = 0, Q' = 1, Q = 1$
- $/\text{CLEAR} = 0, / \text{PRESET} = 0 \Rightarrow Q = /Q = 0^*, Q' = /Q' = 1^*$

D Latch with asynchronous inputs


FCO

- Truth table

/PR	/CL	C	D	Q(t+1)	/Q(t+1)
0	1	X	X	1	0
1	0	X	X	0	1
0	0	X	X	0*	0*
1	1	1	1	1	0
1	1	1	0	0	1
1	1	0	X	Q(t)	/Q(t)

D Latch


FCO

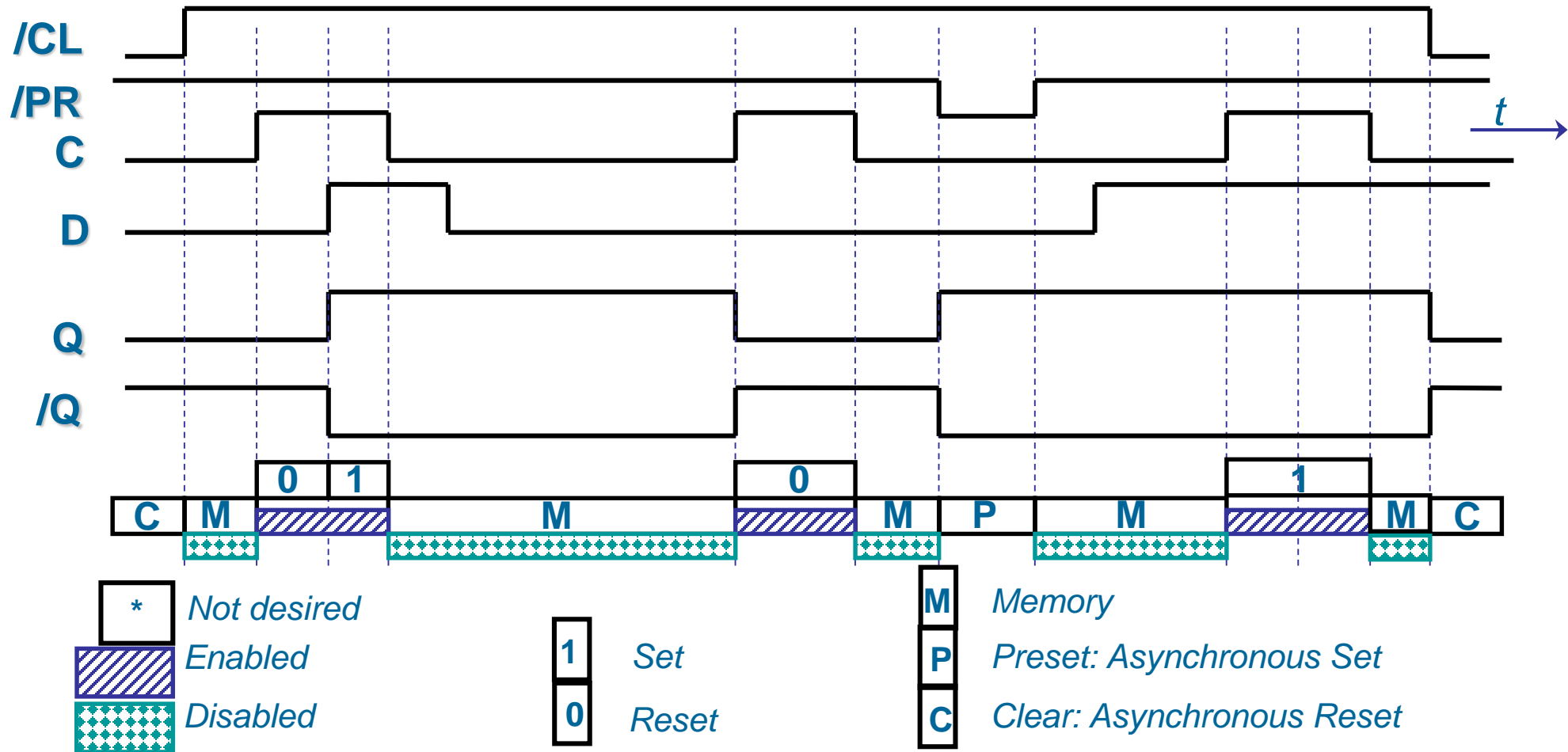

Commercial IC 74175

FCO

 - Integrated circuit 74175
- 4 flip-flops rising-edge triggered with asynchronous inputs for set and reset



Function Table

(Each Flip-Flop)

Inputs			Outputs	
Clear	Clock	D	Q	$\bar{Q} \uparrow$
L	X	X	L	H
H	\uparrow	H	H	L
H	\uparrow	L	L	H
H	L	X	Q_0	\bar{Q}_0


H = HIGH Level (steady state)

L = LOW Level (steady state)

X = Don't Care

\uparrow = Transition from LOW-to-HIGH level

 
Q_0 = The level of Q before the indicated steady-state input conditions were established.




- The SR latch has problems when inputs S and R are activated at the same time
- Solution: design a flip-flop to avoid that problem. The behavior should be as follows
 - Input J (Set operation); when activated and there is a rising edge on CLK $Q(t+1) = 1$
 - Input K (Reset operation) ; When activated and there is a rising edge on CLK $Q(t+1) = 0$
 - When inputs J and K are not activated the state must be maintained: $Q(t+1) = Q(t)$
 - When inputs J and K are activated and there is a rising edge on CLK (Toggle Op.): $Q(t+1) = /Q(t)$

CLK	J	K	$Q(t+1)$	$/Q(t+1)$
0	X	X	$Q(t)$	$/Q(t)$
1	X	X	$Q(t)$	$/Q(t)$
↑	0	0	$Q(t)$	$/Q(t)$
↑	0	1	0	1
↑	1	0	1	0
↑	1	1	$/Q(t)$	$Q(t)$

Truth table

 


Symbol

 

Logic diagram

- It has two inputs: T-input (*toggle*) and clock-input
- Memory (if $T=0$) or Toggle (if $T=1$) each time there is a clock-edge (in this case rising-edge)
- It is not commercialized, but it can be implemented from a D-Flip-Flop or from a JK Flip-flop


Symbol

 

Thruth table

T	Q(t)	D
0	0	0
0	1	1
1	0	1
1	1	0

Logic diagram

 

It is possible to build a T flip-flop falling-edge triggered in a similar way



UNIVERSIDAD
POLITECNICA
DE VALENCIA



Computers Fundamentals

Subject 4. Sequential Circuits
