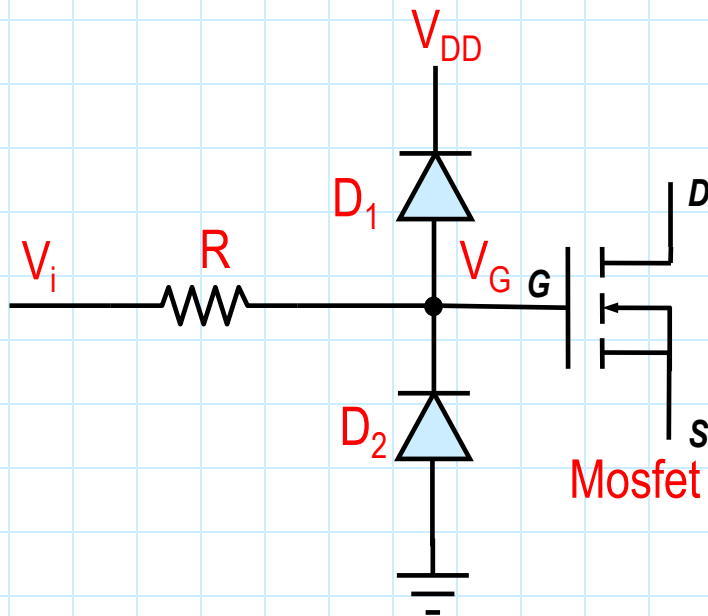


# 1.3 Diode circuits. Digital inputs protection


- **Clipping diodes:** protect the Mosfet inputs of CMOS digital circuits against overvoltages.



- $D_1$  conducts if  $V_i > V_{DD} + 0.7V$
- $D_2$  conducts if  $V_i < -0.7V$
- $-0.7V \leq V_G \leq V_{DD} + 0.7V$


# 1.3. Diode circuits. Digital applications

AND Gate

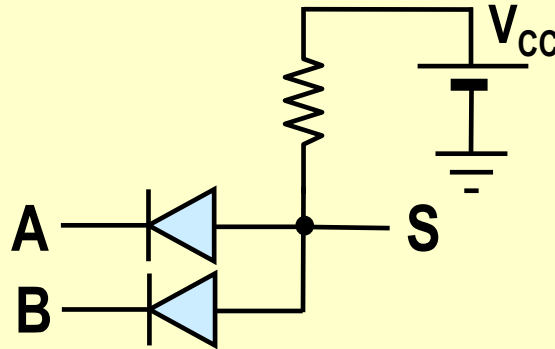

A	B	S
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

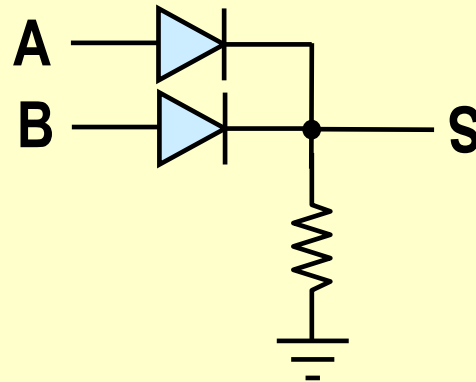


A	B	S
0	0	0
0	1	1
1	0	1
1	1	1

AND

• Case  $A=B=1$  ;  $V_A=V_B=V_{CC}$

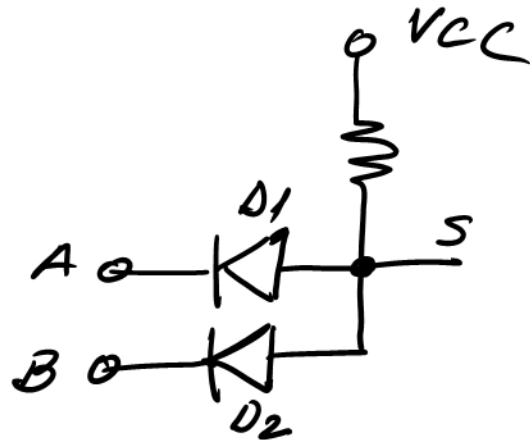

$D_1$  OFF,  $D_2$  OFF (Reverse biased)

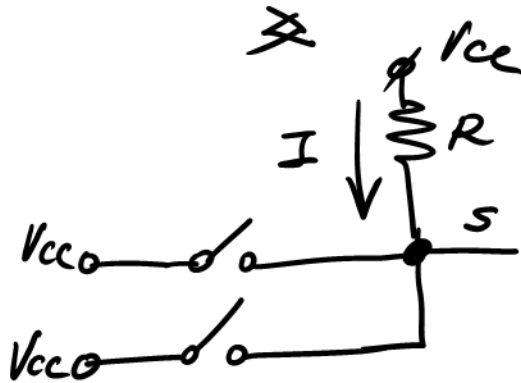


$$I=0 \Rightarrow V_S = V_{CC} - IR = V_{CC}$$


Then

$$\left. \begin{array}{l} A=1 \\ B=1 \end{array} \right\} S=1$$

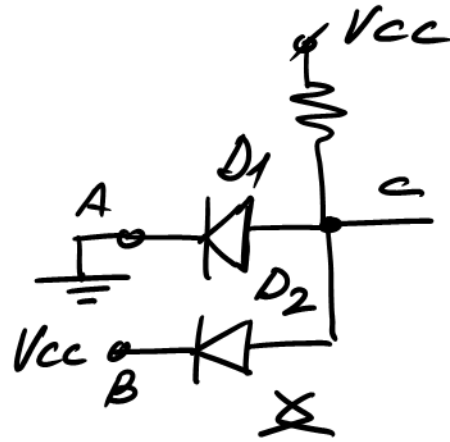AND Case •  $A=0, B=1; V_A=0V; V_B=V_{CC}$



$D_1$  ON  
 $D_2$  OFF

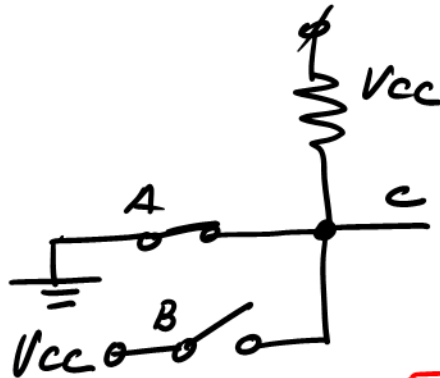


$V_C = 0V \Rightarrow C = 0$

Then


$\left. \begin{matrix} A=0 \\ B=1 \end{matrix} \right\} C=0$ , on the same way:

• Case  $A=1, B=0 \rightarrow \left. \begin{matrix} A=1 \\ B=0 \end{matrix} \right\} C=0$  (simmetry  $A \rightleftharpoons B$ )

AND • Case  $A=B=0$  ;  $V_A=V_B=0V$

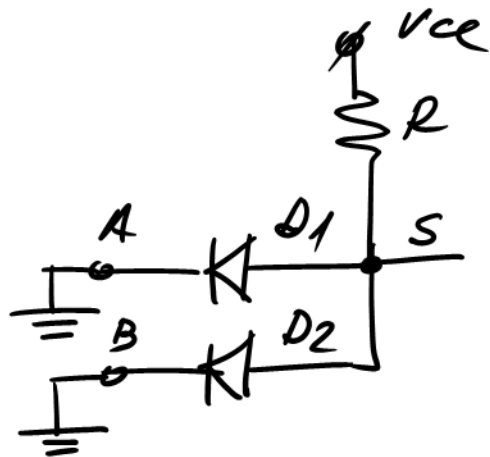

$D_1$  ON  
 $D_2$  ON  $\nrightarrow$

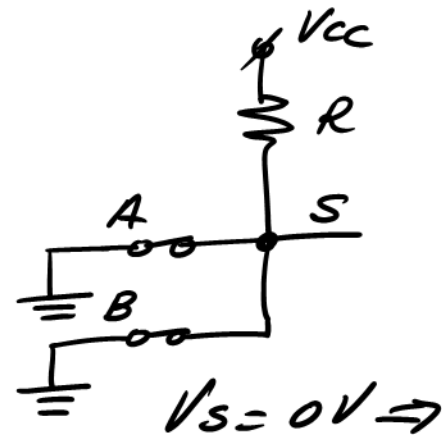


$$\left. \begin{matrix} A=0 \\ B=0 \end{matrix} \right\} S=0$$

Summary:


A	B	S
0	0	0
0	1	0
1	0	0
1	1	1

$\Rightarrow$


$$S = A \cdot B \text{ (AND)}$$

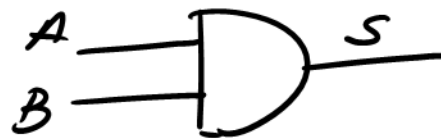

OR gate

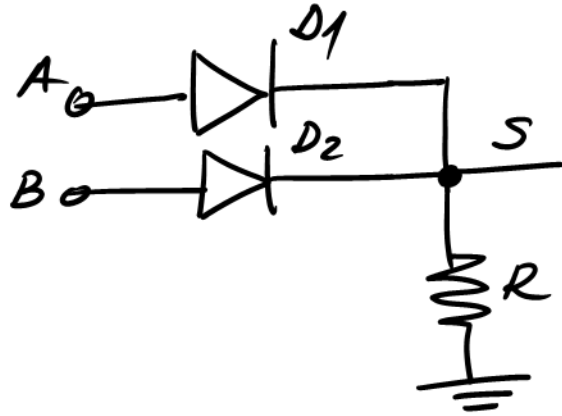

A	B	$D_1$	$D_2$	$V_S$	S
0	0	OFF	OFF	0	0
0	1	OFF	ON	$V_{CC}$	1
1	0	ON	OFF	$V_{CC}$	1
1	1	ON	ON	$V_{CC}$	1

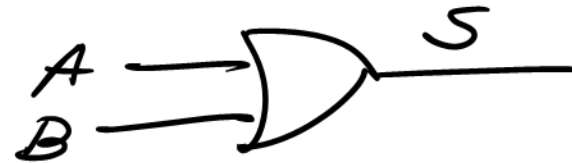

$$S = A + B$$

# 1.3 Other applications in digital circuits

As we will see throughout the course, diodes are present in almost all digital integrated circuits:

- Digital gates based on bipolar transistors (ex: TTL) use diodes for adjusting the voltage levels.
- Each MOS transistor inside NMOS or CMOS digital circuits have implicitly several diodes in reverse mode.

*→ NMOS transistors*


*CMOS { NMOS } transistors*  
*{ PMOS }*

# 1.4 Special purpose diodes.


## Schottky diodes

- Special diodes for switching circuits
- Based on a metal (Al)-semiconductor ("n" not many doped) junction (\*)
- High  $I_s$  (1000 times bigger)
- Low  $V_\gamma$  (0,4V approx.)
- Very fast switching
- Application to high-speed digital circuits


Symbol:

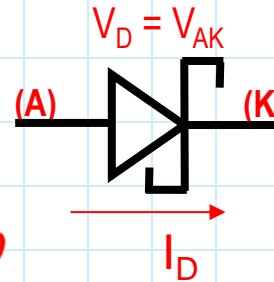

Characteristic curve

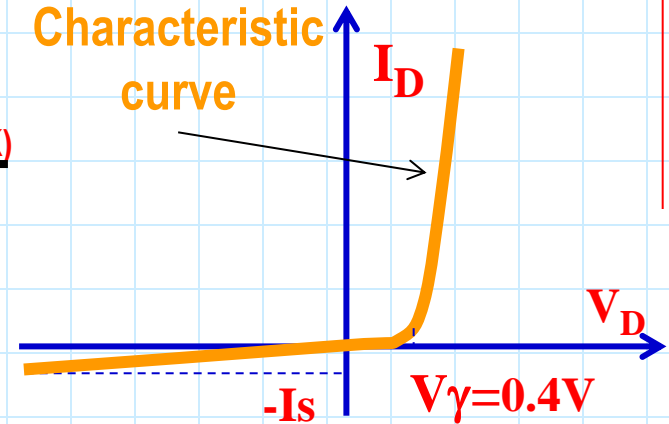


Example: 74LS00  
4 \* NAND 2E

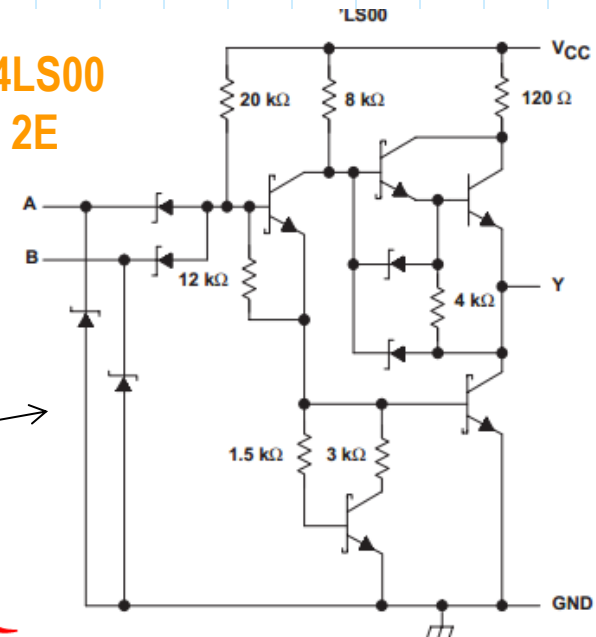

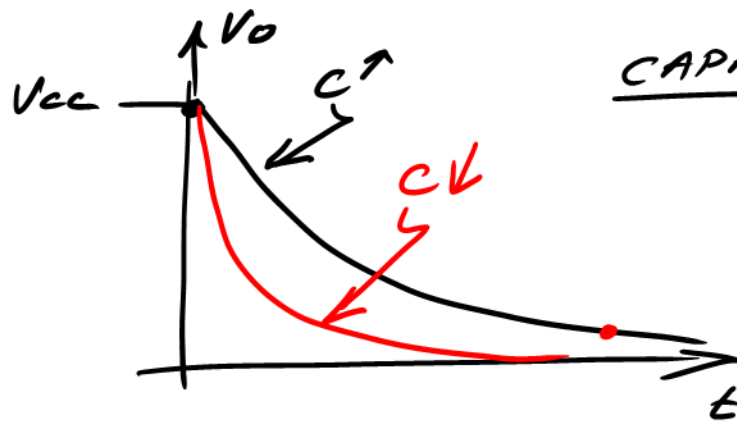
*This junction minimizes parasitic capacitance  $\Rightarrow$  less  $C \Rightarrow$  More speed*





## CAPACITOR DISCHARGE

$$V_o = V_{cc} e^{-t/RC}$$

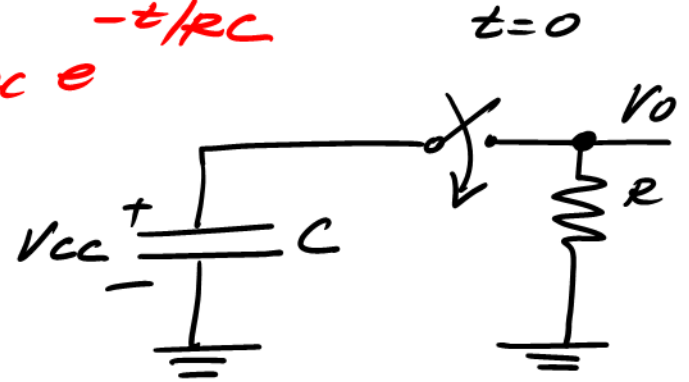

$RC \rightarrow$  Timing constant

$C \uparrow \rightarrow R \uparrow \Rightarrow$  More delay  $\Rightarrow$  less speed


Shottky:  $C \downarrow \Rightarrow R \downarrow \Rightarrow$  Less delay  $\Rightarrow$  More speed

$C$ : Parasitic capacitance

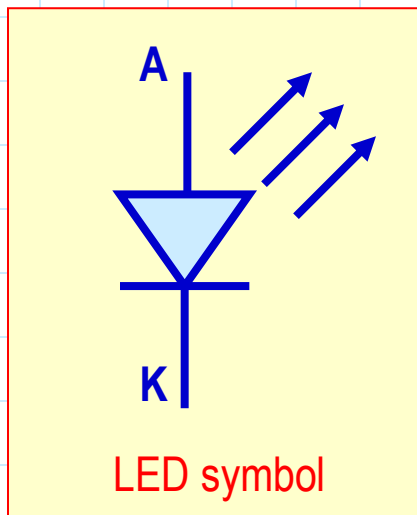
# 1.4 Special purpose diodes. LED

*light*  $\leftarrow$   $e^-$   $E_1$   $h \rightarrow$  Plank constant  
 $E_2$   $f \rightarrow$  freq.  
 $E_1 - E_2 = h \cdot f$  ELECTROLUMINESCENCE

- LED: Light Emitting Diode
- When diode is forward-biased, majority carriers are injected in the P-N junction. The carriers recombine in order to restore the equilibrium, emitting energy in the form of heat or light.
- This last case (light emitting) is produced only in the case of special semiconductor materials: GaAs, GaAsP, SiC, ...




*infrared*

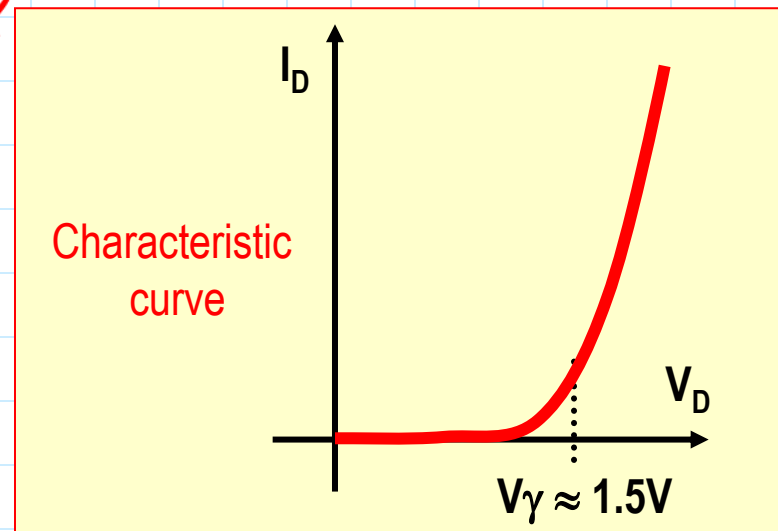


# 1.4 LED features

*Infrared, Red --- Blue, Ultraviolet*

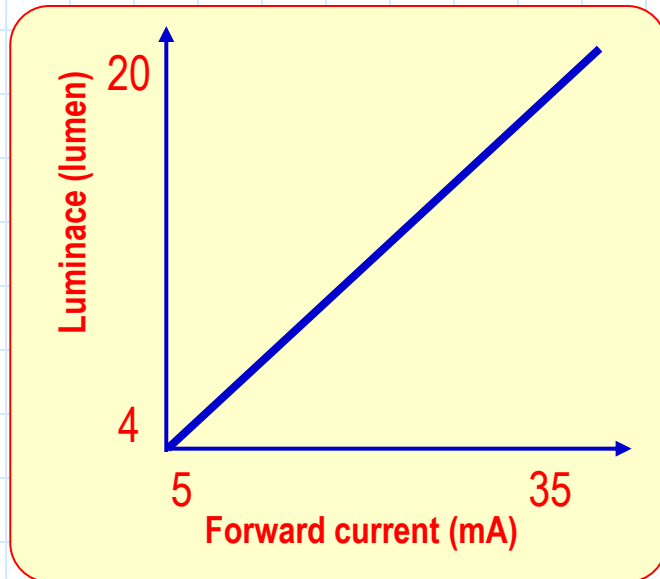

- $V_f$  is among **1.5V to 4V**
- The emitted luminance is directly proportional to the forward current
  - ◆ (for a good visibility, a forward current from **10 to 20mA** is required)
  - ◆ The modern high power LEDs (1 W or more), require more current (\*)
- The radiation is almost monochrome (only one color)
- Radiation frequency of LEDs:
  - ☞ Infrared (with a lot of applications)
  - ☞ Red (the most typical)
  - ☞ Yellow
  - ☞ Green
  - ☞ Blue
  - ☞ Ultraviolet

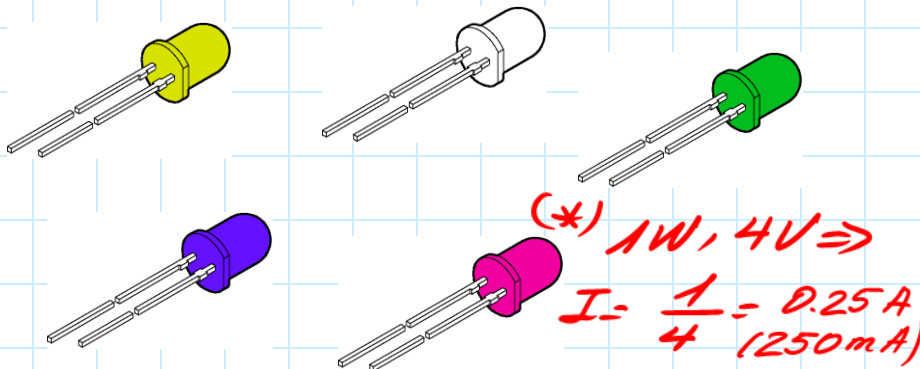

} The latest ones

# 1.4 Blue LED

- In 2014 the **Nobel Prize in Physics** was delivered to the discoverers of **blue** LED : Akasaki, Amano and Nakamura.
- To produce white light, blue LED was missing for many years:
  - White light with 3 LEDs: red, green and blue (RGB)
  - White light with one blue LED+ optical filter of Phosphorus
- After several failed attempts, in 1994 they first obtained a "high" efficiency blue LED (for that time).
- They used a semiconductor based on InGaN / AlGaIn, and obtained an efficiency of about 2.7% (incandescent bulbs have an efficiency of a 4%).
- Now we have more efficiency:

*Red, green: already invented*

*~50%*

*5W led ≈  
50W halogen  
(1/10 reduction  
on power  
consumption)*

