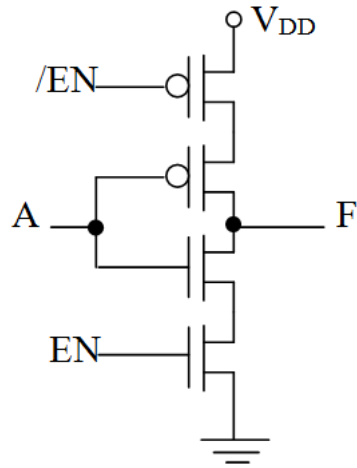


## UNIT 4. CMOS

3.1. The CMOS circuit of figure is:




$$\begin{aligned} EN = 1 &\Rightarrow /EN = 0 \Rightarrow F = \bar{A} \\ EN = 0 &\Rightarrow /EN = 1 \Rightarrow F = \text{"Z"} \end{aligned}$$

- A) An inverter
- ☒ B) A tri-state inverter
- C) A tri-state buffer
- D) An open-drain buffer

# UNIT 4. CMOS

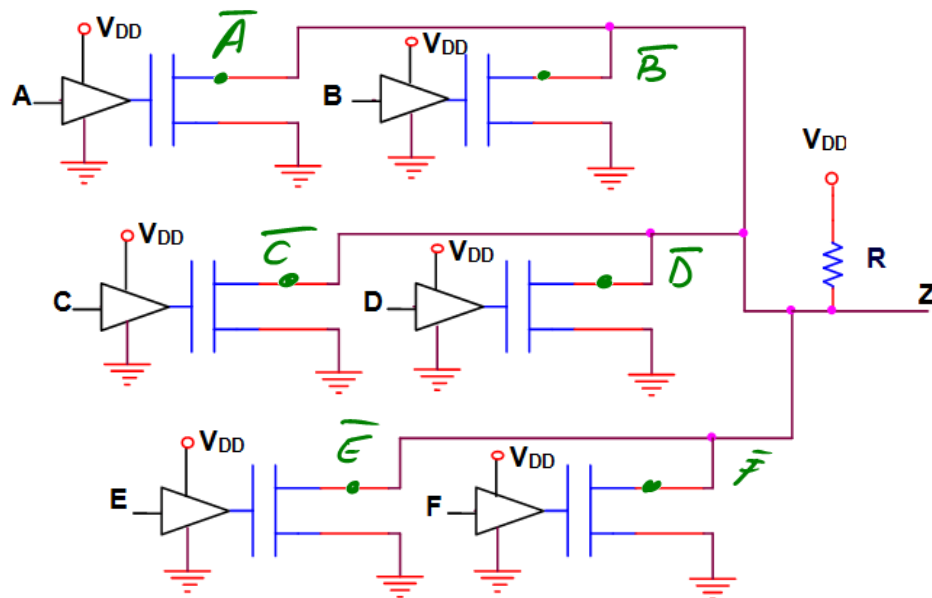3.2. Indicate the logical expression of the wired function Z. The gates have an open-drain output. Suppose that R is a pull-up resistor of appropriate value.


- [A]  $Z = A + B + C + D + E + F$
- [B]  $Z = \overline{A + B + C + D + E + F}$**
- [C]  $Z = (A + B).(C + D).(E + F)$
- [D]  $Z = A.B.C.D.E.F$



$$Z = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E} \cdot \overline{F} = \overline{A \cdot B \cdot C \cdot D \cdot E \cdot F} = \overline{A + B + C + D + E + F}$$

## UNIT 4. CMOS

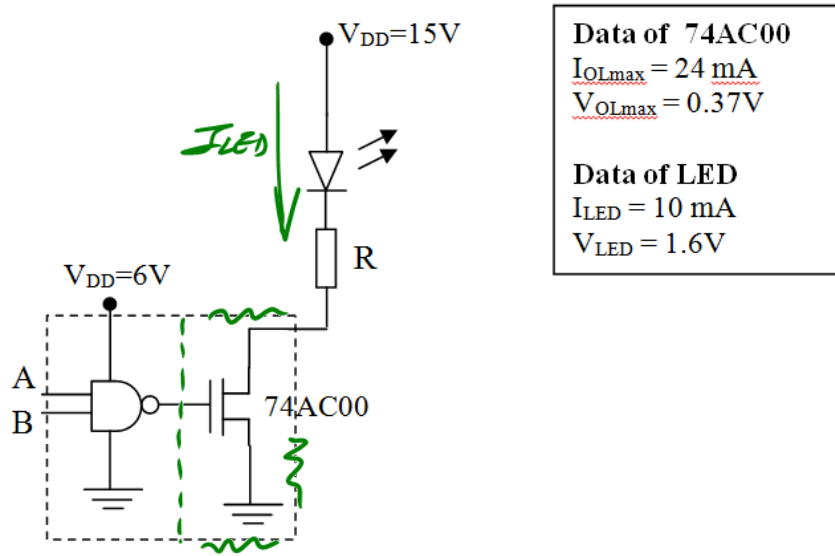3.3. The following Figure shows the control circuit of a LED with a NAND gate with open-drain output. 74AC gates have been used for this purpose, as they provide enough current to the LED (74HC gates have a maximum output current of only 4 mA). Design the appropriate value of resistor R so that the LED lights properly.



$$I_{LED} = 10 \text{ mA}$$

$$R = \frac{V_{DD} - V_{OLmax} - V_{LED}}{I_{LED}}$$

$$R = \frac{15 - 0.37 - 1.6}{10} = \underline{\underline{1.3 \text{ K}}}$$

- A)  $R = 130\Omega$
- B)  $R = 3k3$
- ☒ C)  $R = 1.3K\Omega$
- D) None of the previous answers is correct