

CH1. BASIC SEMICONDUCTOR DEVICES


20. Choose the statement **TRUE** among the following statements related to bipolar transistors:

[A] The transistor is the union of two diodes in opposition. ✗

[B] It is a symmetric three-terminal device, because you can swap the collector and emitter terminals. ✗

[C] The base terminal is serving as the control terminal. ✓

[A]

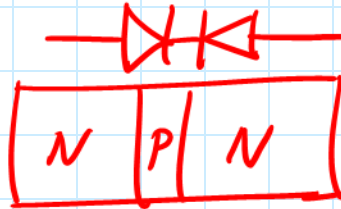

Two diodes in opposition don't amplify. We need a narrow base and special configuration for do so.

[B]

Changing $E \leftrightarrow C$ transistor enters in reverse active mode, and don't amplify.

CH1. BASIC SEMICONDUCTOR DEVICES

21. In the circuit with transistor of figure, and taking into account the following data, what will be the operating (quiescent) point of transistor?


DATA: $V_{BE(ON)}=0.7V$, $V_1=2.7V$, $R_1=200k$, $\beta=500$


- [A] ($V_{CE}=1.25V$, $I_C=15mA$)
- [B] ($V_{CE}=2.5V$, $I_C=10mA$)
- [C] ($V_{CE}=3.75V$, $I_C=5mA$)**
- [D] ($V_{CE}=2.5V$, $I_C=10mA$)

• From curves: $V_{CC}=5V$
 $V_{CC}/R_2=20mA$
 $\Rightarrow R_2=0.25k$

• As $V_1 > V_{BE(ON)} \Rightarrow T$ is ON

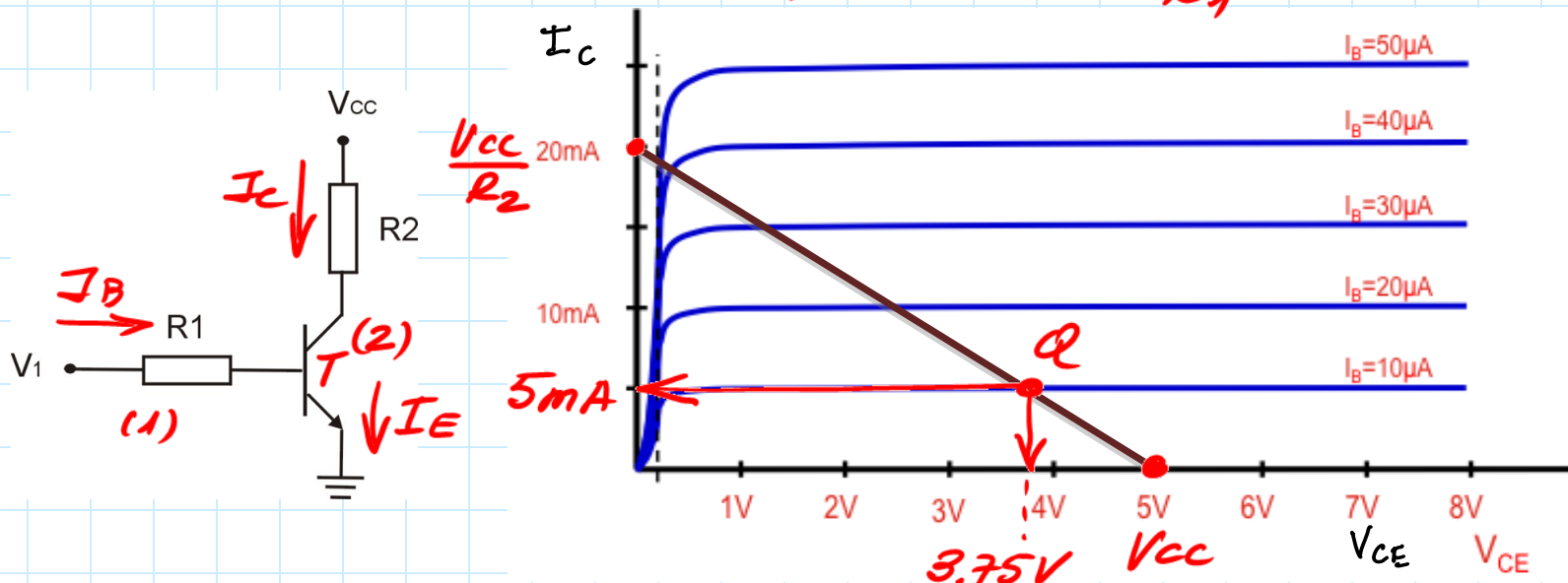• Input loop (1) } $I_B = \frac{V_1 - V_{BE(ON)}}{R_1} = 10\mu A$



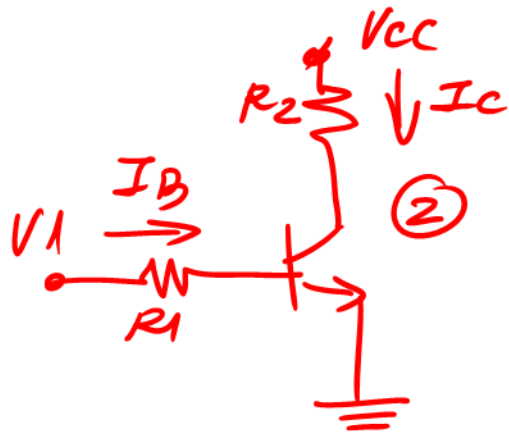

Output loop:

Assuming active region:

$$I_C = \beta I_B = \underline{5 \text{ mA}}$$

$$V_{CE} = V_{CC} - R_2 I_C = 5 - 0.25 \cdot 5 = 3.75 \text{ V.}$$

As $V_{CE} > V_{CE(\text{SAT})} = 0.2 \text{ V} \Rightarrow T$ is in active region \Rightarrow



$$Q (I_B = 10 \mu\text{A}; I_C = 5 \text{ mA}; V_{CE} = 3.75 \text{ V})$$

- We can also solve this exercise in a graphical form (see previous page)

CH1. BASIC SEMICONDUCTOR DEVICES

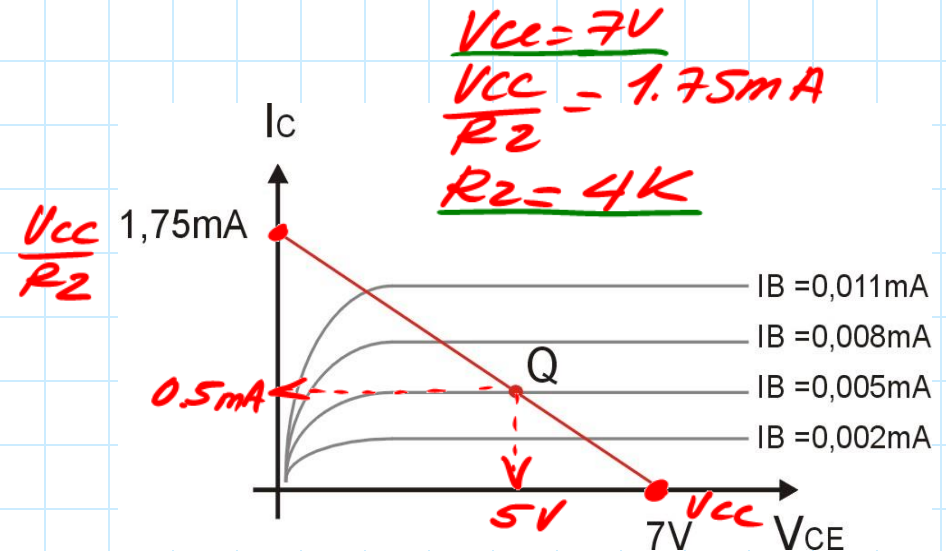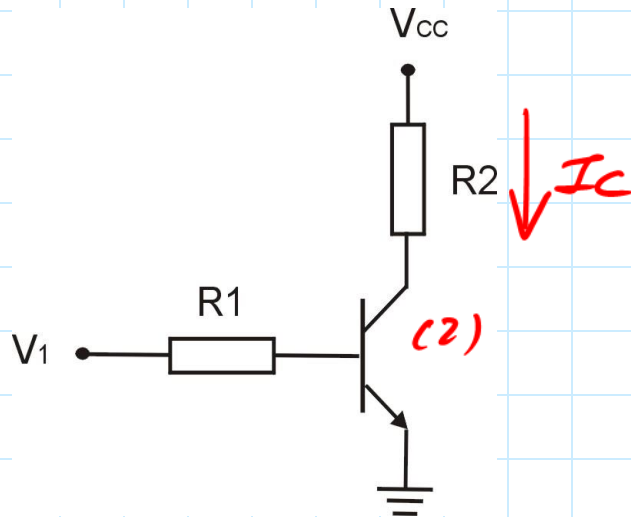(22) Given the following circuit, the corresponding load line, operating point Q and characteristic curves of the transistor, which of the following statements is correct?

DATA: $V_{CESAT} = 0,2V$; $V_{BEON} = 0,7V$ y $\beta=100$ (I_B is not negligible).





- [A]. The transistor is saturated. X
- [B]. The I_C of transistor is 1,75mA. X
- ☒ [C]. The V_{CE} of transistor is 5V.
- [D]. The value of R_2 is 3K. X

$$\begin{aligned} I_B &= 0,005mA \\ \text{active region} \end{aligned} \left\{ \begin{aligned} I_C &= \beta I_B = 0,5mA \\ (2) V_{CE} &= V_{CC} - I_C R_2 = 7 - 0,5 \cdot 4 = 5V \end{aligned} \right.$$

CH1. BASIC SEMICONDUCTOR DEVICES

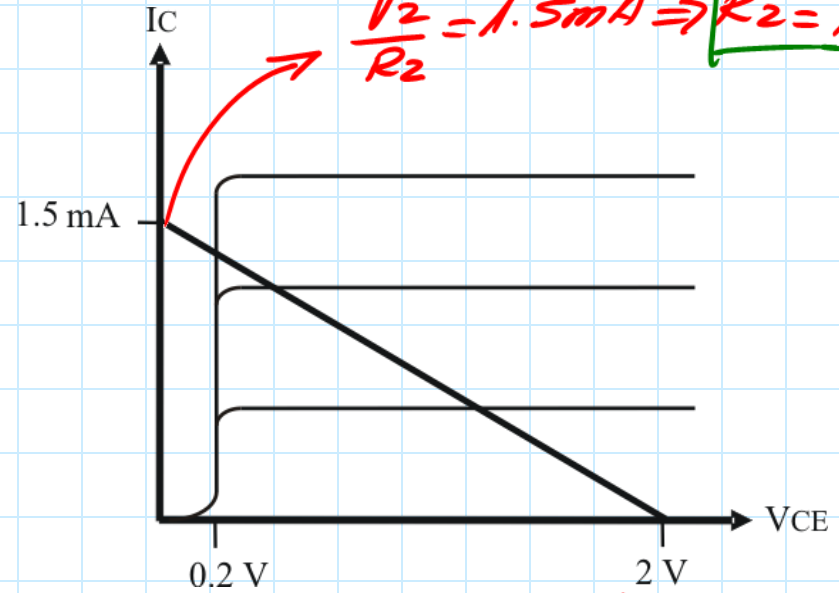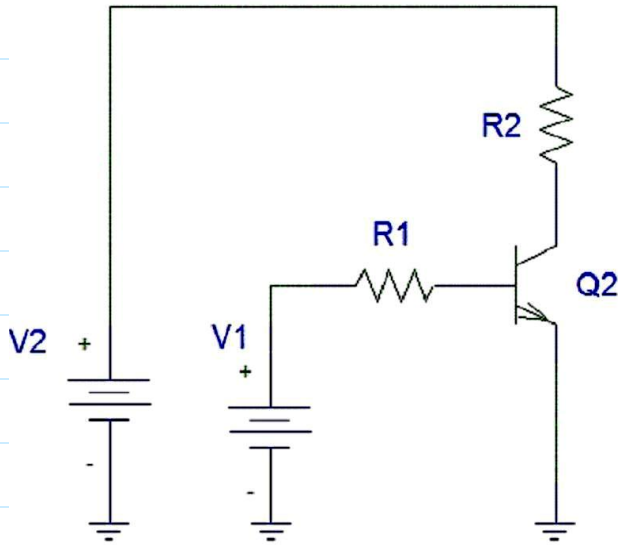23. Indicate, using the attached figures, the value of resistance R_2 . (Data: $\beta = 100$, $V_{CE(SAT)} = 0.2V$; $V_{BE(ON)} = 0.7V$; $V_1 = 6V$; $R_1 = 100k\Omega$)



- [A] 1,33 $k\Omega$
- [B] 1,2 $k\Omega$
- [C] 0,87 $k\Omega$
- [D] Some data are missing.


CH1. BASIC SEMICONDUCTOR DEVICES

29. In a circuit based on a NPN bipolar transistor whose current gain β is 100, the following currents and DC voltages are measured:

$V_{BE} = 0.7V$	$I_B = 0.1mA$	$I_E = 3.5mA$
-----------------	---------------	---------------

Taking into account these data, we can state that:

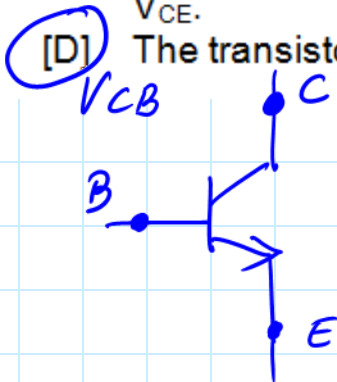- [A] The transistor is in cut-off mode.
- [B] The transistor is in active region.
- [C] The operating region cannot be known, because it is not known the value of V_{CE} .
- [D] The transistor is saturated.



$$V_{BE} = V_{BE_{ON}} \Rightarrow T \text{ is ON}$$

$$I_E = I_B + I_C \Rightarrow I_C = I_E - I_B = 3.4mA$$


$$\frac{I_C}{\beta} = 0.034mA$$

$$\text{As } I_B = 0.1mA > \frac{I_C}{\beta} = 0.034mA \Rightarrow T \text{ is SATURATED}$$

CH1. BASIC SEMICONDUCTOR DEVICES

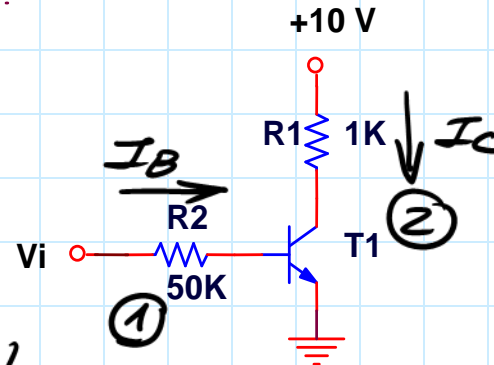30. Given the circuit of the figure, where $V_{BE(ON)} = 0.7V$, $V_{CE(SAT)}$ and $\beta = 100$; indicate the operating region of the transistor for:

- [A] $V_i = 0.7V$
- [B] $V_i = 4V$
- [C] $V_i = 6.7V$



A) As $V_i = V_{BE(ON)}$
$$I_B = \frac{V_i - V_{BE(ON)}}{R_2} = 0mA$$
 } Then T_1 is in CUT-OFF reg.
but in the limit to ACTIVE $Q(I_B=0, I_E=0, V_{CE}=10V)$

B) $V_i > V_{BE(ON)} \Rightarrow T_1$ is ON


①
$$I_B = \frac{V_i - V_{BE(ON)}}{R_2} = \frac{4 - 0.7}{50K} = 0.066mA$$

Assuming active region:

$$I_C = \beta I_B = 6.6mA$$

②
$$V_{CE} = V_{CC} - R_1 I_C = 10 - 1 \cdot 6.6 = 3.4V$$

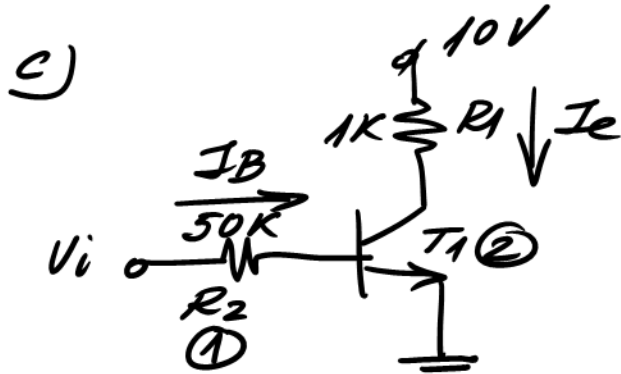As $V_{CE} > V_{CE(SAT)} \Rightarrow T_1$ is in ACTIVE region
 $Q(I_B = 0.066 \text{ mA}; I_C = 6.6 \text{ mA}; V_{CE} = 3.4 \text{ V})$



$V_i > V_{BE(ON)} \Rightarrow T_1 \text{ ON}$

$$\textcircled{1} I_B = \frac{V_i - 0.7}{R_2} = \frac{6}{50\text{K}} = \underline{0.12 \text{ mA}}$$

Assuming ACTIVE region:

$$I_C = \beta I_B = 12 \text{ mA}$$

$\textcircled{2} V_{CE} = 10 - R_1 I_C = 10 - 12 = -2 \text{ V}$, then T_1 is not in active region, then is saturated

$$V_{CE} = V_{CE(SAT)} = \underline{0.2 \text{ V}} \Rightarrow \textcircled{2} I_C = \frac{10 - V_{CE(SAT)}}{R_1} = \frac{10 - 0.2}{1}$$

$$I_C = 9.8 \text{ mA}$$


$Q(I_B = 0.12 \text{ mA}, I_C = 9.8 \text{ mA}, V_{CE} = 0.2 \text{ V})$

CH1. BASIC SEMICONDUCTOR DEVICES

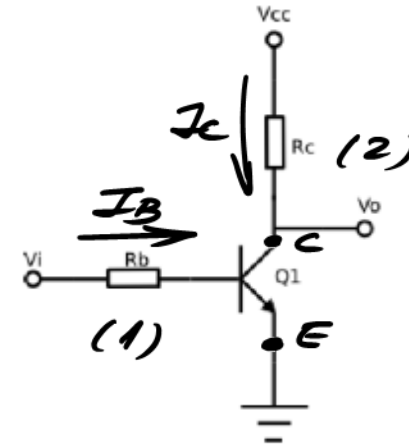27. Indicate the working region of transistor of figure for an input voltage V_i of 3.7 V:

(DATA: $V_{CC} = 5V$; $R_b = 100\text{ k}\Omega$; $R_c = 2\text{ k}\Omega$, Q1: $V_{BE(ON)} = 0.7V$, $V_{CE(SAT)} = 0.2V$, $\beta = 100$)

- [A] Cutt-off
- [B] Active
- [C] En el límite entre Active and Saturation regions.
- ☒ [D] Saturation



• As $V_i > V_{BE(ON)} \Rightarrow Q_1$ is ON

$$(1) I_B = \frac{V_i - V_{BE(ON)}}{R_b} = \frac{3.7 - 0.7}{100K} = 0.03\text{ mA}$$

• Assuming linear region:

$$I_C = \beta I_B = 3\text{ mA}$$

(2) $V_{CE} = V_{CC} - R_C I_C = 5 - 2 \cdot 3 = -1V$ (Impossible, then Q_1 is saturated $\Rightarrow V_{CE} = V_{CE(SAT)} = 0.2V$)

$$(2) I_C = I_{C(SAT)} = \frac{V_{CC} - V_{CE(SAT)}}{R_C} = \frac{5 - 0.2}{2K} = 2.4\text{ mA}$$

$Q_1 (I_B = 0.03\text{ mA}, I_C = 2.4\text{ mA}, V_{CE} = 0.2V)$ saturated