

Unit 3:

Introduction to integrated logic families

Objectives

At the end of this Unit, the student should:

- Understand the definition of the states of logic gates.
- Know and understand the behavior of input and output terminals of a logic circuit.
- Understand the characteristic parameters of a logic gate, both at electrical and temporal level.
- Understand the problem of interconnecting integrated logic circuits with different technologies, solving some case studies of interconnection.
- Know the different TTL subfamilies

Bibliography


1. M.H. Rashid. "Circuitos Microelectrónicos. Análisis y diseño" (2002). International Thomson. Capítulo 12.
2. A.R. Hambley. "Electrónica" (2ª ed., 2001). Prentice Hall. Capítulo 6.
3. R.H. Katz and Gaetano Borriello, "Contemporary Logic Design" (2nd ed., 2004). Prentice Hall.
4. J.F. Wakerly, "Digital Design. Principles and practices" (2006). Prentice Hall. Capítulo 3.
5. R. Tokheim. "Electrónica digital, principios y aplicaciones" (7ª ed., 2008). Mcgraw-hill.
6. A.P. Malvino. "Principios y aplicaciones digitales" (1988). Marcombo.

Contents

- 1. Introduction**
- 2. Types of outputs and inputs**
- 3. Characteristic parameters**
- 4. Interconnection of digital elements**
- 5. TTL family and subfamilies**

Introduction.




The logic gate

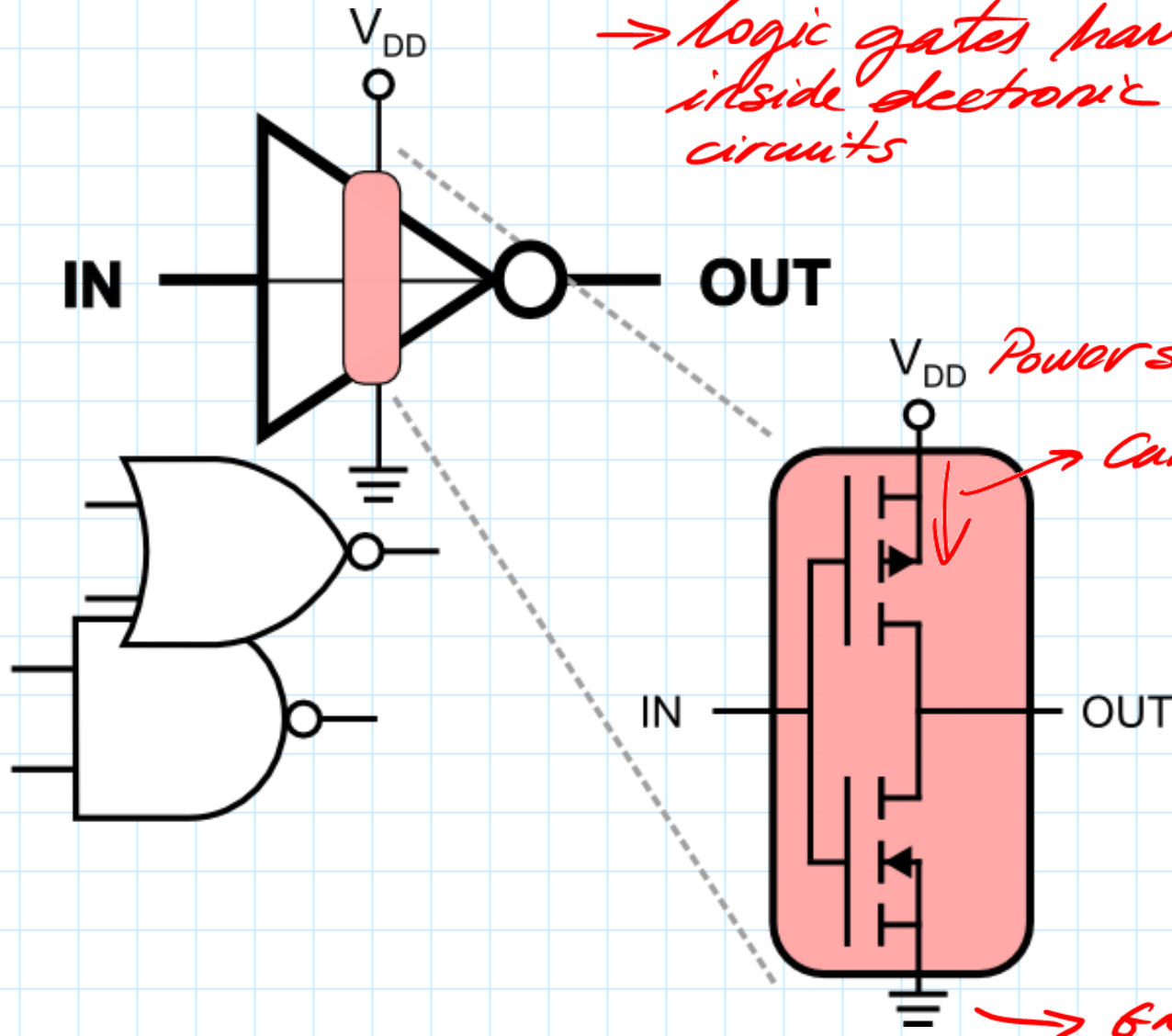


Introduction.

Abstraction of "0" and "1"

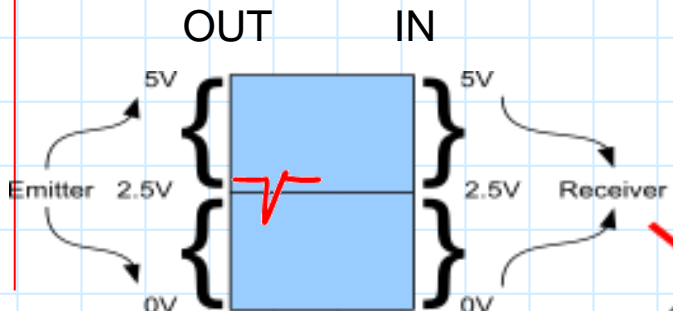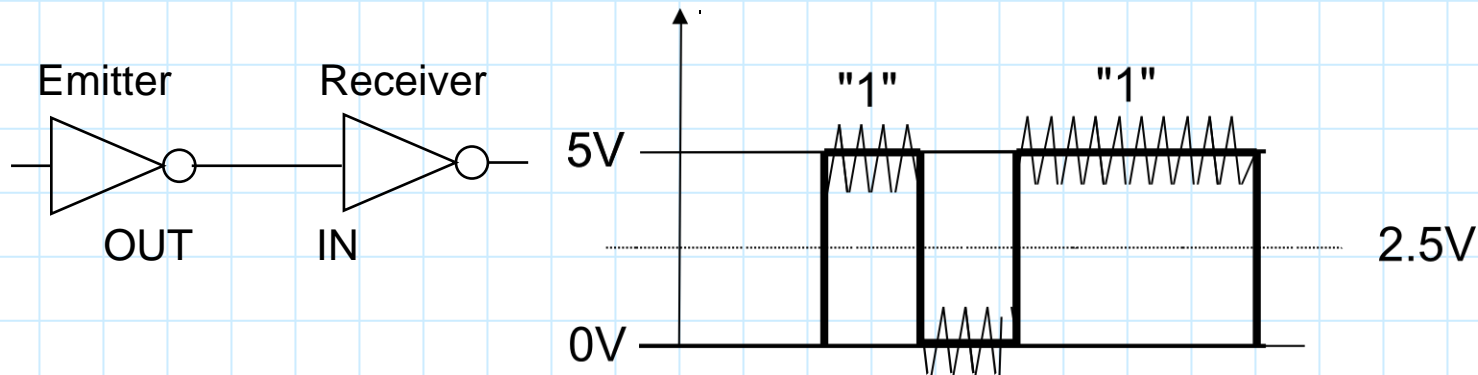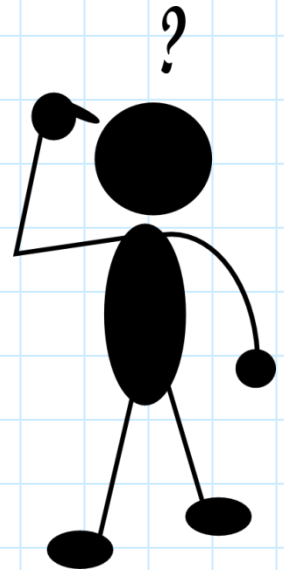
Logic levels "0" and "1" are not fixed voltage values, each one is associated with a different voltage range



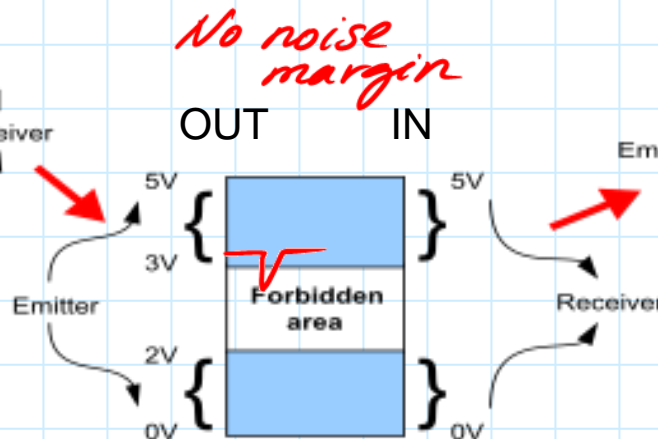*Easy to pass
from 1 → 0 (or 0 → 1)
if noise*



No noise margin

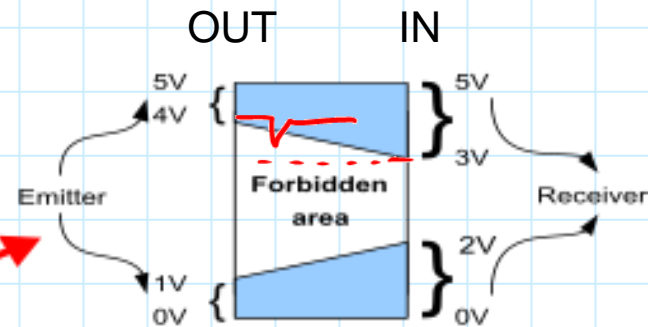

Noise margin

Introduction.

What is a logic family?

Logic family

- Set of functional elements (logic gates, biestables, decoders, counters, ...) with the same base circuit and the same manufacturing technology
- Electric compatibility, direct interconnection

all family members understand themselves

Main logic families

- Bipolar
 - Transistor Transistor Logic (**TTL**, **LSTTL**, STTL, ASTTL, ALSTTL, FAST)
 - Emitter Coupled Logic (ECL) *(old)*
- MOS
 - **PMOS, NMOS**
 - **CMOS**
 - **Pass-transistor CMOS**
 - Dynamic CMOS (Domino)
- BiCMOS (Bipolar- CMOS)
- Ga As (Gallium Arsenide)


Standard (old)

} CMOS: high integration density

*High Output Current
High Speed*

Introduction. Logic families evolution

Product Life Cycle

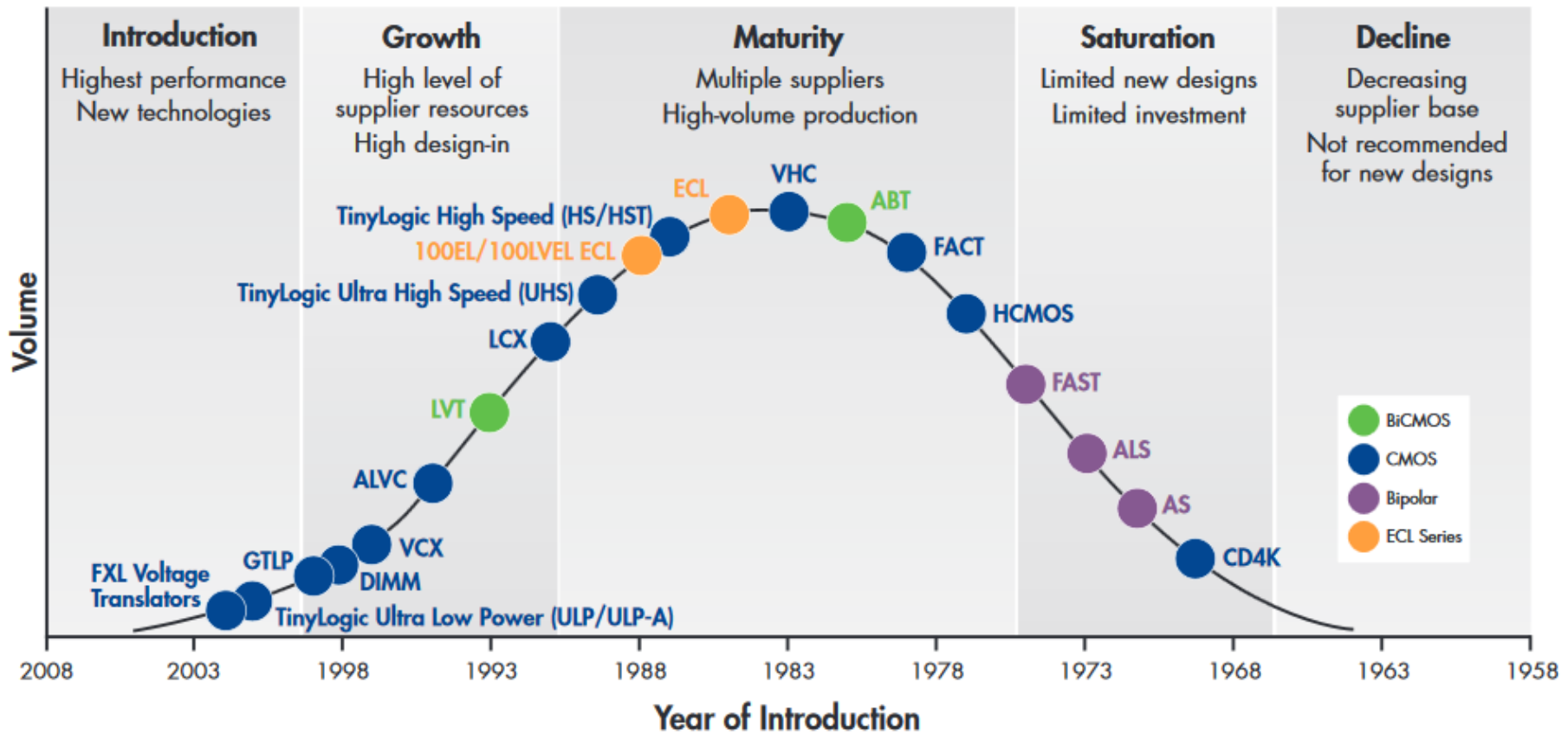

Source: <https://www.fairchildsemi.com/collateral/Logic-Selection-Guide.pdf> (2008)

Introduction.

Integration scales

SSI (Small Scale of Integration): up to 10 gates (*simple gates, flip-flops*)

MSI (Medium Scale of Integration): 10 to 100 gates (*decoders, multiplexers, adders, counters, registers, ...*)

LSI (Large Scale of Integration): 100 to 1000 gates (*microprocessors (8bits), memories, ...*)

VLSI (Very Large Scale of Integration): 1000 to 100000 gates (*memories, microprocessors and big PLDs*) *Normally, this is used today*

ULSI (Ultra Large Scale of Integration): more than 100K gates (*microprocessors (32+), FPGA, microcontrollers, SoC ...*)


GSI: (Giga Scale of Integration). More than 1M gates.

Today: 1 billion transistor / chip or more

Approx. Conversion Factor: For CMOS technology: 6 transistors/gate

Introduction Packages

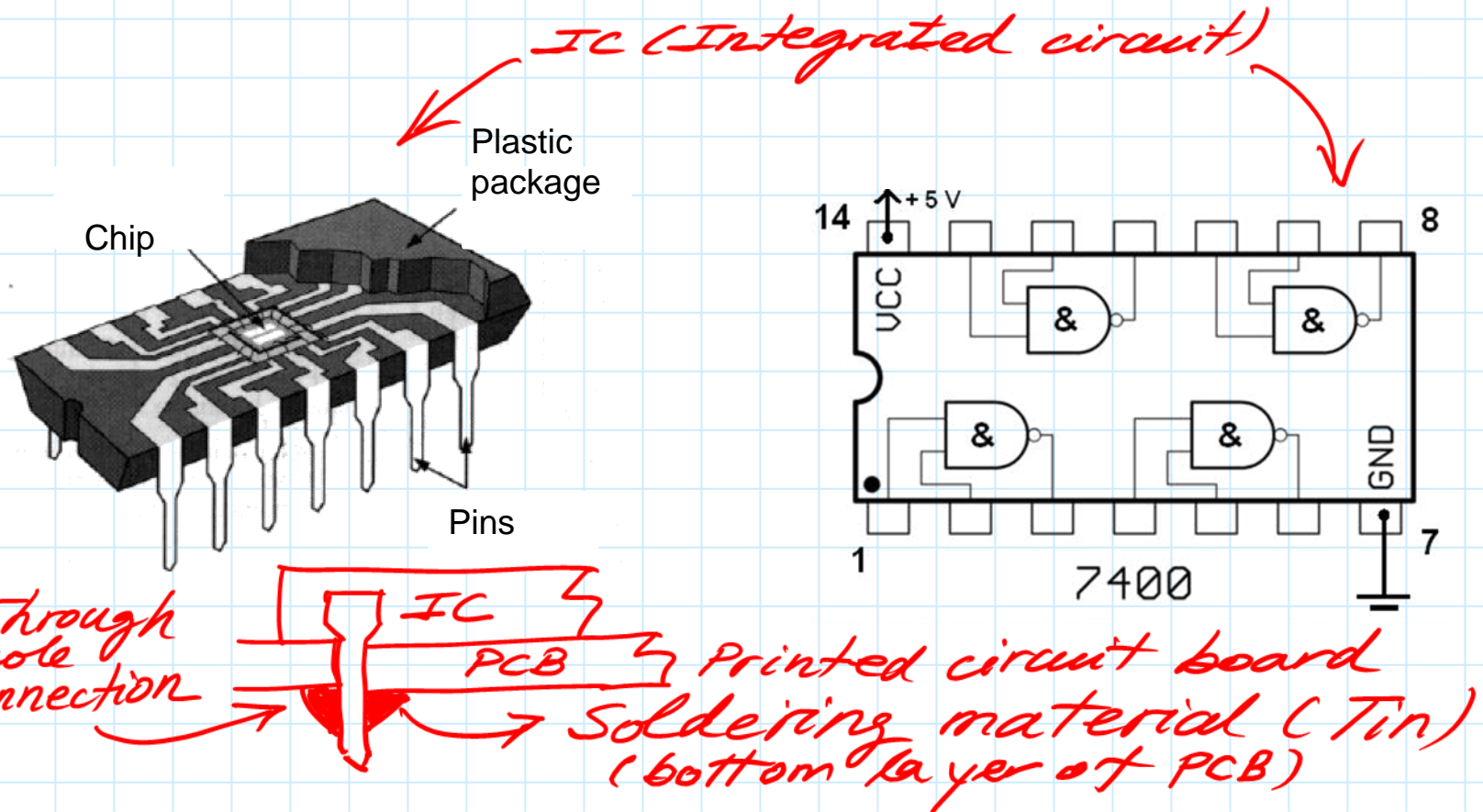To place the integrated circuit in an electronic system built on a printed circuit board (eg. a motherboard of a modern computer) is necessary to insert the chip in a protective shell called package.




Introduction Packages

→ Soldered in upper layer
SMD: Surface Mount Device

Packaging technology has followed a development parallel to the integration density

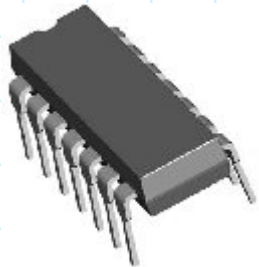*Dual-In-Line Package (DIP ó DIL)
(until 80 pins)*




*Plastic Leaded Chip Carrier (PLCC)
(until 84 pins)*



SMD

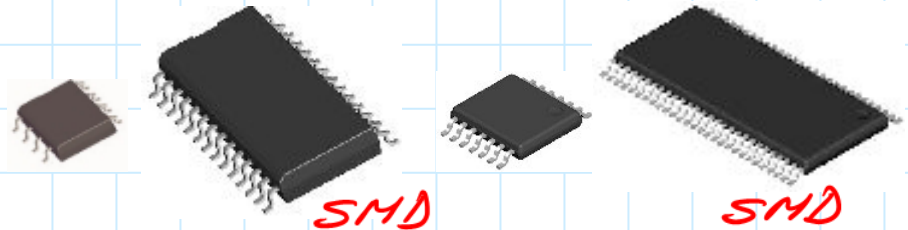
*Small Outline Integrated Circuit (SOIC) / Shrink
Small Outline Package (SSOP),
Thin Shrink Small Outline Package (TSSOP)*



SMD

SMD

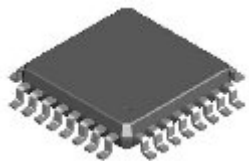*Quad Flat Pack (QFP)
Thin Quad Flat Package (TQFP)
(until 300 pins)*



SMD

*Pin Grid Array (PGA)
(until 400 pins)*




*Ball Grid Array (BGA)
(greater pin number)*




SMD

Quad Flat No-Lead Plastic Package (QFN)

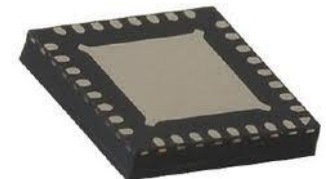

SMD

Introduction Packages

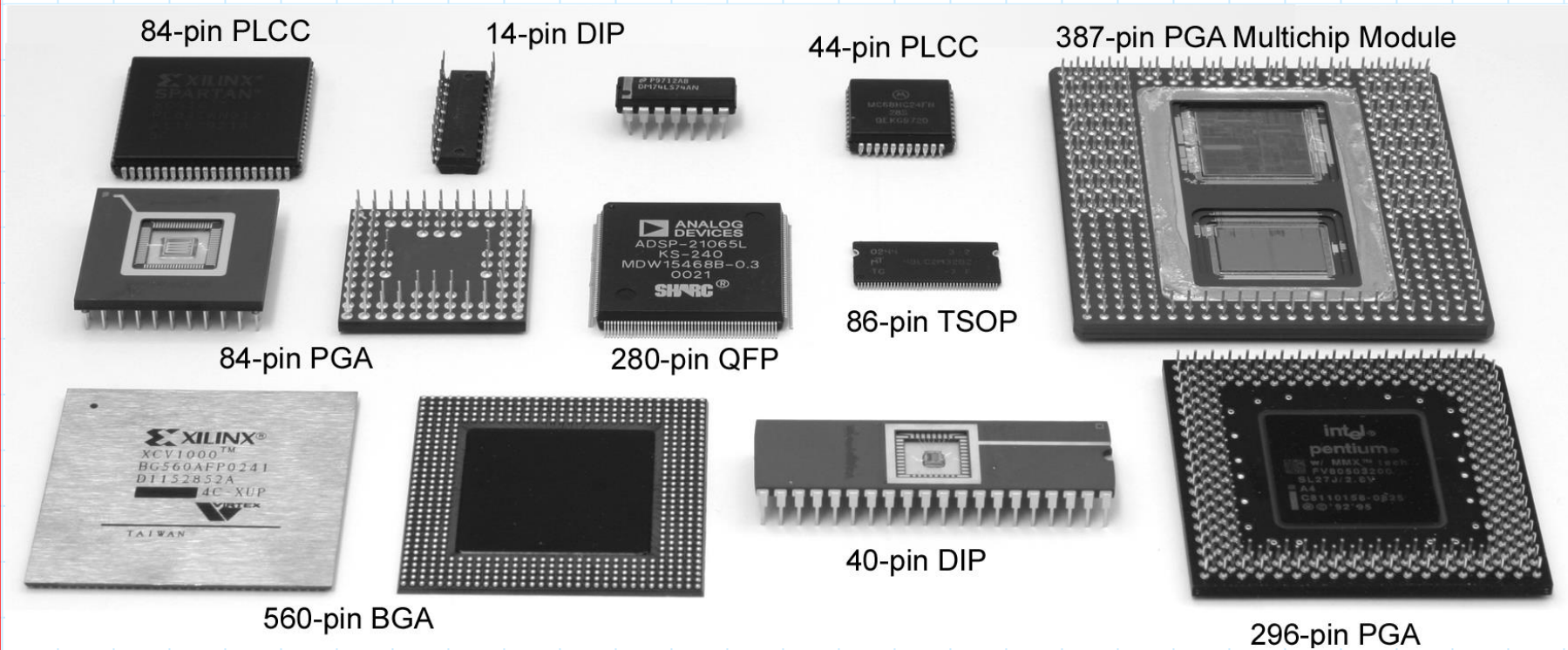


Output types

State of one terminal

One output can have 3 different states: “0”, “1” and Hi-Z (or “Z”)

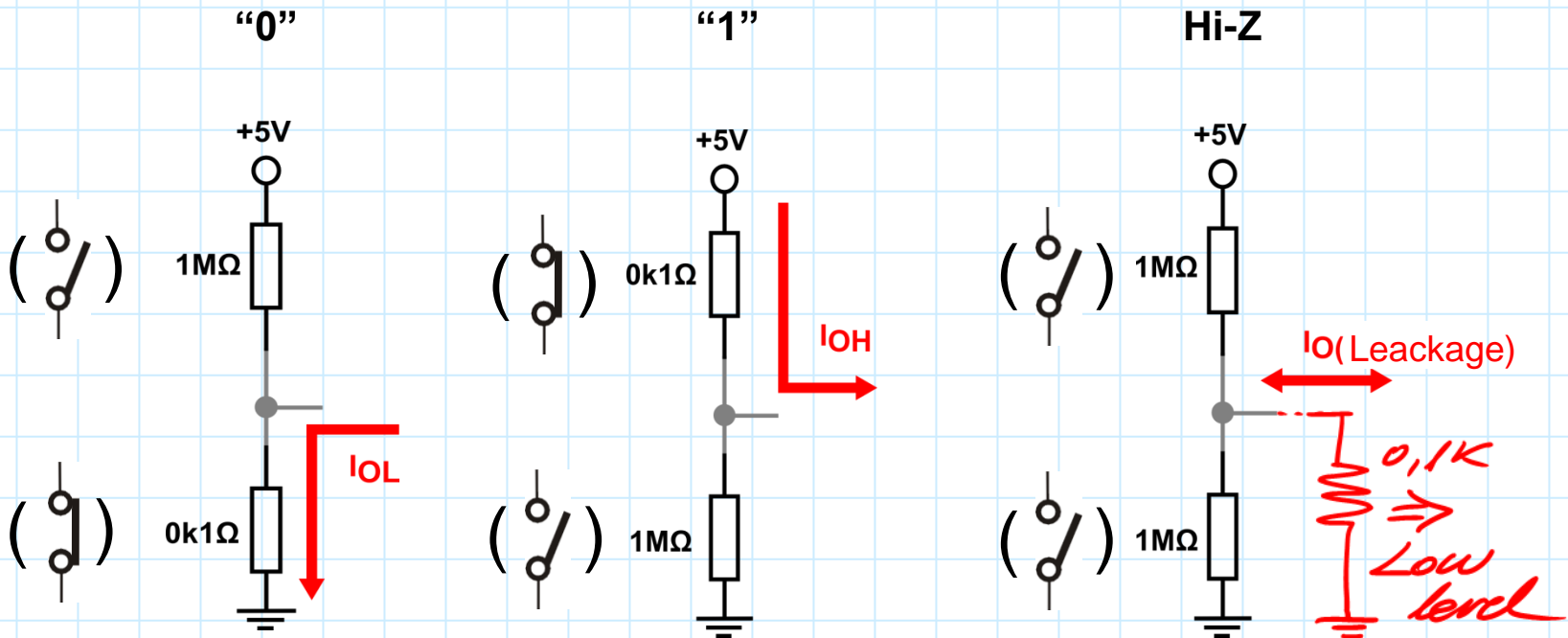- Hi-Z: High impedance output; voltage established **without force**
- “0”, “1”: Low impedance outputs; voltage established **with force**



IBIS model. I/O Buffer Information Specification. Employed by manufacturers to offer a model of their circuits hiding its internal design (SPICE). I/V tables and V/t tables.

Output types

Output types in terms of possible output values:

"0" and "1." Standard Output, Totem-Pole.

↳ Standard TTL

"0" and Z. Open collector and open drain.

Used in processor interrupt lines, serial communication buses such as I2C, lines of digital I/O in μ Controllers

"0", "1" and "Z". Tri-state outputs


Used on data buses in a single-processor computers, and on address buses in systems with multiple processors.

Output types. Totem-pole/Standard (“0” and “1”)

$V_0 = \frac{V_{CC}}{2}$? \Rightarrow undefined!

What value has $F(0,1)$?

¿What value has $F(0,1)$?

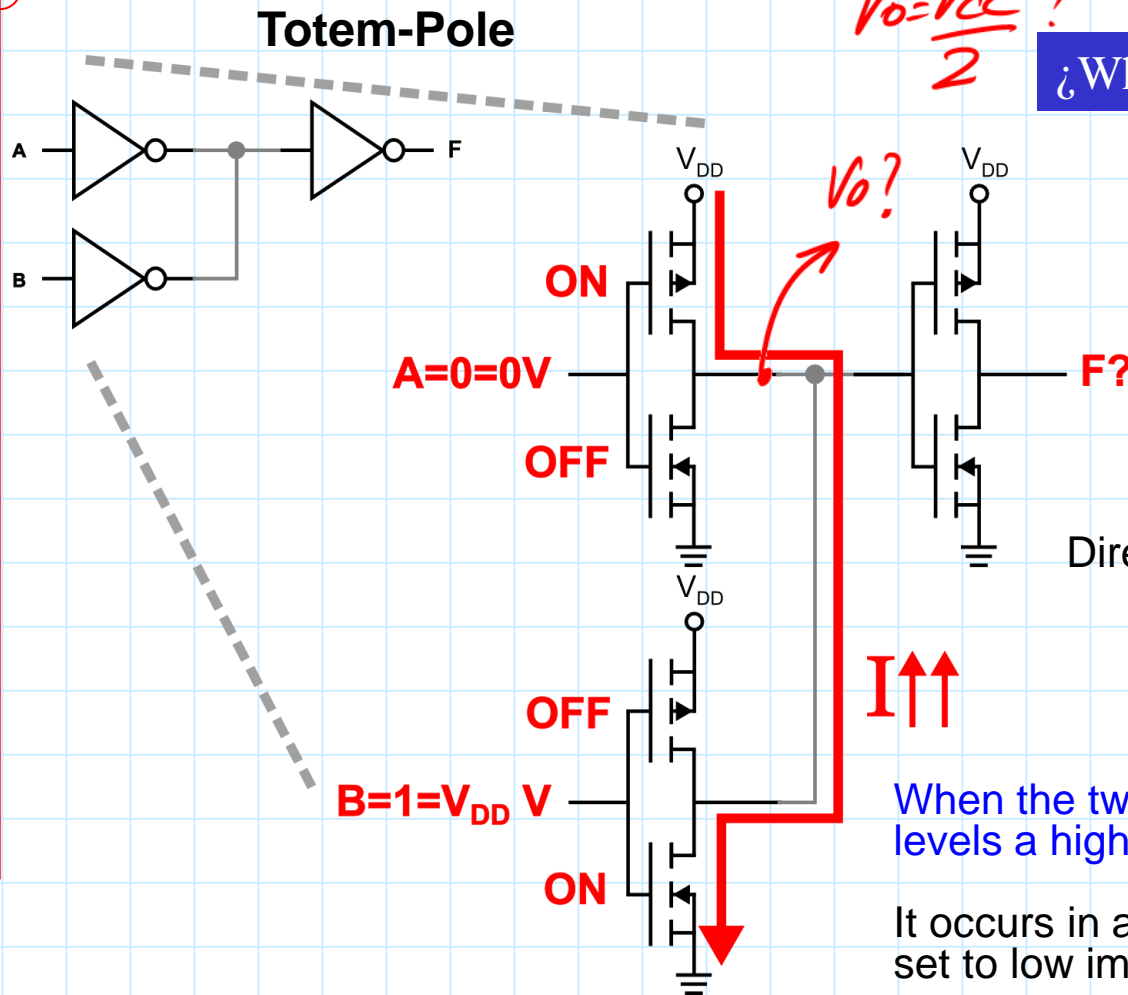

A totem-pole output of a logic gate imposes "strongly" voltage value on the interconnection line.

Direct connection among outputs of two different gates not allowed

When the two outputs have different logic levels a high current path(s) are set!


It occurs in any technology whose outputs are set to low impedance.

Output types.

Open collector/drain ("0" and "Z")

1. Allows the **wired-logic**
2. It is necessary an external "**Pull-up**"-resistor (R_{pu}), to obtain the High level
3. The outputs implement a **wired-AND**


¿What is the value of $F(1,0,1)$?

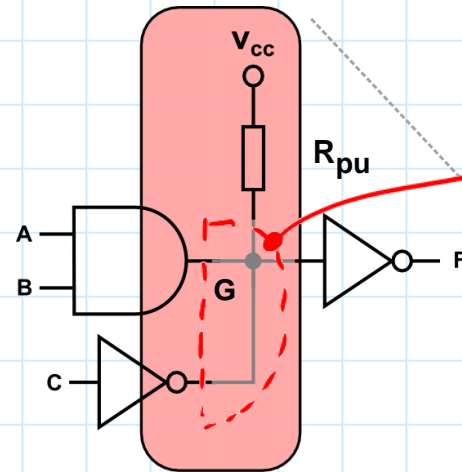

$$G = (A \cdot B) \cdot \overline{C}$$


$$F = \overline{G}$$



TTL-open collector AND gate

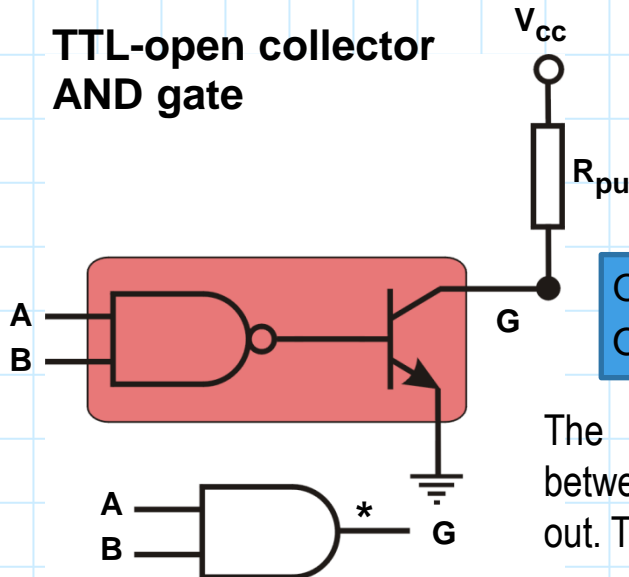

Output "0" → Transistor ON
Output "1" → Transistor OFF

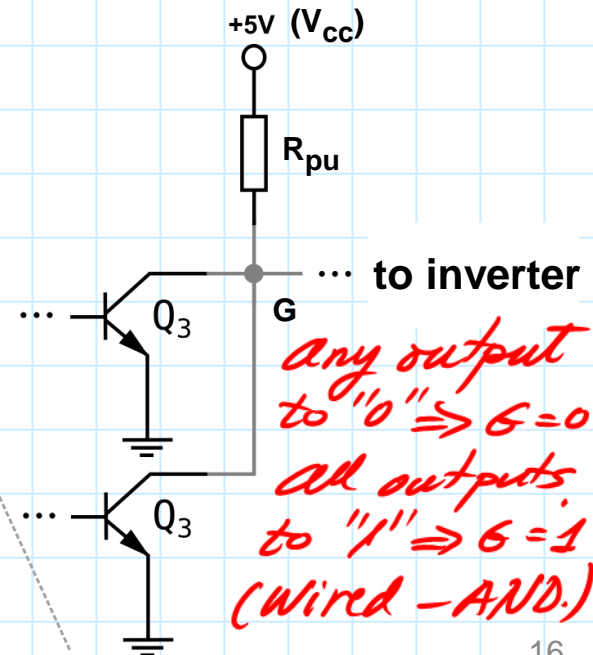The value of R_{pu} is a compromise between speed, power dissipation and fan out. Typical values of the order of $k\Omega$.



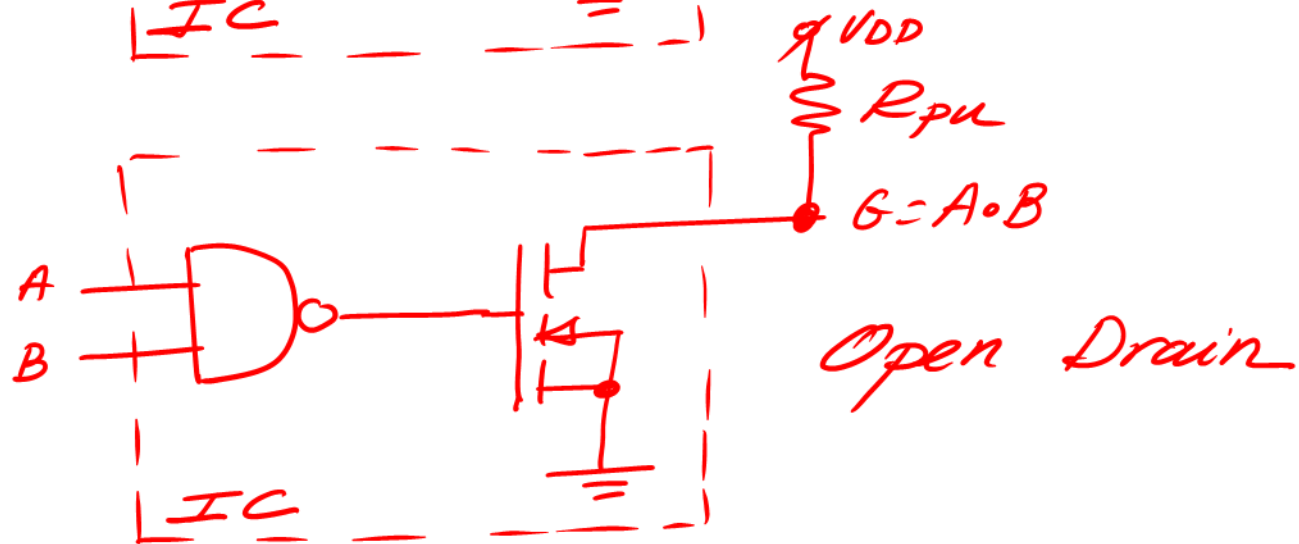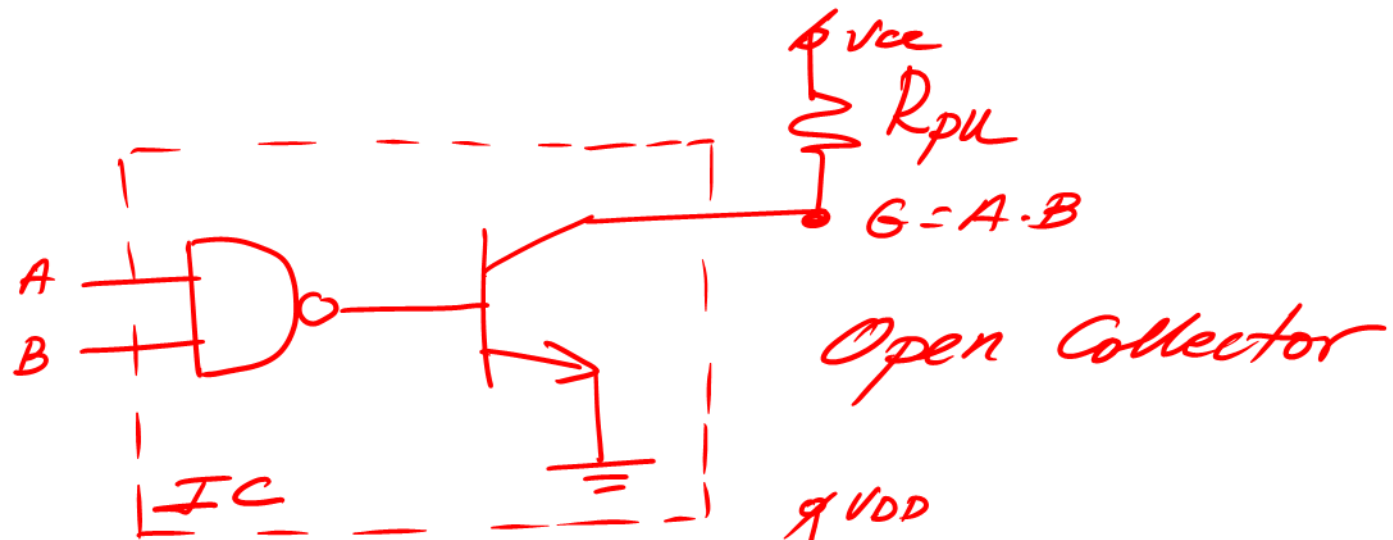

R_{pu} is outside IC (Integrated Circuit)

Output types

Open collector/drain (“0” and Z)

Used in the interruption lines of computers

Open Collector/Drain outputs

