

4.5 Characteristic parameters (related to standard CMOS)

- Supply voltage:
 - V_{DD} typically between 3V and 15V in SSI and MSI chips
 - GND (V_{SS}) = 0 V
 - In 1980's, $V_{DD} = 5V$
 - V_{DD} has been reducing over the years in VLSI chips:
 - High V_{DD} may affect small current transistors of nowadays
 - A low V_{DD} decreases power consumption
 - $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$
 - VLSI chips have normally with 2 voltage supplies:
 - Logic "Core": low V_{DD} (e.g. 1V) \rightarrow *Low power*
 - I/O cells: high V_{DD} (e.g. 2.5V) \rightarrow *High current*

4.5 CMOS characteristic parameters (2)

- Power Consumption:
 - Static regime: virtually null (\approx nA, pA), as there is always a transistor in cut-off mode (PMOS or NMOS)
 - Leakage currents:
 - Insulated Gate \rightarrow *Now high K dielectric instead of SiO_2*
 - Subthreshold (when $V_{GS} < V_T$ if V_T is very small) \rightarrow *reverse currents*
 - Increasingly important in VLSI (a billion transistors nowadays)

$$P_{\text{leakage}} = V_{DD} \times I_{\text{leakage}}$$

\rightarrow *Provoques heating \Rightarrow Less integration density*


$1\text{nA} \times 1000 \cdot 10^6 = 1\text{A}!!$

4.5 CMOS characteristic parameters (3)

- Dynamic regime: $P_d = (V_{DD})^2 C_L f_i$, where:


- $C_L \rightarrow$ parasitic capacitance of the load
- $f_i \rightarrow$ switching frequency of inputs
- This dissipated power is due to:
 - loading / unloading of C_L *Great*
 - Current peaks during transitions: the two transistors (PMOS and NMOS) conduct simultaneously. *Small*
- Dynamic power consumption is the most important in CMOS technology:

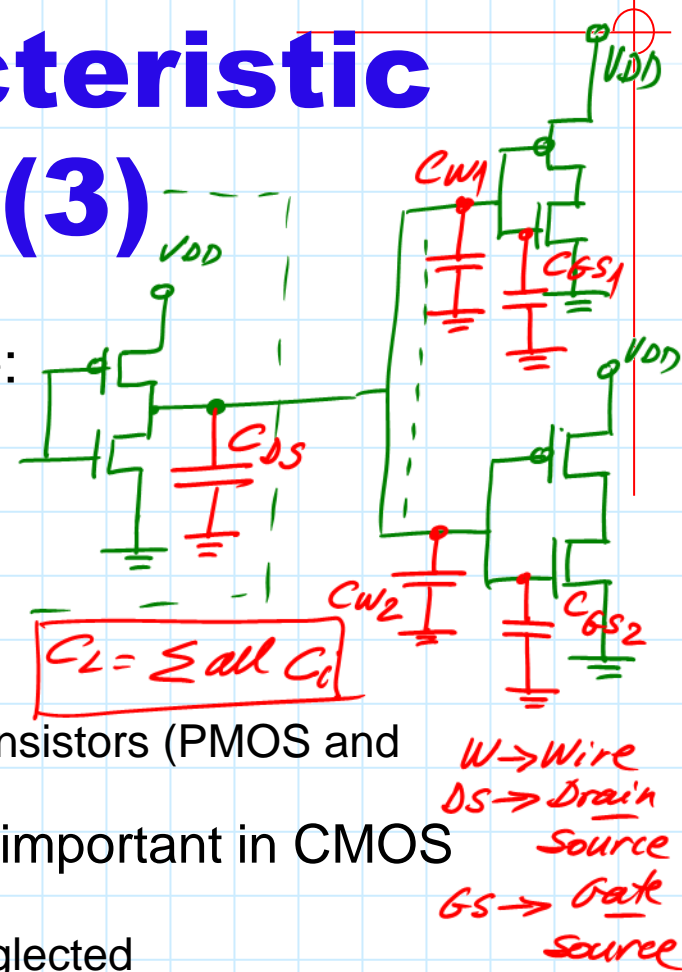- In fact, static power consumption can be neglected
- Note: If we refer P_d to the clock frequency “f” of the system:
 - $P_d = \alpha (V_{DD})^2 C_L f$ where:
 - $\alpha \rightarrow$ average activity factor of the inputs (average number of transitions in one clock cycle)
 - $\alpha < 1 \rightarrow$ Normally, $\alpha < 0.5$: Input freq. is equal or less than $f/2$



4.5 CMOS characteristic parameters


(4): Dynamic power consumption

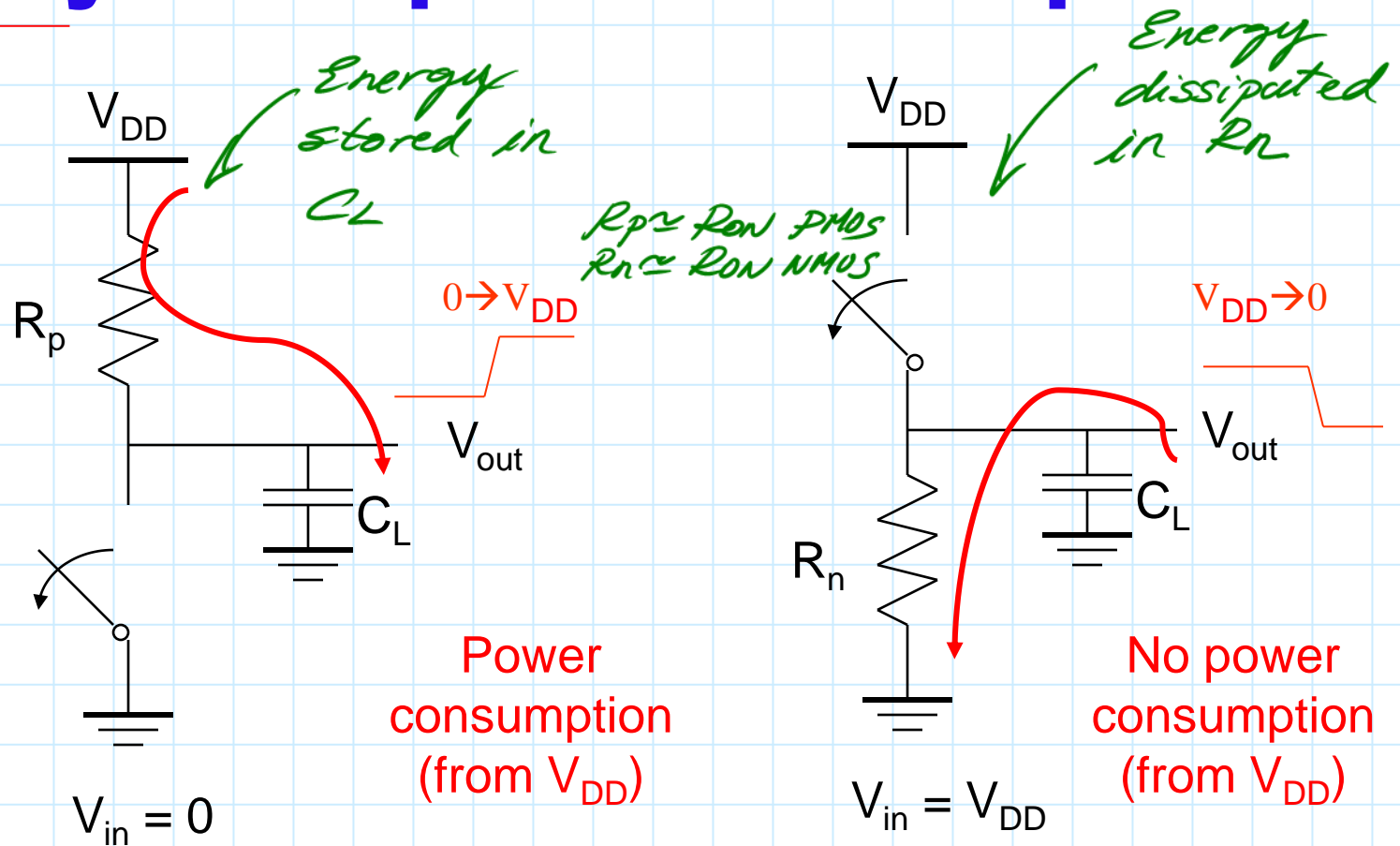

- The relevant dynamic consumption occurs in the transition $L \rightarrow H$
- In the transition $H \rightarrow L$ there are only consumption due to simultaneous conduction of 2 transistors: short circuit.

 4.5 CMOS characteristic parameters (5)

- Logic levels. Noise Immunity
 - Very ideal transfer curve



Standard CMOS values:

$$V_{OHmin} = V_{DD} - 0.1V$$

$$V_{OLmax} = 0.1V$$

$$NM \approx 30\% V_{DD}$$

(1.5V for $V_{DD}=5V$)

Excellent noise immunity (increases with V_{DD})

** TTL : 0.4V only!*

4.5 CMOS characteristic parameters (6)

- Current levels. FAN-OUT (Standard CMOS current values)

I_{OH}	-0.5 mA	High level output current	Exits
I_{OL}	0.5 mA	Low level output current	Enters
I_{IH}	10 pA	High level input current	Enters
I_{IL}	-10 pA	Low level input current	Exits

- Very small input currents → We can connect a lot of inputs to a single output

Static fan-out

$$Fan-Out_L = \left| \frac{I_{OL}}{I_{IL}} \right| = 50.000.000 \quad \swarrow \quad Fan-Out_H = \left| \frac{I_{OH}}{I_{IH}} \right| = 50.000.000$$

- Real constraint to not increase the delays and dynamic power consumption: the manufacturer recommends Fan-out = 50

dynamic fanout the most important!

4.5 CMOS characteristic parameters (7)

- Propagation delays

$$t_p = \frac{1}{2}(t_{pLH} + t_{pHL}) \approx \frac{C_L}{2V_{DD}} \left(\frac{1}{K_p} + \frac{1}{K_n} \right)$$

- Depend on V_{DD} , C_L and K of transistors


- Lower delay if high V_{DD}
- Higher delay for high C_L
- Lower delay if high K

$$K = \frac{1}{2} \mu C_{ox} \frac{W}{L}$$

- t_{pLH} and t_{pHL} can be equal, adjusting the NMOS and PMOS transistors size

- CMOS is now very fast, with similar delays to TTL

- High Speed CMOS Subfamilies

 


$$\mu_n \approx 3\mu_p$$

$$\left(\frac{W}{L}\right)_p \approx 2\left(\frac{W}{L}\right)_n$$

- Product Propagation Delay * Power consumption (PDP):
 $t_p * P \rightarrow \text{pJ}$, rather low due to low consumption, although there is a small increase because propagation delays

RC model for propagation delay

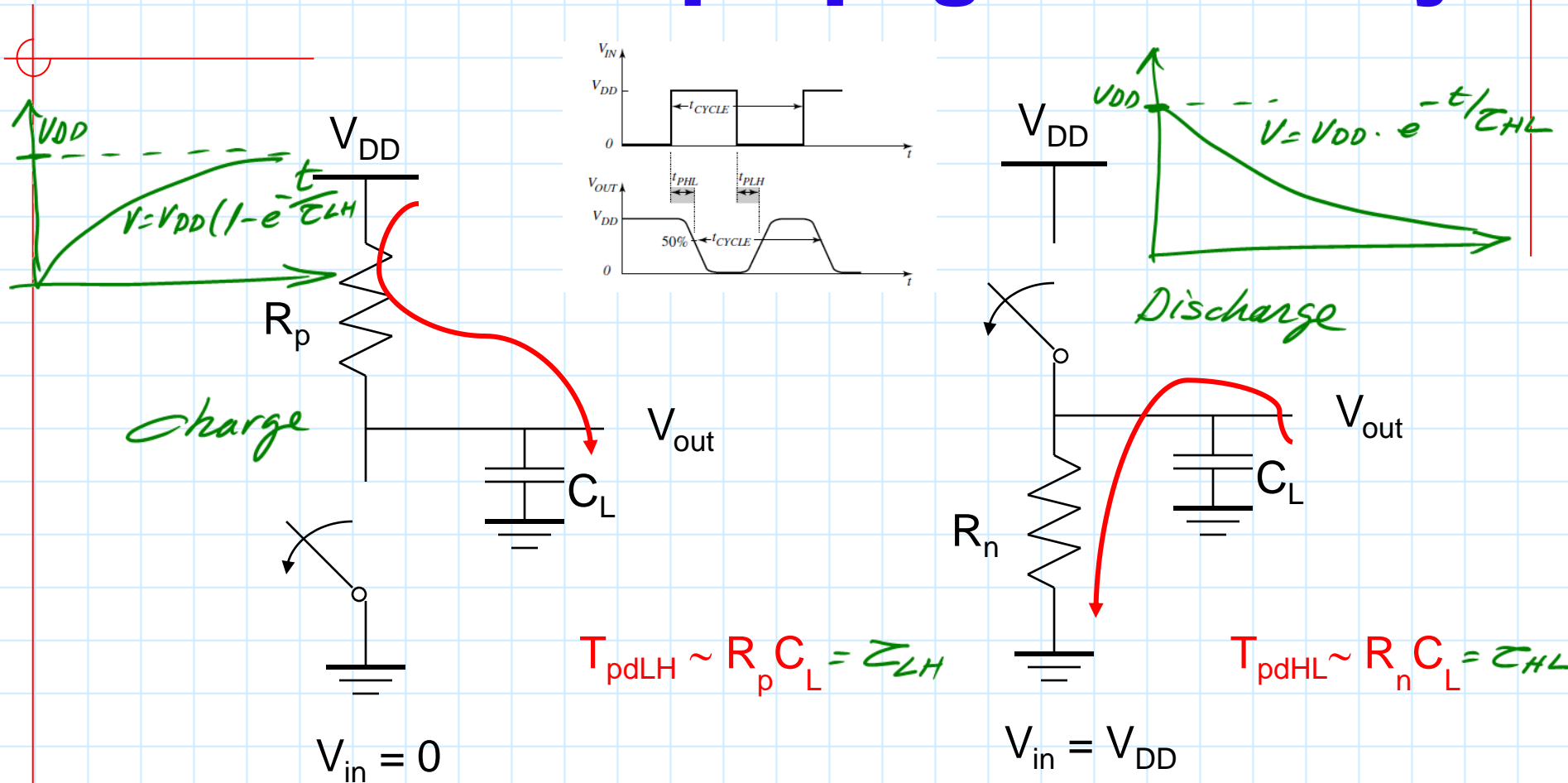

- The delays are given by the charging time of C_L through R_p , and by the discharging time of C_L through R_n

4.6 CMOS subfamilies

- CD 4XXX : original family
 - 4XXXA: conventional
 - 4XXXB: with output buffer
- 74CXXX: TTL functionally CMOS compatible (pins and functions), but not electrically
- 74HCXXX: high speed CMOS
- 74HCTXXX: high speed CMOS with TTL compatible inputs
- 74ACXXX: Advanced high speed CMOS
- 74ACTXXX: Advanced high speed CMOS with TTL compatible inputs
- 74FCTXXX: Fast CMOS, TTL compatible
- BCT: BiCMOS (Bipolar-CMOS)
- ABT: Advanced BiCMOS
- LVC, ALVC: Low Voltage CMOS

4.6 CMOS subfamilies (2)

- The HC, AC and BCT subfamilies:
 - Have higher output current than standard CMOS
 - Are faster
 - The logic levels are not as extreme
 - More restricted supply voltage (between 2V and 6V)
- The HCT, ACT and FCT subfamilies:
 - Have TTL compatible inputs and CMOS outputs
 - Have a voltage supply of +5 V, as TTL
- LVC and ALVC subfamilies:
 - Work with V_{DD} less or equal to 3.3V (2.5, 1.8, 1.5,...)
 - Low-power applications

4.6 CMOS subfamilies (2)

- Example: 54/74HC00 (4 2-input NAND gates)
 - 54HC: military version (it works between -40°C to $+85^{\circ}\text{C}$)
 - 74HC: commercial version (it works between -55°C to $+125^{\circ}\text{C}$)
- VDD between 2V and 6V (typical = +5V)
 - $V_{IHmin} = 3.15\text{V}$, $V_{ILmax} = 1.35\text{V}$
 - $V_{OHmin} = 3.84\text{V}$, $V_{OLmax} = 0.33\text{V}$
 - $I_{IHmax} = 1\mu\text{A}$, $I_{ILmax} = -1\mu\text{A}$
 - $I_{OHmax} = -4\text{mA}$, $I_{IHmax} = 4\text{mA}$
 - $I_{CC(typ)} = 2\mu\text{A}$ (average static current consumption)
 - $T_{pd(typ)} = 9\text{ ns}$ (average delay)
 - C_{pd} (gate capacity, without load) = 22pF
 - Comparing with standard CMOS:
 - Less extreme output voltage levels
 - Lower noise margin
 - Higher output currents
 - More speed

5V

	HC CMOS	
V_{OHmin}	3.84	4.9
V_{IHmin}	3.15	3.5
V_{ILmax}	1.35	1.5
V_{OLmax}	0.33	0.1
N_{MH}	0.69	1.4
N_{ML}	1.02	1.4