 


UNIT 5. SEMICONDUCTOR MEMORY TECHNOLOGY. PROPOSED QUESTIONS AND EXERCISES

- 1) A memory has 2048 words of 32 bits. What is its storage capacity in KBytes?
[A] 2KB
[B] 4KB
[C] 8KB
[D] 16KB
- 2) Given a 2^{14} -word semiconductor memory and provided that each word has 32 bits, we can conclude that:
[A] It requires 14 address lines
[B] It requires 6 address lines
[C] Its storage capacity is 16KBytes
[D] Its storage capacity is 64Kbits
- 3) Concerning the mask-programmed ROMs, we can state that:
[A] They are volatile memories which lose their content when power is switched off.
[B] They are no random access memories.
[C] They are programmed during the manufacturing process.
[D] We can re-write its content by using the appropriate programming device.
- 4) The data stored in a given address of SRAM memory are lost when:
[A] Power is switched off.
[B] We read the data in this address.
[C] It passes longer time than the memory refresh time.
[D] None of the above.
- 5) A ROM is:
[A] A non-volatile memory
[B] A volatile memory
[C] A read/write memory
[D] A memory based on FAMOS cells
- 6) The storage cell in a SRAM is:
[A] A fuse
[B] A capacitor
[C] A flip-flop
[D] An NMOS transistor
- 7) The storage cell in a DRAM is:
[A] A fuse
[B] A capacitor
[C] A flip-flop
[D] An NMOS transistor
- 8) The storage cell in a FLASH is:
[A] A fuse
[B] A capacitor
[C] A flip-flop
[D] A FAMOS transistor
- 9) A DRAM should be:
[A] Regularly replaced
[B] Regularly refreshed
[C] Always enabled
[D] Programmed before each use


- 10) A FLASH memory is:
- [A] Volatile
 - [B] Read-only memory
 - [C] A read/write memory
 - [D] Non-volatile
 - [E] The answers [A] & [C]
 - [F] The answers [C] & [D]
- 11) Signal the FALSE statement among the following related to semiconductor-based memories:
- [A] PROMs are non-volatile, random access memories.
 - [B] The cells inside ROMs are implemented in the manufacturing process, then they are not programmable by the end user.
 - [C] SRAMs are non-volatile random access memories, as soon as they do not need a refreshing process.
 - [D] The cells of EPROMs and FLASHs are based on FAMOS transistors that have floating gates for cutting the selected transistors.
- 12) Indicate the pros and cons of flash memory in relation to SRAM and DRAM memories.
- 13) Given a DRAM chip of a capacity of $2M \times 1$, we can state that:
- [A] Its internal structure can be an array of 2^{11} rows and 2^{10} columns.
 - [B] It has a capacity of 2MBytes.
 - [C] It has 20 address lines and 1 data line
 - [D] We can build a 16Mbytes memory grouping 8 of the same type.

- 14) Given the memory cell of the figure, indicate the CORRECT answer:



- [A] It is a 6T dynamic memory cell
- [B] The input data are in /BL, and output data in BL
- [C] The storage core is the flip-flop formed by transistors M1-M2-M3-M4.
- [D] The pass transistors M5 and M6 provide access to the cell in read/write, when $WL = "0"$

 
15) Given the memory cell of the figure, indicate the CORRECT answer:



- [A] It is a 6T dynamic memory cell
- [B] The reading process is: Precharge of BL and /BL; activate WL to '1', and read the bit lines.
- [C] The input data are placed in /BL and the output data in BL.
- [D] The pass transistors M5 and M6 provide access to the cell in read/write, when WL="0"

 
16. Given the memory cell of the figure, indicate the CORRECT answer:

- [A] It is a 6T dynamic memory cell
- [B] For writing a '1' in the cell ($Q=1$ y $\bar{Q}=0$), we have to set /BL to '0' and BL to '1', enabling afterwards the cell setting WL='1'.
- [C] The resistors R_{ON} of all transistors of the cell should be approximately the same value, to properly writing and reading in the cell.
- [D] The connections shown in the figure are wrong. BL and /BL are interchanged.



 
17. Given the memory cell of the figure, indicate the CORRECT answer:

- [A] This is a DRAM cell including the refresh circuit.
- [B] Writing process is the following: precharge BL with the data to be written and /BL with the opposite, activate WL to 0 and wait the data to be written into the cell.
- [C] BL bit line is for data reading, and /BL for data writing.
- [D] Transistors M1, M2, M3 and M4 implement a flip-flop that stores the logic value of the cell.



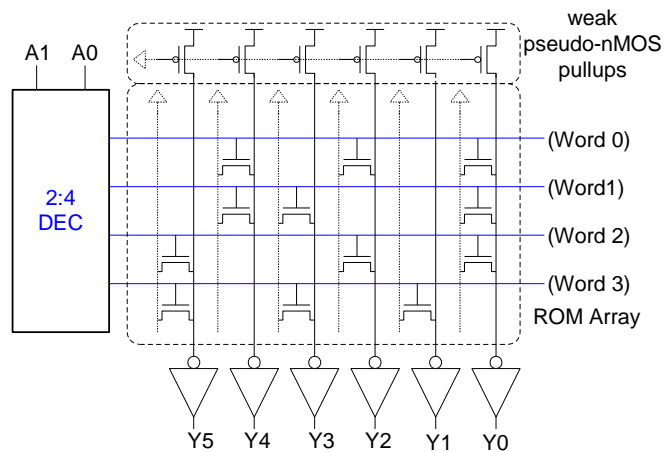
18. Given the memory of figure, point out the FALSE statement:

- [A] This is a ROM memory of 4 words of 6 bits.
- [B] When A1=1 and A0=1, the word "100101" is obtained in the data bus.
- [C] The presence of transistor sets to "0" the cell, but a "1" is read at the output Yx.
- [D] The transistors are placed in the manufacturing process, not allowing subsequently any modification, and giving non-volatility at these memories.



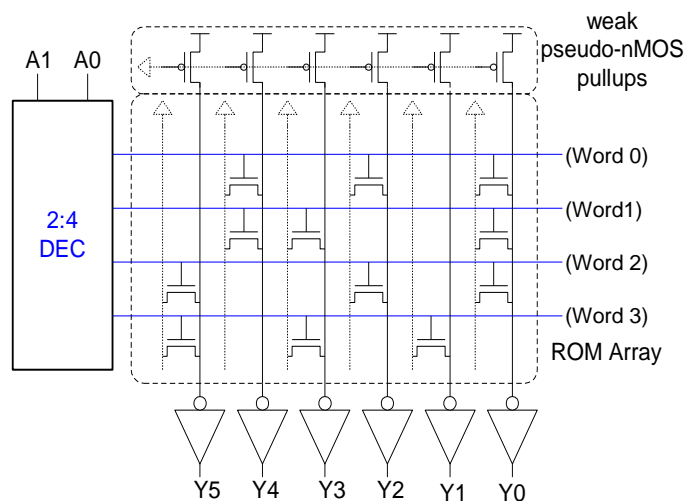19. Given the memory of figure, point out the FALSE statement:

- [A] This is a ROM memory of 4 words of 6 bits.
- [B] When A1=1 and A0=1, the word "100101" is obtained in the data bus.
- [C] The presence of transistor sets to "0" the cell, but a "1" is read at the output Yx.
- [D] Pull up transistors behave as a pull up resistors connected to power supply..




20. Indicate the relative size of transistors of a 6T SRAM cell: (NMOS, PMOS pass transistors). Justify your answer.

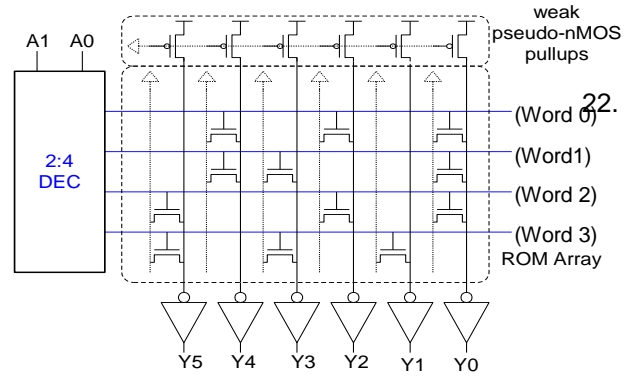
21. Signal the **CORRECT** statement among the following related to the memory of figure:

Note: A1 is the most significant bit and A0 the least significant.

- [A] This is an example of a NAND ROM structure.
- [B] It corresponds to a non-volatile programmable memory, since it is easy to add or remove transistors, at any time by the user.
- [C] When A1=0 and A0=1, the word "011001" is read in the Y5, Y4,..., Y0 data lines.
- [D] The presence of an NMOS transistor puts a '1' in the cell, which is read as '0' in the corresponding output Yx.




 22. Given the memory cell of the figure, indicate the CORRECT answer:



- [A] This is a DRAM cell with 3 transistors.
- [B] Data are stored in the gate capacitance of M1 transistor.
- [C] If we want to write a "1", we set BL="1", WL="1", and the capacitor CS is charged through M1 pass transistor.
- [D] Reading the cell do not require the precharge of BL line.

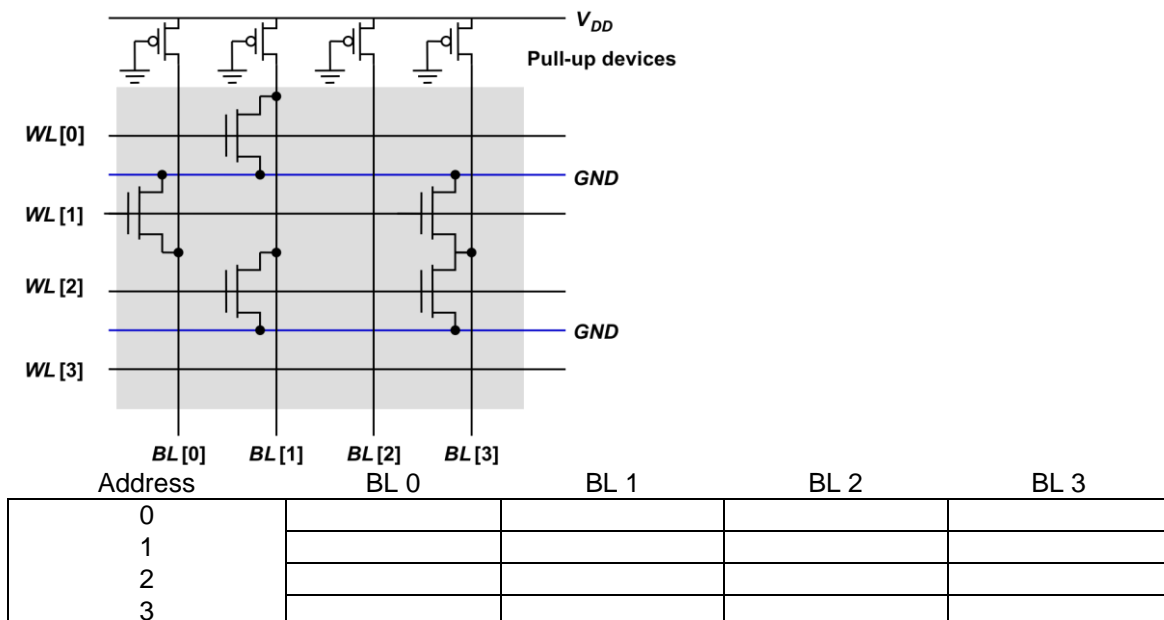23. Determine the values ("0" or "1") of the data stored at addresses 0,1, 2 and 3 of the ROM in the following figure.




24. Draw the basic cell of the FLASH memory and explain its non-volatility.

25. With respect to Flash type semiconductor memories, it can be stated that:

- [A] The storage cell is based on FAMOS transistors, with an intermediate floating gate that is discharged when turning off the power.
- [B] The number of erasing and rewriting operations is unlimited.
- [C] When the floating gate of the FAMOS transistor is charged with electrons, channel formation is prevented, so that the transistor will always be in cut-off region, regardless of the voltage applied in normal gate.
- [D] They are faster than static RAM memories, but slower than dynamic RAMs.

 26. The integrated circuit CY62256, whose pinout is shown in the figure, is a SRAM with a typical access time of about 70ns. Analyzing the pin out of the figure, we can say that:


- [A] The storage capacity is of 16Kbytes (2^{14} words of 8 bits).
- [B] 70 ns is the maximum time it takes for data to be written in the storage cells from which the address is stabilized.
- [C] /CE (pin 20) corresponds to the selection of chip, so it should be maintained to '0' during any read or write operation affecting the chip.
- [D] /WE allows to control the timing of the reading process, while /OE allows to control the timing of the writing process.



27. Design a Full Adder using a ROM NOR. Draw the internal structure and indicate the memory size.

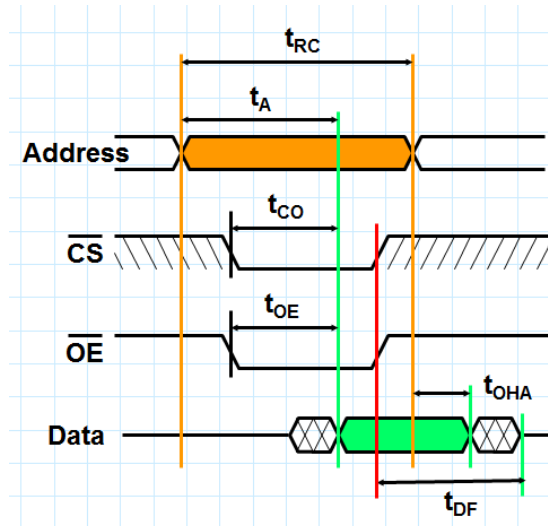
28. Taking into account the following timing diagram, indicate what is the correct statement:

- [A] t_{RC} is the minimum read cycle time.
- [B] t_{DF} is the maximum access time from the valid address.
- [C] The timing diagram does not correspond to a read timing diagram, is actually a write timing diagram.
- [D] The timing diagram is not complete, as Read / Write (RW) line is missing.



 29. Taking into account the following timing diagram, indicate what is the correct statement:

- [A] $(t_{RCD} + t_{CAS})$ is the minimum read cycle time.
- [B] It corresponds to a read timing diagram in a DRAM memory.
- [C] It corresponds to a write timing diagram in a DRAM memory.
- [D] The timing diagram is not complete, as Chip Select (CS) line is missing.



30. Concerning dynamic memory refresh, indicate which is the FALSE:

- [A] It is the periodic re-write operation of the DRAM information.
- [B] It is done by a refresh circuit that can be independent or be inside the DRAM memory.
- [C] Refresh can interfere with the memory access cycles by the CPU.
- [D] In each access to the DRAM, for Read or Write, a whole column of the bit array is refreshed.